

Meter Sensitivity (ohm-per-volt Rating)

① The ohms per volt figure is often called the "sensitivity" of the instrument.

→ Measured in Ω/V or ohm/volt

→ Higher the sensitivity, more accurate is the measurement

→ Sensitivity of meter is defined as $S = \frac{1}{I_m}$

Example: if $I_m = 50 \mu A$



$$\text{then } S = \frac{1}{I_m} = \frac{1}{50 \times 10^{-6}} = 2000 \Omega/V$$

$$S = 2000 \Omega/V$$

$$\Rightarrow \text{Sensitivity} = \frac{\text{ohms}}{\text{volt}} = \frac{1}{\frac{\text{volt}}{\text{ohms}}} = \frac{1}{\text{Ampere}}$$

Note: The sensitivity of a voltmeter is given in ohms-per-volt.

Voltmeter:

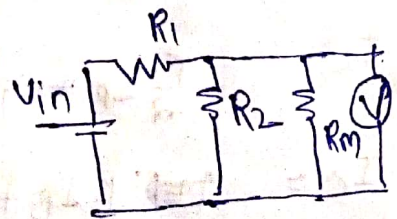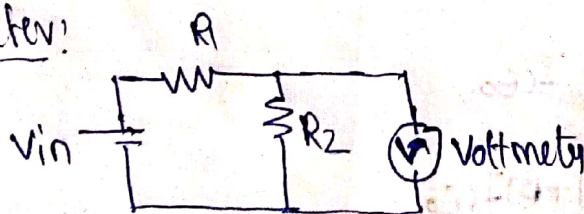


$$V_m = \frac{(R_2 \parallel R_m) V_{in}}{R_1 + (R_2 \parallel R_m)}$$

Prob A simple series ckt of R_1 and R_2 connected to 250 dc source. If the voltage across R_2 is to be measured by the voltmeter having

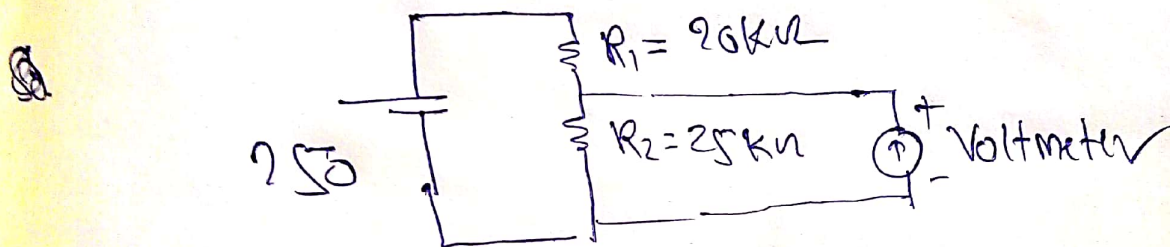- (i) a sensitivity of 500 Ω/V
- (ii) a sensitivity of 10,000 Ω/V

find which voltmeter will read more accurately.
Both the meters are used on the 150 V range



Soln

By voltage divider across R_2 -

$$V = \frac{250 \times 25}{(20+25)} = 138.88V$$

↓ True voltage

Case-i

$$S = 500 \Omega/V$$

The voltmeter resistance will be -

$$R_V = S \times V = 500 \times 150 \\ = \underline{\underline{75k\Omega}}$$

Case-II

$$S = 10,000 \Omega/V$$

$$\rightarrow R_V = 10,000 \times 150 = \underline{\underline{1.5M\Omega}}$$