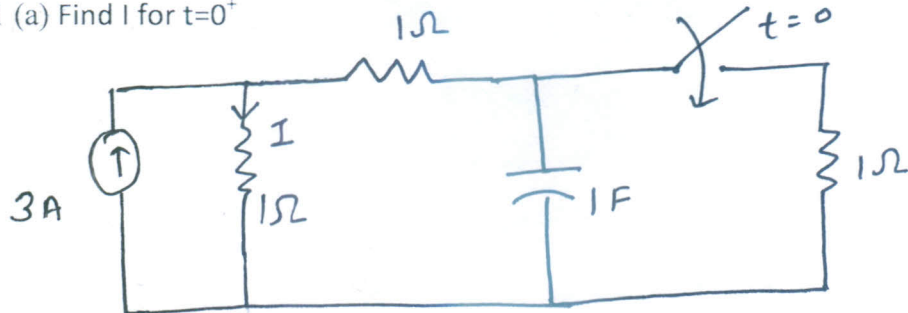



**JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY**  
 Electronics and Communication Engineering  
**Electrical Science-2 (15B11EC211) – 2016 EVEN SEM**  
 TUTORIAL -1 First order circuit response to DC and Non-constant input

Q.1 (a) Find  $I$  for  $t=0^+$



Ans.  $i(0^+) = 3A$

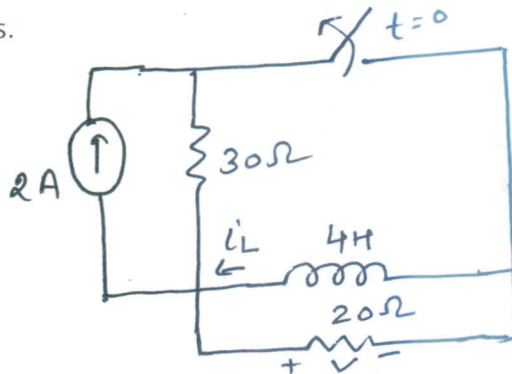
(b) The switch in the circuit shown below has been closed since dinosaurs last walked the earth. If the switch is opened at  $t=0$ , Find  $i_L(0^+)$  and  $V(0^+)$ , the instant after the switch changes.



Ans.  $i_L(0^+) = 2A$


$V(0^+) = 40V$

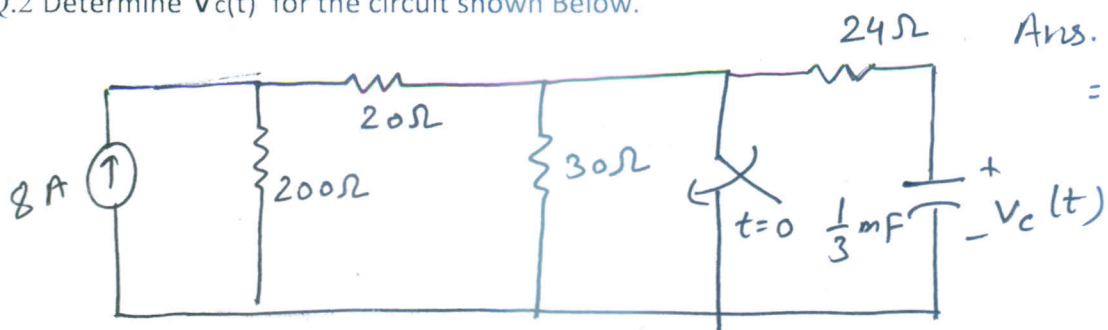Q.2 Determine  $V_c(t)$  for the circuit shown Below.




Ans.  $V_c(t) = 192e^{-125t}$

Q.3 Find  $V(t)$  across capacitor.

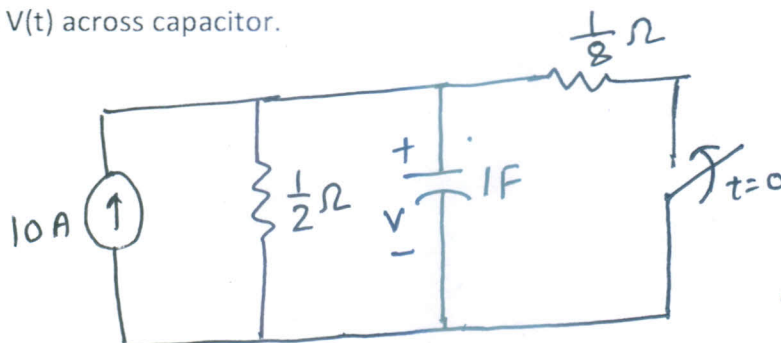


Ans.  $V(t) = 1 + 4e^{-10t}$

Q.4 Find  $i(t)$  for  $t > 0$ .

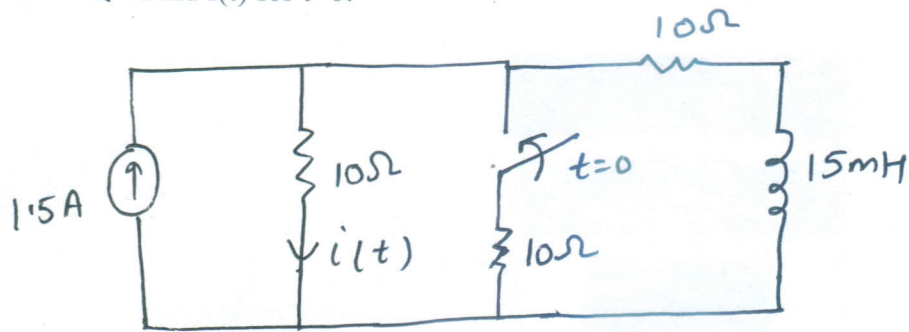

Ans.  $i(t) = 0.5 - 0.125e^{-1000t}$  A


Q.5. Find  $i(t)$  for  $t > 0$ .

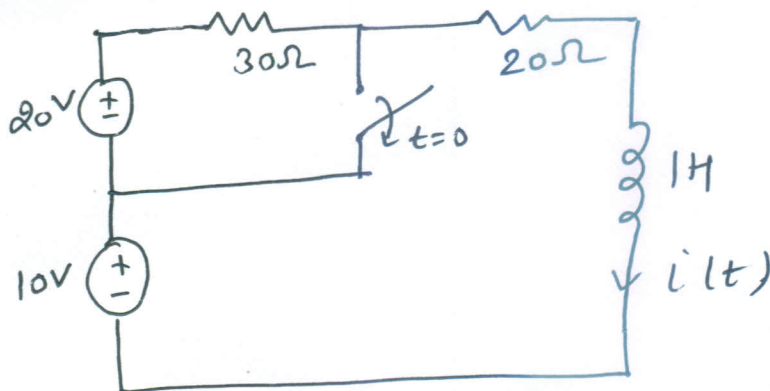

Ans.  $i(t) = 0.6 - 0.1e^{-50t}$


Q.6. After having been closed for a long time, the switch is opened at  $t=0$ .

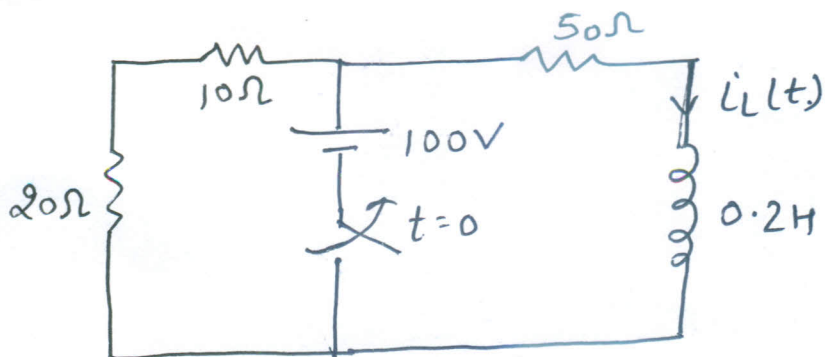(a) Find  $i_L(t)$  for  $t > 0$  (b) Find  $t_1$  if  $i_L(t_1) = 0.5 i_L(0)$ .



Ans.  
 $i_L(t) = 2e^{-400t}$   
 $t_1 = 1.73 \text{ msec.}$

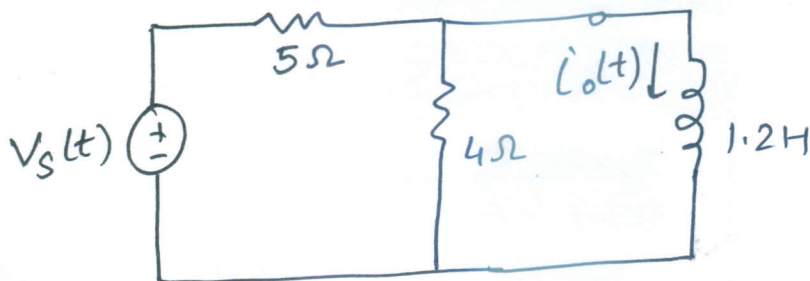
Q.7 The input to the circuit shown in figure is the voltage of the voltage source  $V_s(t)$ . The output is the current across the inductor  $i_o(t)$ . Determine the output of this circuit when the input is  $V_s(t) = -7 + 13 u(t)$  V.



Ans.  $i_o(t) = \{-1.4 \text{ A} \quad t \leq 0$

$1.2 - 2.6 e^{-1.85t} \text{ A} \quad t > 0 \}$

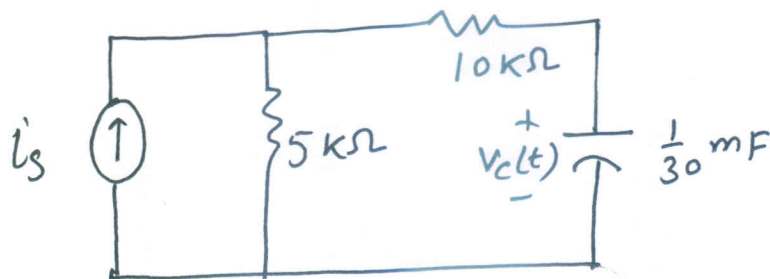Q.8. Find  $V_c(t)$  for  $t > 0$  for the circuit shown in fig. when  $i_s = [2 \cos 2t] u(t)$  mA.



Ans.  $V_c(t) = -5 e^{-2t} + 5 \cos 2t + 5 \sin 2t \text{ V}$