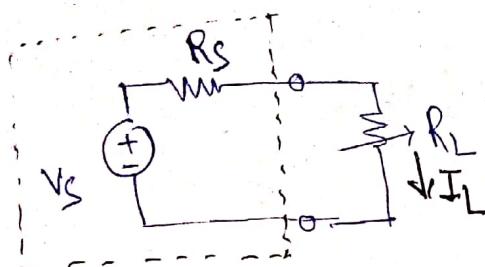


Maximum Power Transfer Theorem in DC Network

Statement: Maximum power transfer theorem states that "maximum power is transferred from the source to the load when load resistance is equal to the thevenin's equivalent resistance". i.e. $R_L = R_{th}$



Practical voltage source

$V_s \rightarrow$ Source voltage

$R_s \rightarrow$ Internal source resistance of voltage source

$R_L \rightarrow$ Load resistance.

From the above figure -

$$I_L = \frac{V_s}{R_s + R_L} \quad \text{(i)}$$

$$P = V \cdot I$$

$$P = \frac{V^2}{R}$$

$$P = I^2 R$$

Now, power transferred to load resistance

$$P_L = I_L^2 \cdot R_L \quad \text{(ii)}$$

Put the value of I_L in the equation (ii)

$$P_L = \left(\frac{V_s}{R_s + R_L} \right)^2 \cdot R_L \quad \text{(iii)}$$

for max^M power across the load, apply max^M and min^M-

To get maximum power transfer, differentiate equation (iii)

w.r.t. R_L , where R_L is variable

$$\frac{dP_L}{dR_L} = \frac{d}{dR_L} \left[\frac{V_s^2 R_L}{(R_s + R_L)^2} \right]$$

For maximum power —

$$\frac{dP_L}{dR_L} = 0$$

i.e. $\frac{dP_L}{dR_L} = \frac{d}{dR_L} \left(\frac{V_s^2 R_L}{(R_s + R_L)^2} \right) = 0$

$= V_s^2 \left[\frac{(R_s + R_L)^2 \times 1 - R_L \times 2(R_s + R_L)}{(R_s + R_L)^4} \right] = 0$

{ Here R_s and V_s are fixed quantity

$V_s \neq 0 ; (R_s + R_L)[R_s + R_L - 2R_L] = 0$

$$R_s = R_L \quad \underline{\underline{V.V.}}$$

i.e. load resistance $=$ internal resistance of source voltage
 (R_L) \downarrow (R_s)

This is a condition of maximum power transfer.

What is the value of maximum power —

Substitute the value of $R_s = R_L$ in the equation (iii)

We get

$$P_L = \frac{V_s^2 \cdot R_L}{(R_L + R_L)^2} = \frac{V_s^2 \cdot R_L}{(2R_L)^2} = \frac{V_s^2}{4R_L} = \frac{V_s^2}{4R_s}$$


$$P_{\max} = \frac{V_s^2}{4R_s} \text{ watt} \quad \underline{\underline{V.V.}}$$

~~Note~~ and maximum current $I_{L\max} = \frac{V_s}{R_s + R_s} = \frac{V_s}{2R_s}$

$[: R_s = R_L]$

Maxm power transfer theorem is applicable when load is variable
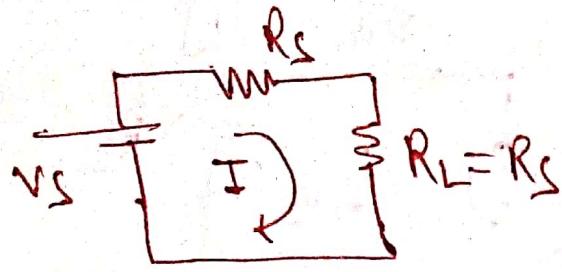
$$\text{Efficiency } (\eta) = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\%.$$



$$I = \frac{V_s}{2R_s}$$

$$P_{\text{out}} = \frac{V_s^2}{4R_s} \rightarrow \text{output power}$$

What is the power given by the battery -

$$P_{\text{in}} = -V_s \times I = -\frac{V_s \times V_s}{2R_s}$$

$$P_{\text{in}} = \frac{-V_s^2}{2R_s}$$

minus sign means power given by the battery

$\left. \begin{array}{l} - \rightarrow \text{Power given} \\ + \rightarrow \text{Power absorb} \end{array} \right\}$

Therefore,

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\% = \frac{\frac{V_s^2}{4R_s}}{\frac{-V_s^2}{2R_s}} \times 100\%$$



$$\eta = \frac{2}{4} \times 100\%$$

$$\boxed{\eta = 50\%}$$

Note
For max^m power across the load, the $\eta = 50\%$.

remain power loss across the R_s

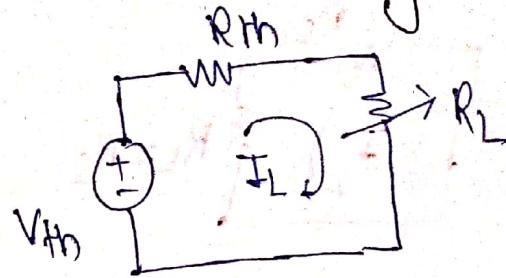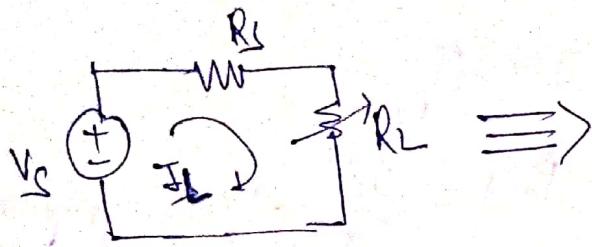Maximum Power transfer based problem solve using Thévenin's theorem



$$P_{\max} = \frac{V_s^2}{4R_s} = \frac{V_s^2}{4R_L}$$

and


$$R_s = R_L$$

$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}}$$

and


$$R_L = R_{Th}$$

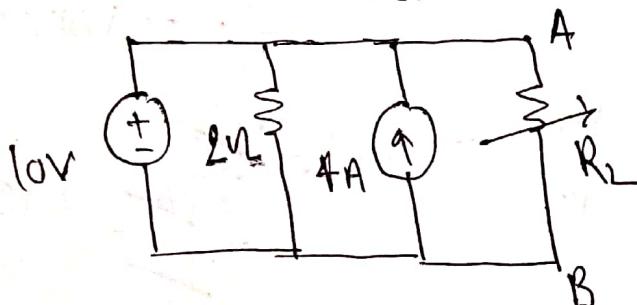Prob: 1 find the value of R_L and P_{\max} of the given circuit.



Solⁿ: Apply the Thévenin's theorem - Remove load resistance (R_L)
 for $V_{Th} \rightarrow$ open terminal voltage
 $R_{Th} \rightarrow$ Resistance across open terminal


for V_{Th} :-

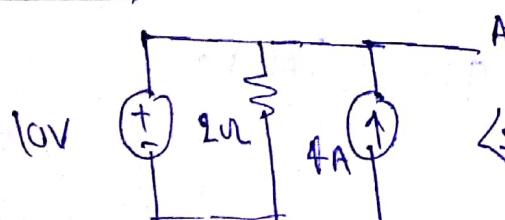

→ Voltage source → S.C
 → Current source → O.C

$$V_{AB} = V_{Th} = 10 \text{ Volt}$$

for R_{Th}

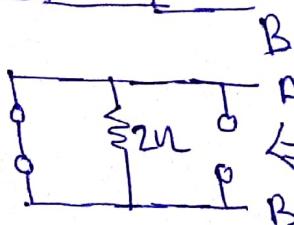


$$R_{AB} = R_{Th} = 0$$

$$\left\{ \sum I \Rightarrow I \right\}$$


$$\text{For } P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(10)^2}{4 \times 0} = 0 \text{ Watt.}$$

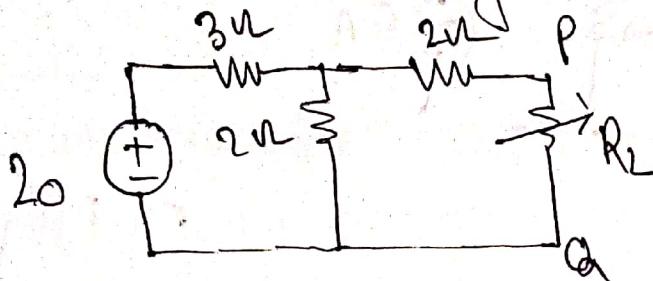Prob: 2 calculate the value of R_L and P_{\max} of the following circuits.




Soln: Apply the Thvenin's theorem to find the value of R_{Th} and V_{Th} .

For V_{Th}

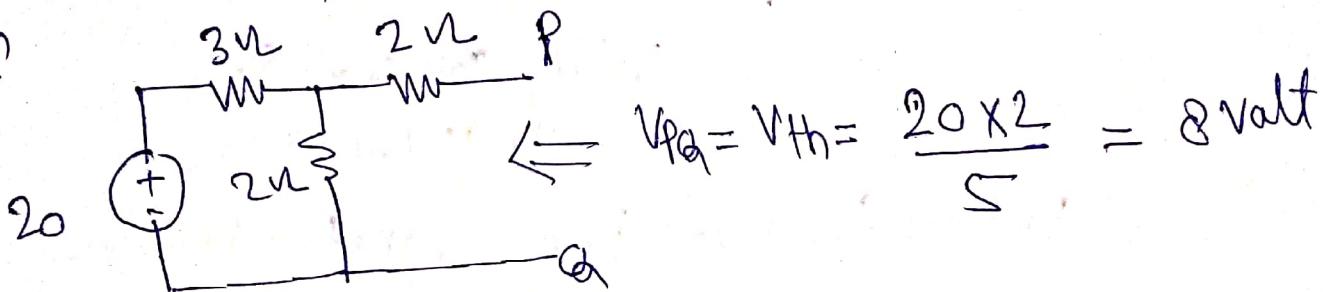

for R_{Th}

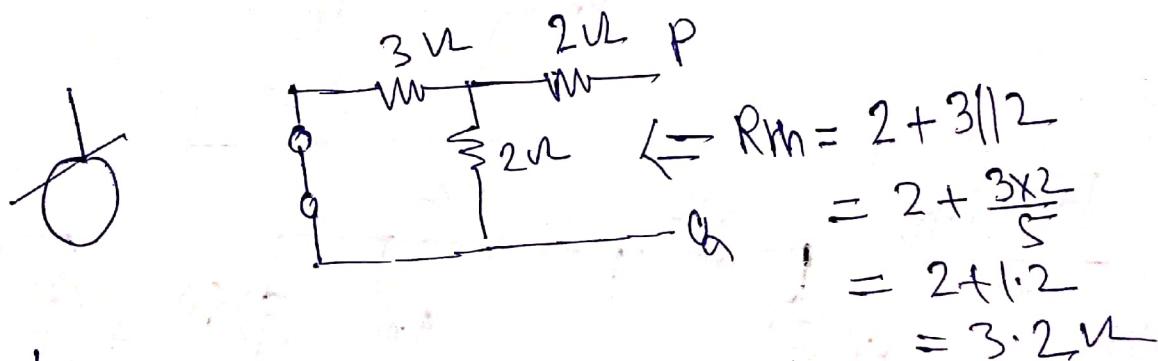


Therefore, the value of $P_{\max} = \frac{V_{Th}^2}{4R_{Th}}$

$$P_{\max} = \frac{8^2}{4 \times 3.2} = \frac{64}{4 \times 3.2} = 5 \text{ Watt}$$

$$P_{\max} = \frac{(4 \times 10)^2}{4 \times 32} = 5 \text{ Watt}$$

and

$$R_L = R_{Th} = 3.2 \Omega$$

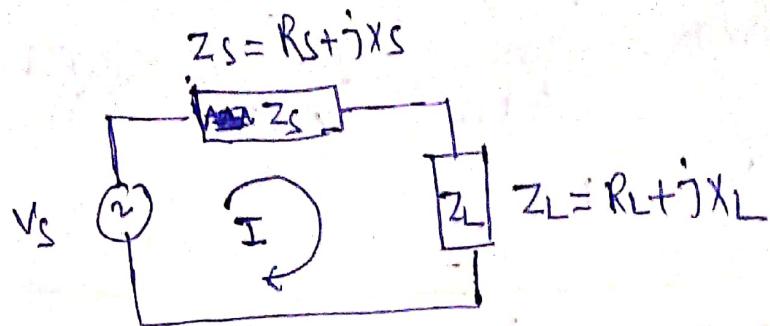

$$I = \frac{V_s}{Z_S + Z_L} = \frac{V_s}{(R_s + jX_s) + (R_L + jX_L)}$$

$$I = \frac{V_s}{(R_s + R_L) + j(X_s + X_L)}$$

$$|I| = \sqrt{\frac{V_s}{(R_s + R_L) + j(X_s + X_L)}} = \frac{V_s}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

$$|I| = \frac{V_s}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}} \quad \text{--- (i)}$$

Power across the load (R_L) = Active power across load (R_L)

Note: Active power is always flow across the R_L but not across the ~~reactive power~~ reactance.

$$P_L = I^2 \cdot R_L \quad \text{--- (ii)}$$

Substitute the value of (i) in the (ii)

$$P = I^2 Z_L \rightarrow \text{gives complex power}$$

Also called Ph
Apparent power

$$P_L = I^2 R_L = \frac{V_s^2 \cdot R_L}{(R_L + R_S)^2 + (X_S + X_L)^2} \quad (\text{ii})$$

↓
It is a power across the load.

For maximum power \rightarrow Differentiate power w.r.t. variable element

Possible cases for maximum power:

Case-1 When R_L is variable and X_L is fixed.

$$\frac{dP_L}{dR_L} = 0 \quad (\text{Apply max and min.})$$

From-(ii)

$$\frac{dP_L}{dR_L} = 0 = \frac{\left[(R_L + R_S)^2 + (X_S + X_L)^2 \right] \cdot V_s^2 - V_s^2 \cdot R_L \times [2(R_L + R_S)]}{\left[(R_L + R_S)^2 + (X_S + X_L)^2 \right]^2}$$

$$R_L^2 + R_S^2 + 2R_L R_S + (X_S + X_L)^2 = 2R_L^2 + 2R_L R_{\text{th}}$$

$$R_L^2 = R_S^2 + (X_L + X_S)^2$$

$$R_L = \sqrt{R_S^2 + (X_L + X_S)^2} \quad (\text{A})$$

Case-2 only X_L is variable, R_L is fixed.

$$\frac{dP_L}{dX_L} = 0 = \left[(R_L + R_S)^2 + (X_L + X_S)^2 \right] X_0 - V_s^2 R_L [2(X_L + X_S)] =$$

$$X_L + X_S = 0; \quad X_L = -X_S \quad (\text{B})$$

Case-3 When R_L and X_L are variable.

It means that both condition (A) and (B) should be satisfied.

$$\text{i.e. } R_L = \sqrt{R_s^2 + (X_L + X_S)^2}$$

and

$$X_L = -X_S$$

From equation (A) and (B). Substitute the value of X_L in
of B into A.

$$R_L = \sqrt{R_s^2 + (X_S - X_S)^2} = R_s$$

$$\boxed{R_L = R_s}$$

So for Case-III

$$\boxed{R_L = R_s \text{ and } X_S = -X_L}$$

Given in the circuit —

$$Z_L = R_L + jX_L$$


$$Z_L = R_L - jX_L$$

$$Z_L = R_s - jX_S$$

$$\boxed{Z_L = Z_S^*}$$

Case-4

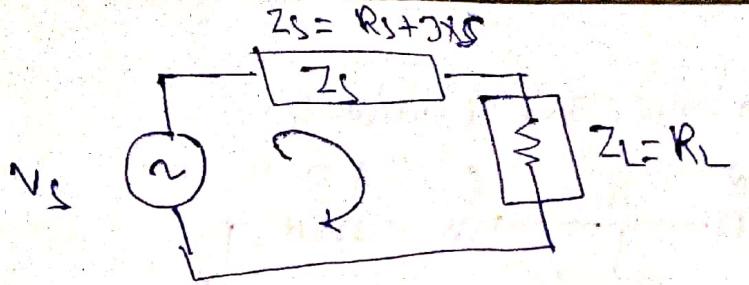When the load is only resistive. i.e. $Z_L = R_L$



When we know that - $I = \frac{V_s}{\sqrt{(R_s+R_L)^2 + (X_s+X_L)^2}}$

But given circuit is only R_L and $X_L \leq 0$

We get $I = \frac{V_s}{\sqrt{(R_s+R_L)^2 + X_s^2}}$

$$P = I^2 R_L = \frac{V_s^2 \times R_L}{(R_L+R_s)^2 + (X_s)^2}$$

Apply the same procedure —

$$\frac{dP_L}{dR_L} = 0$$

$$R_L = \sqrt{R_s^2 + X_s^2}$$


(Conclusion) ① only R_L is variable.
 $R_L = \text{[Remaining element]}$

② only X_L is variable

$$X_L = -(\text{Remaining Reactance})$$


Maximum Power Transfer Theorem in AC Circuits

For DC Network

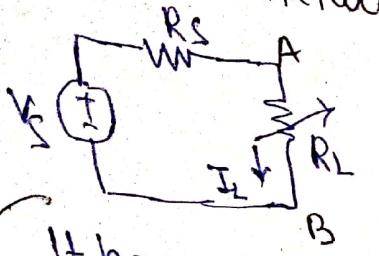

If has only resistive part

Convert into Thévenin's equivalent

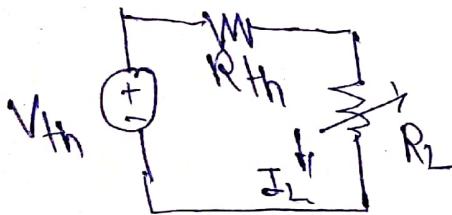

Condition for max^M Power Transferred-


$$(1) R_L = R_{th}$$

$$(2) P_{max} = \frac{V_{th}^2}{4R_{th}}$$

Note :- Max^M power transferred theorem is applicable when the load is variable.


Load	$\text{In DC} \rightarrow R_L$ $\text{In AC} \rightarrow Z_L = R_L + jX_L$
------	---

for AC Network

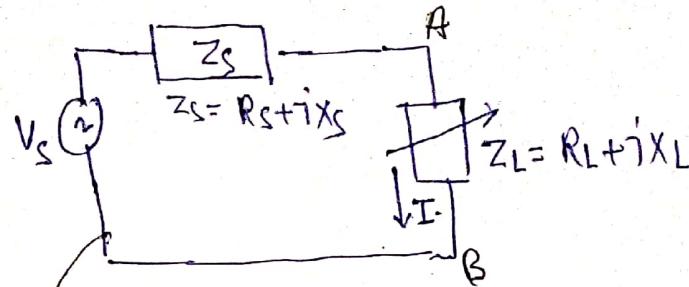

If has both resistive and reactive part

Convert into Thévenin's equivalent

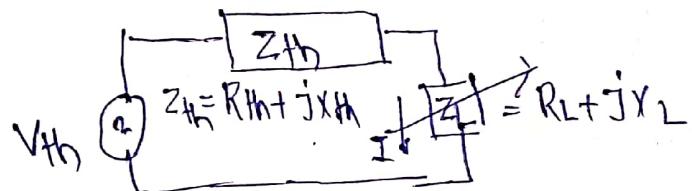

Condition for max^M power transferred
There are four cases

Case-1 R_L is variable and X_L is fixed

$$R_L = \sqrt{R_{th}^2 + (X_L + X_{th})^2}$$

Case-2 X_L is variable and R_L is fixed.

$$X_L = -X_{th}, \\ Z_L = R_L - jX_{th}$$


Case-3 Both R_L and X_L are variable

$$R_L = R_{th}, X_L = -X_{th} \\ Z_L = R_{th} - jX_{th} \\ Z_L = Z_{th}^*$$

Load is purely resistive ($X_L = 0$)


$$R_L = \sqrt{R_{th}^2 + X_{th}^2}$$

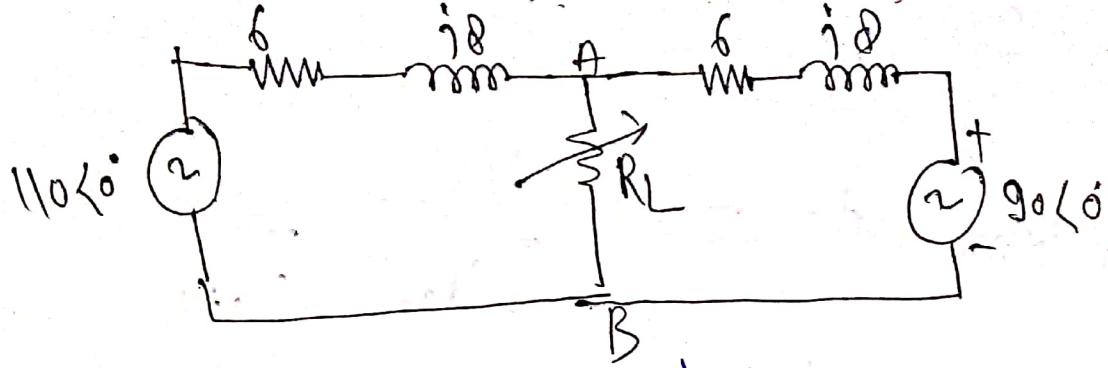Prob: find the maximum power across the load.




Soln

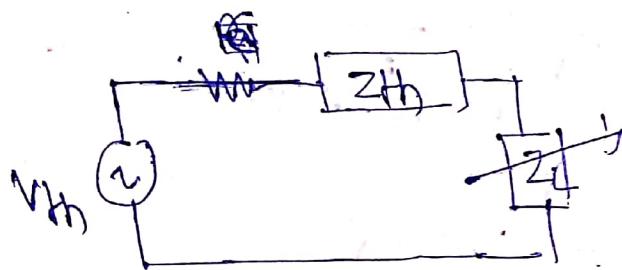First giving circuit into thevenin's equivalent circuit
then apply maxm power transfer theorem.



For V_{th} :

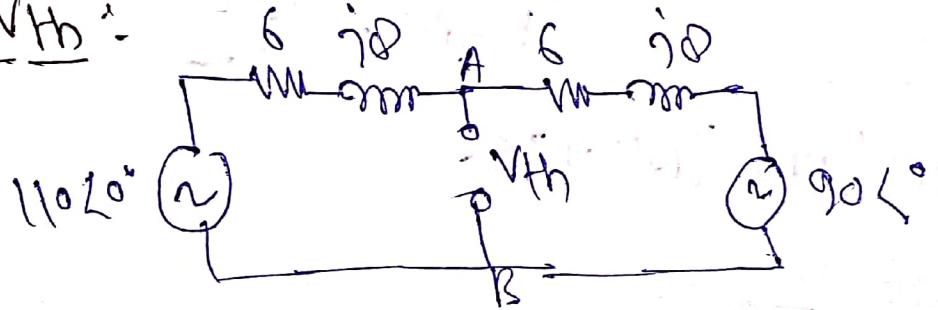

Apply nodal at A (KCL) —

$$\frac{V_{th} - 110\angle 0^\circ}{6+j8} + \frac{V_{th} - 90\angle 0^\circ}{6+j8} = 0$$

$$2V_{th} = 200$$

$$V_{th} = 100 \text{ volt}$$


for R_m :

Step-1 Remove load

Step-2 Voltage source \rightarrow S.C


Step-3 Current source \rightarrow O.C

Step-4 find R_{th} across open terminal

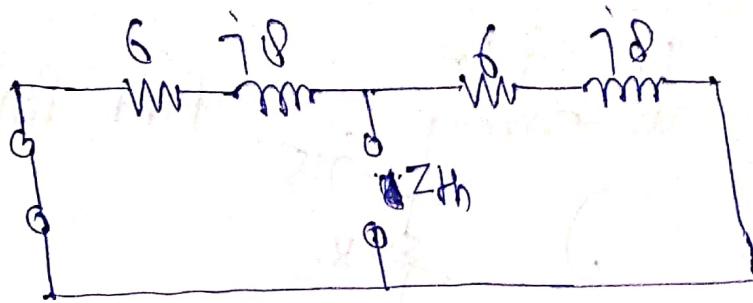

$$Z_{th} = \frac{(6+j8) \times (6+j8)}{2(6+j8)} = 3+j4$$

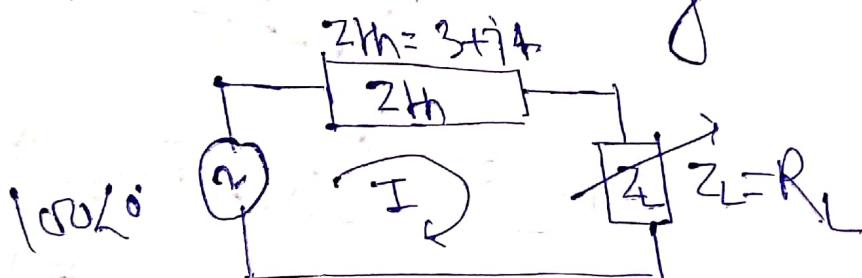Replace the entire circuit by V_{th} and Z_{th}



$$R_L = |\text{Remaining element}| = |3+j4| = 5$$


$$R_L = \Sigma v$$

$$I = \frac{100}{\sqrt{(8)^2+16}} = \frac{100}{\sqrt{64+16}} = \frac{100}{\sqrt{80}}$$

$$P = I^2 R_L = \frac{(100)^2}{80} \times 5 = \frac{(100)^2}{16} = \frac{10000}{16} = 625 \text{ watt}$$

$$P = 625 \text{ watt}$$

Prob:

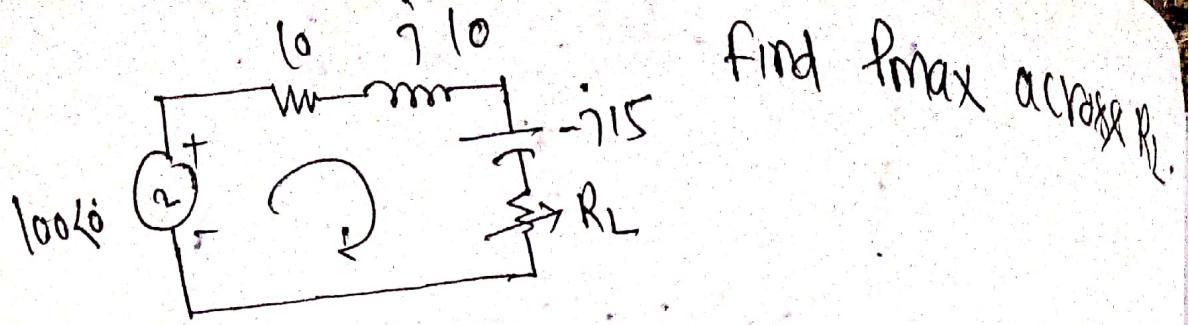

Sol:

$$R_L = \left| \begin{matrix} \text{Remaining} \\ \text{elements} \end{matrix} \right| = \left| \begin{matrix} 10 + j(10 - j15) \\ = |10 - j15| \end{matrix} \right|$$


$$R_L = \sqrt{100 + 25} = \sqrt{125} = 11.18$$

$$I = \frac{100∠0}{\sqrt{(10+R_L)^2 + (10-15)^2}}$$

$$P = I^2 \times R_L = I^2 \times 11.18 = 54.68 \text{ W}$$

Prob:

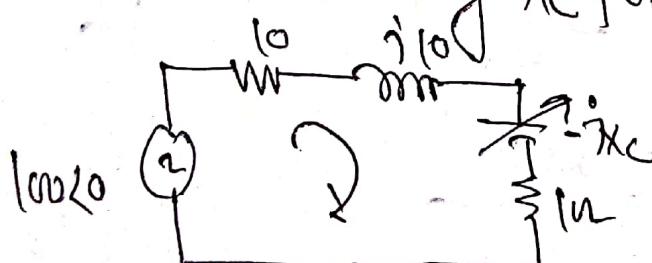Find the value of X_C for the max^M power load.



Sol:


When X_C is variable -

$$X_L = -X_S$$

$$\Rightarrow X_C = -j10$$

$$\left| X_C = 10 \text{ ohm} \right|$$

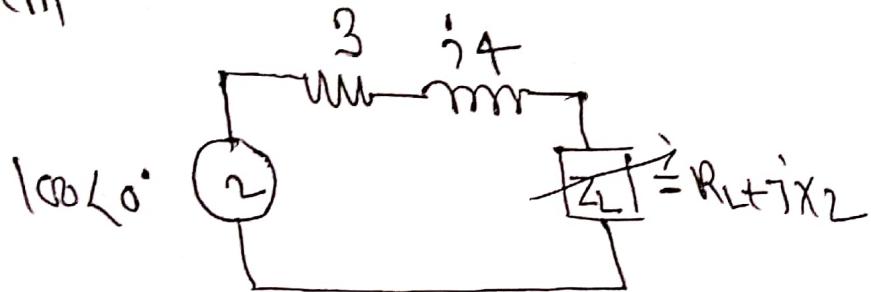Prob: Determine the value of Z_L in maximum power transfer theorem



Soln: When Z_L is variable or both R_L and X_L are variable

$$R_L = R_{Th}, \quad X_L = -X_{Th}$$

$$Z_L = R_L + jX_L$$

$$Z_L = R_{Th} - jX_{Th}$$

$$\boxed{Z_L = 2\angle -90^\circ}$$

$$\boxed{Z_L = 3 - j4}$$