

ELECTRICAL SCIENCE-II

(15B11EC211)


Content

- Example
- Single-Capacitor RC Circuit and Single-Inductor RL Circuit
- Initial and final value
- Comparison between **RC** and **RL** Circuits
- Complete Solution by the Differential Equation Approach


Example

- The circuit shown in Figure is at steady state before the switch closes at time $t = 0$. Determine the capacitor voltage $v(t)$ for $t > 0$.

Ans $v(t) = 2 + e^{-2.5t} \text{ V for } t > 0$

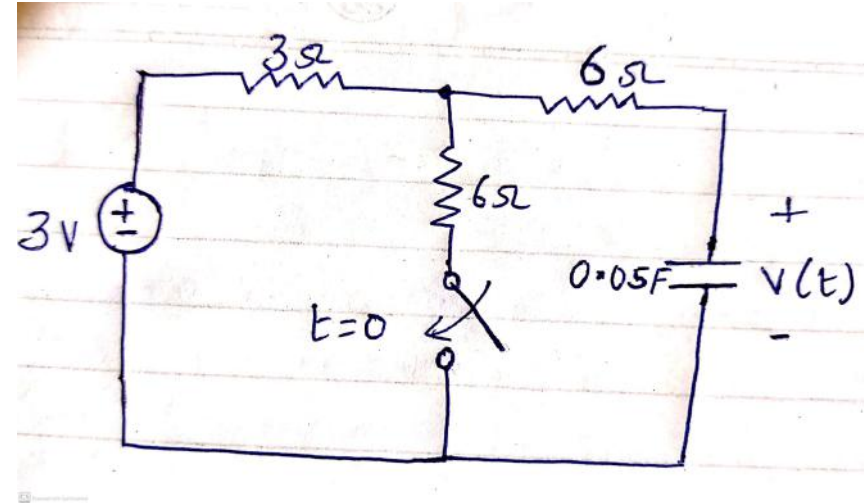

Example 3

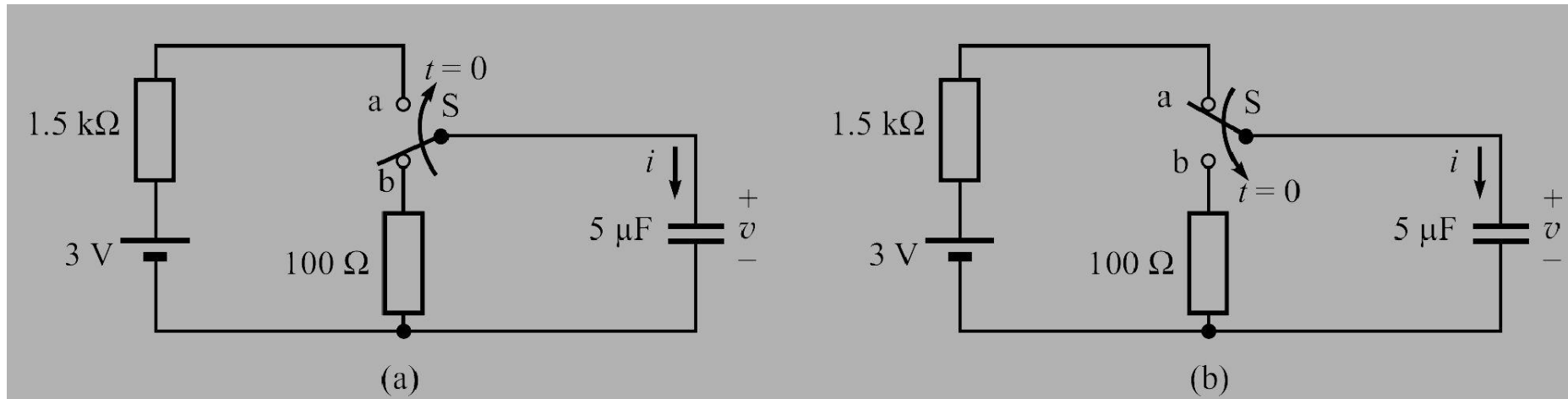

The single-pole double-throw switch S has been in position b for a long time so that the $5\text{-}\mu\text{F}$ capacitor is fully discharged. Now, at $t = 0$, the switch is thrown to position a . Determine

- (a) $v(0+)$,
- (b) $i(0+)$,
- (c) time constant τ ,
- (d) v and i at $t = 15\text{ ms}$.

Solution :

(a) Since the voltage across a capacitor cannot change instantaneously, we have $v(0+) = v(0-) = \mathbf{0\ V}$

$$(b) \quad i(0^+) = I_0 = \frac{V_0}{R} = \frac{3\ \text{V}}{1.5\ \text{k}\Omega} = \mathbf{2\ \text{mA}}$$

$$(c) \quad \tau = RC = (1.5\ \text{k}\Omega)(5\ \mu\text{F}) = \mathbf{7.5\ \text{ms}}$$

(d) At $t = 15\ \text{ms}$:

$$v = V_0(1 - e^{-t/\tau}) = 3(1 - e^{-(15\ \text{ms}) / (7.5\ \text{ms})}) = \mathbf{2.594\ \text{V}}$$

$$i = I_0 e^{-t/\tau} = (2\ \text{mA}) e^{-(15\ \text{ms}) / (7.5\ \text{ms})} = \mathbf{0.27\ \text{mA}}$$


Single-Capacitor RC Circuit and Single-Inductor RL Circuit


- The *time constant* for

- For LR circuit, $\tau = L / R_{Th}$

- For CR circuit, $\tau = CR_{Th}$

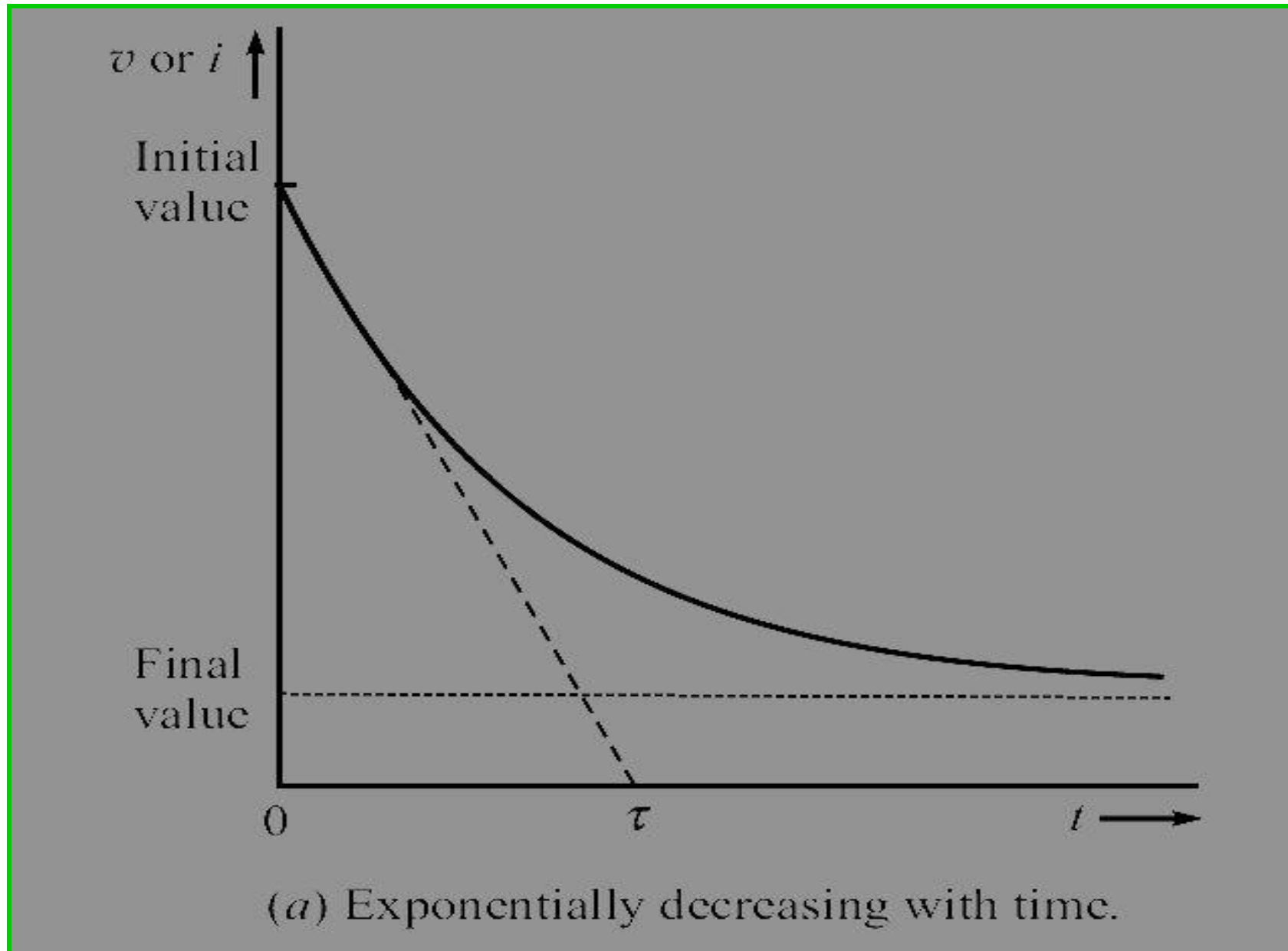Here, R_{Th} is Thevenin resistance as “seen” by the capacitor or inductor.



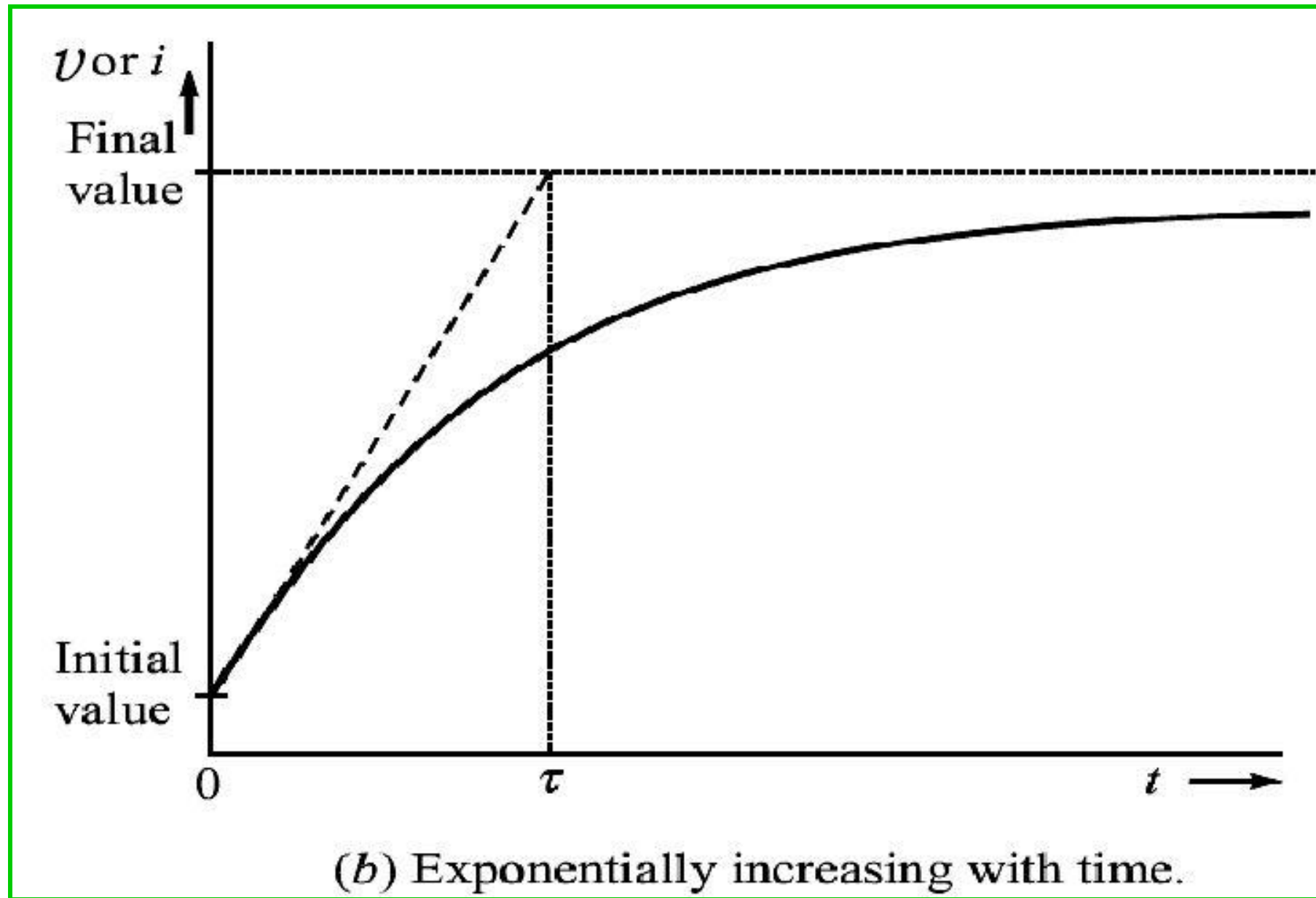

- The voltages and currents approach their final values asymptotically.
- It means that they never actually reach them.
- However, after *five time-constants* they change by 99.3 % of their total change.

Important Point

(For solving Problems)

If immediately after switching,

$v(0+)$ and $i(0+)$ are *initial values*

and $v(\infty)$ and $i(\infty)$ are *final values*.

Then, the expressions for all the voltages and currents in the circuit for any time t are given as

$$\begin{aligned} v(t) &= v(\infty) + [v(0^+) - v(\infty)]e^{-t/\tau} \text{ V} \\ i(t) &= i(\infty) + [i(0^+) - i(\infty)]e^{-t/\tau} \text{ A} \end{aligned}$$

Comparison between *RC* and *RL* Circuits

Though both give similar response, but we prefer *RC* over *RL* circuit, because

- Inductors are not as nearly ideal as capacitors.
- Inductors are relatively bulky, heavy and difficult to fabricate, especially using integrated-circuit techniques.
- Inductors are relatively costlier.
- The magnetic field emanating from the inductors can induce unwanted voltages in other components.

Complete Solution by the Differential Equation Approach

5 major steps to find the complete solution:

- Determine initial conditions on capacitor voltages and/or inductor currents.
- Find the differential equation for either capacitor voltage or inductor current (mesh/loop/nodal analysis).
- Determine the natural solution (complementary solution).
- Determine the forced solution (particular solution).
- Apply initial conditions to the complete solution to determine the unknown coefficients in the natural solution.

Here we will consider three cases for the input to the circuit.

- First case

$$v_s(t) = V_0$$

- Second case

$$v_s(t) = V_0 e^{-t/\tau}$$

- Third case

$$v_s(t) = V_0 \cos(\omega t + \theta)$$

These three cases are special because the forced response will have the same form as the input.