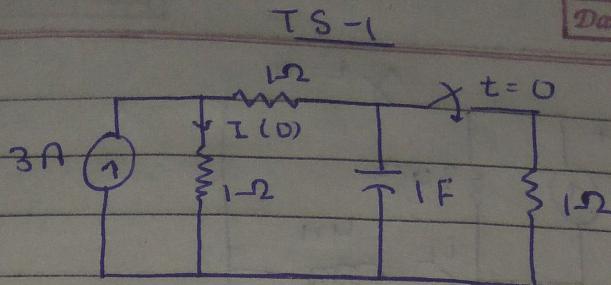


18/11/18


Page No.

Date:

(i)

find  $I$  for  $t=0$ .


Ans

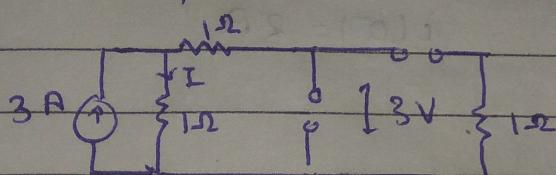 $t=0$ ,

$$V = 1R$$

$$= 3 \times 1$$

$$= 3V$$

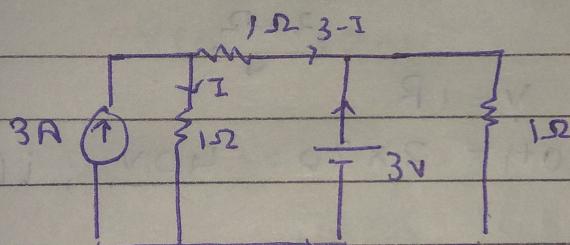

$$I(I) + I(3-I) = 3$$

$$I + 3 - I = 3$$

$$I - (3-I) = 3$$



$$I - 3 + I = 3$$

$$2I = 6$$

$$\underline{I = 3}$$


Cap remains in steady state

$$0 = (a)v$$

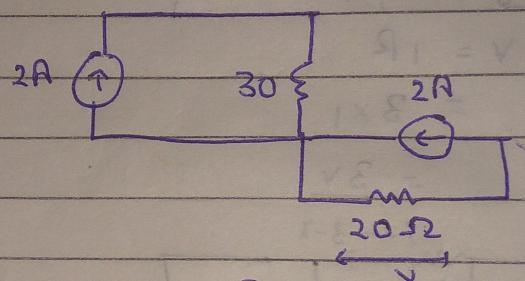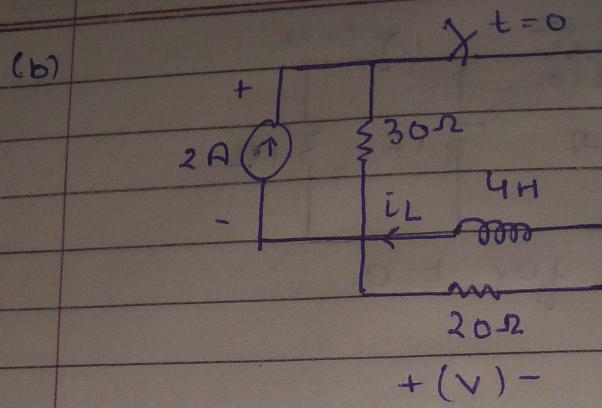

$$V(0^+) = 2 \times 20 = 40V ; i(0^+) = 2A$$

(3)

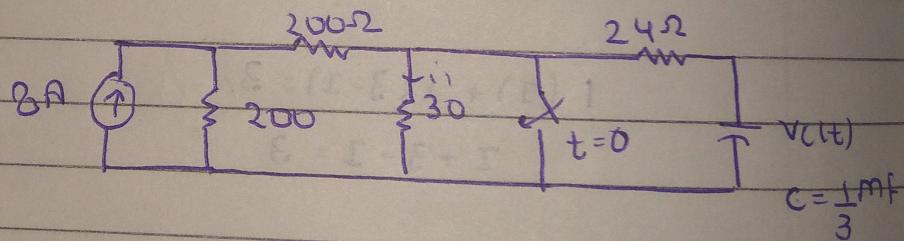

$$Vc(t) = V(\infty) + [V(0) - V(\infty)] e^{-\frac{t}{T}}$$

$$I_1 = \frac{200 \times 8}{200 + 50} = 6.4A$$

$$\begin{aligned} V(0) &= 6.4 \times 30 \\ &= 192 \\ V(\infty) &= 0 \end{aligned}$$

$$R_{Th} = RC$$

$$= 24 \times \frac{1}{3} \times 10^{-3}$$


$$= 8 \times 10^{-3}$$

$$- \frac{6 \times 10^3}{t}$$

$$V_C(t) = 192 e^{-\frac{t}{8}}$$

$$= 192 e^{-\frac{125t}{8}}$$


(4)

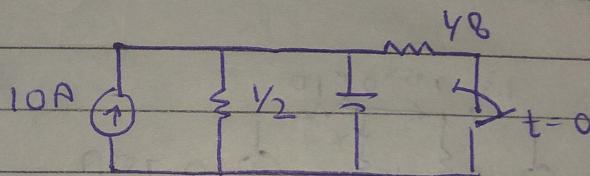

$$V(0) = 10 \times \frac{1}{2} = 5V$$

$$R_{Th} = \frac{1}{10}$$

$$V(\infty) =$$

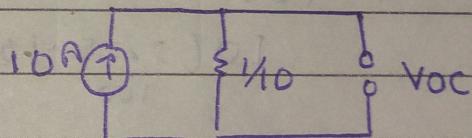

$$V(\infty) = V_{OC} = 10 \times \frac{1}{10} = 1V$$


$$V_L(t) = V(\infty) + [V(0) - V(\infty)] e^{-\frac{t}{T}}$$

$$= 1 + 4e^{-\frac{t}{10}}$$

$$= (1 + 4e^{-\frac{-10 \cdot 0.01}{10}}) V$$

$$= 2.55 V$$


(5)

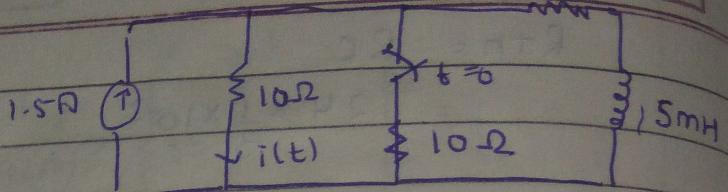

$$i(t) = -$$

$$\begin{aligned} V &= 1.5 \times 10 \\ &= 15V \end{aligned}$$

$$i_L(0^-) = 0.75A$$

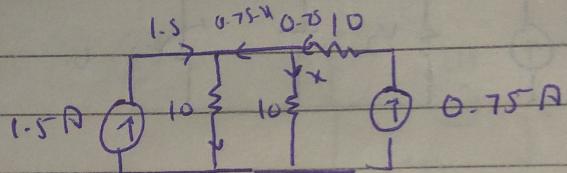

$$10(1.5 + 0.75 - x) = 10x$$

$$10\left(\frac{2.25}{100} - x\right) = 10x$$

$$\begin{array}{r} 1.5 \\ 0.75 \\ \hline 2.25 \end{array}$$

$$\begin{array}{r} 1+1 \\ 20 \quad 10 \\ \hline 1+2 \\ 20 \end{array}$$

$$\frac{20}{3}$$

$$22.5 - 10x = 10x$$

$$20x = 22.5$$

$$\begin{array}{r} 6.500 \\ 0.375 \\ \hline 0 \end{array}$$

$$\frac{2000}{a}$$

$$i = 1.5 + 0.75 - x$$

$$= \frac{2.25}{100} - \frac{22.5}{200}$$

$$= 22.5 \left[ \frac{100}{200} \right]$$

$$= \frac{22.5}{2} = 112.5$$

1.5mH

$$1.5 = 2 i(0) + 0.75$$

$$i(0) = 0.375 \text{ A}$$

$$i(\infty) = 0.5 \quad \left( \frac{1.5}{3} \right)$$

$$\begin{aligned} \therefore i(t) &= I(0) + [I(\infty) - I(0)] e^{-\frac{L}{Rt}} \\ &= 0.5 + [0.375 - 0.5] e^{-\frac{t}{\tau}} \end{aligned}$$

$$R_{th} = \frac{10}{3}$$

$$R_{th} = \underline{15}$$

$$\frac{L}{R} = \frac{15 \times 3}{10} = \frac{3 \times 10^{-3}}{3}$$

$$\begin{aligned} \frac{1+1}{20+10} &= \frac{3 \times 10^{-3}}{10} = \frac{9}{2} \\ \frac{1+2}{20} &= \frac{10}{20} = 1 \end{aligned}$$


$$\frac{20}{3} \quad i(t) = 0.5 - 0.125e$$

$$\frac{6.500}{0.375} \quad \frac{L}{R} = \frac{15 \text{ mH}}{15} = 1 \text{ mH} = 10^{-3} \text{ H}$$


$$\frac{2000}{9} \quad i(t) = 0.5 - 0.125e^{-\frac{1000t}{9}}$$

$$6218 = 9 \times 10^{-3} = \frac{V}{9} = 1$$

(6)

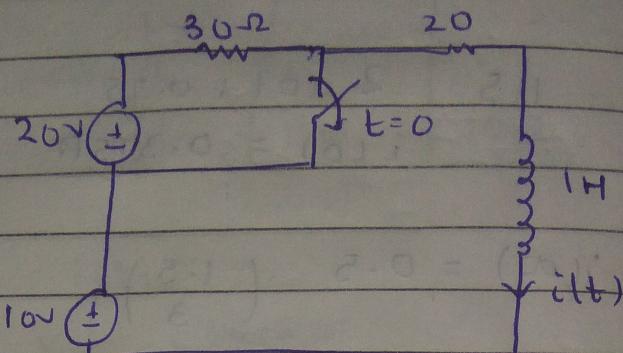


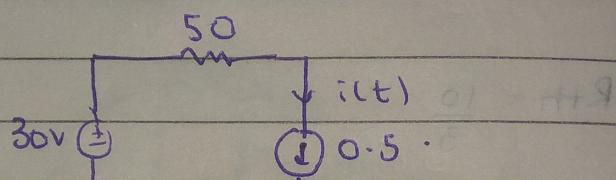
$$I = \frac{V}{R} = \frac{10}{20} = 0.5 \text{ A}$$



$$i(\infty) = \frac{30}{50} = 0.6 \text{ A}$$

$$i(t) = 0.6 + [0.5 - 0.6]e^{-50t}$$

(7)

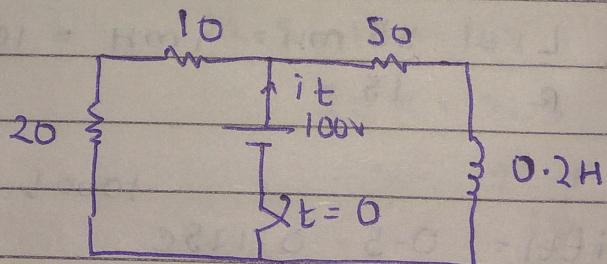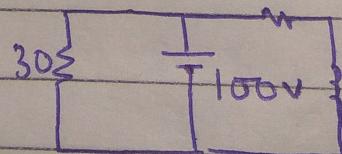Ans

$$R = \frac{1}{30} + \frac{1}{50} = \frac{150}{8}$$

$$I = \frac{V}{R} = \frac{2 \times 100 \times 8}{3150} = \frac{16}{3} \text{ A}$$

$$v(\infty) = 0 \text{ V}$$


$$i(0) = \frac{16 \times 30}{3 \times 80} 10 \\ = 2 \text{ A}$$

$$i(t) = 0 + (2-0) e^{-\frac{t}{\tau}} \\ = 2 e^{-400t}$$


$$R_{th} = 50 + 30 = 80$$

$$0.5 \times 2 = 2 e^{-400t}$$


$$t = 1.73 \text{ ms}$$

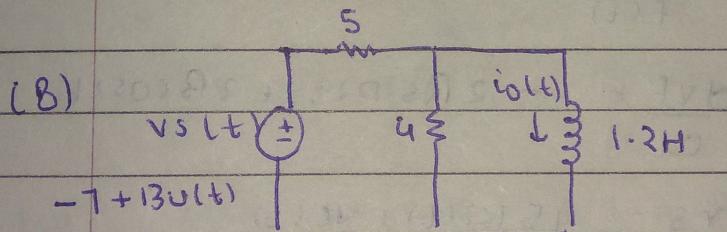

$$t = 0,$$

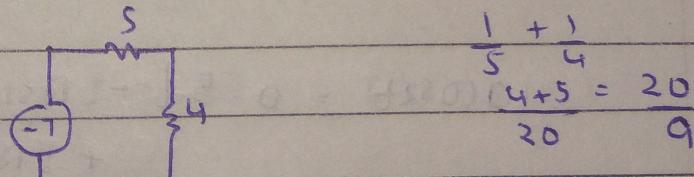
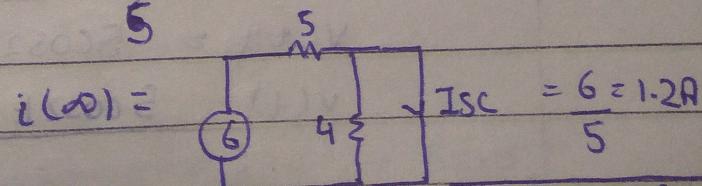
$$i(0^-) = \frac{-7}{5} = -1.4 \text{ A}$$




$$i(t) = 1.2 + (-1.4 - 1.2) e^{-1.85t} = 1.2 - 2.6 e^{-1.85t}$$


112/18

(i)

(a)

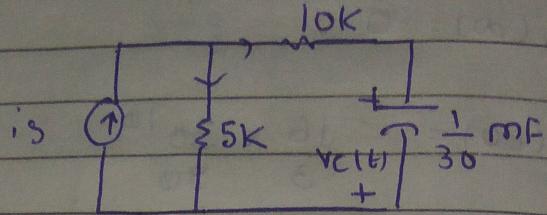

Ans

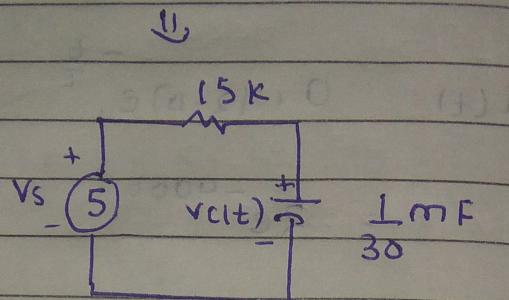

$$v_c(t) = D e^{-2t}$$

$$v_c(0) = 0 \Rightarrow 0 = D e^0 + 5 \Rightarrow D = -5$$

$$\frac{2 \cos 2t}{f(t)}, \quad v_f = A \cos 2t + B \sin 2t$$

$$\frac{dv_f}{dt} = -2A \sin 2t + 2B \cos 2t$$

$$\begin{aligned} v_s &= 15k i_s(t) + v_c(t) \\ &= 15 \times 1 \times C \frac{dv_c(t)}{dt} + v_c(t) \end{aligned}$$

$$10 \cos 2t = 0.5 [-2A \sin 2t + 2B \cos 2t] + [A \cos 2t + B \sin 2t]$$

$$A + B = 10, \quad 0 = -A + B$$

$$A = 5, B = 5$$

$$v_c(t) = 5 \cos 2t + 5 \sin 2t + D e^{-2t}$$

$$v_c(t) = 5 \cos 2t + 5 \sin 2t - 5 e^{-2t}$$

(ii)

(iii)