

Name: _____

Jaypee Institute of Information Technology, Noida
T1 Examination, 2020
B.Tech. 2nd semester

Course Name: Electrical Science-1
Course Code: 15B11EC111

Max Time: 1 Hr
Max Marks: 20

After pursuing this course, the students will be able to:

- CO1 Recall the concepts of voltage, current, power and energy for different circuit elements. Apply the kirchhoff's laws and different analyzing techniques to identify the different circuit parameters.
- CO2 Define and apply the networks theorems in the complex AC and DC circuits, networks. Demonstrate the physical model for given sinusoidal AC signal and construct the phasor diagrams.
- CO3 Demonstrate the concepts of resonance and operate different instrumental and measurement equipments.
- CO4 Demonstrate the construction and working of single phase transformer.

Note: Attempt all the questions.

Q.1 For the circuit as shown in Fig. 1, $i_0 = 3A$. Calculate i_x and the total power absorbed by the entire circuit. [4, CO1]

Q.2 If $R_{eq} = 50 \Omega$ in the circuit as shown in Fig. 2, Find the value of R. [3, CO1]

Q.3 Determine the value of the voltage that is measured by the voltmeter as illustrated in Fig. 3. [4, CO1]

Q.4 Find the currents i_1 , i_2 and i_3 in the circuit as given in Fig. 4. [5, CO1]

Q.5 Use superposition theorem to find the v_x in the circuit as demonstrated in Fig. 5. [4, CO2]

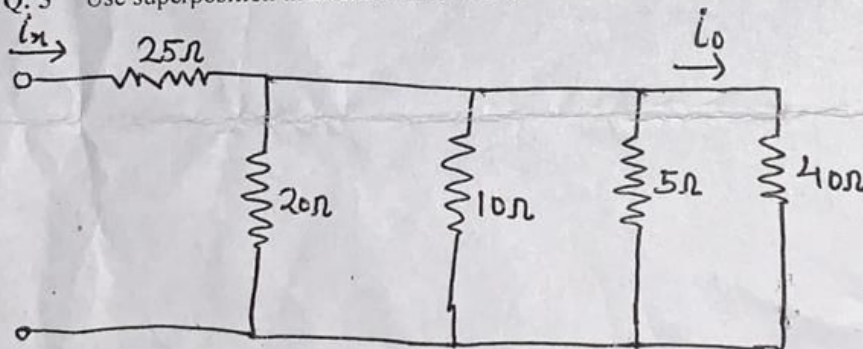


Fig. 1.

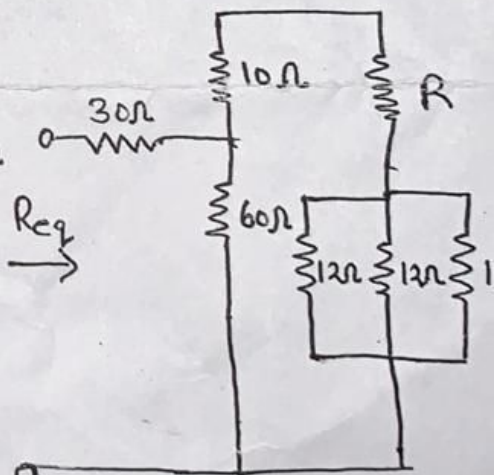


Fig. 2

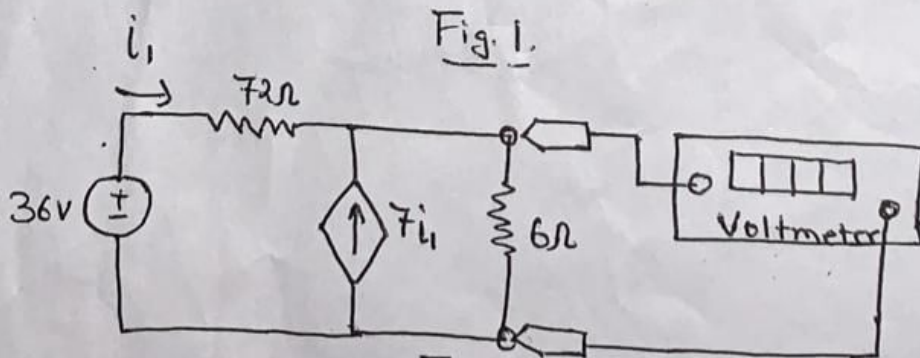


Fig. 3.

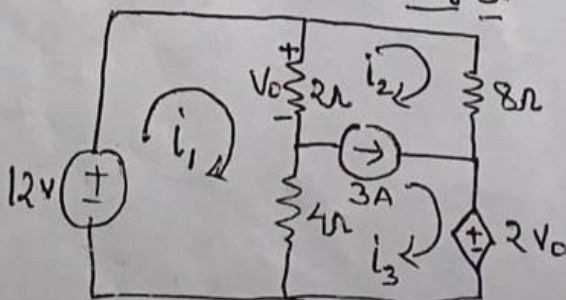


Fig. 4

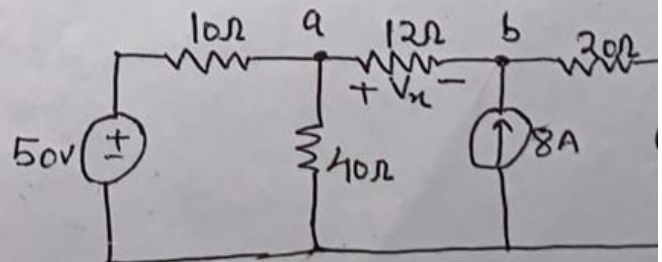


Fig. 5