

# VIRTUAL LAB EXPERIMENT-1

**AIM:-**To verify the voltage divider rule (VDR) and the current divider rule (CDR).

**RESULT:-**

**VERIFICATION OF VOLTAGE DIVIDER RULE:**

**1.**


## Voltage Divider Calculator

A voltage divider circuit is a very common circuit that takes a higher voltage and converts it to a lower one by using a pair of resistors. The formula for calculating the output voltage is based on Ohms Law and is shown below.

$$V_{out} = \frac{V_s \times R_2}{(R_1 + R_2)}$$

where:

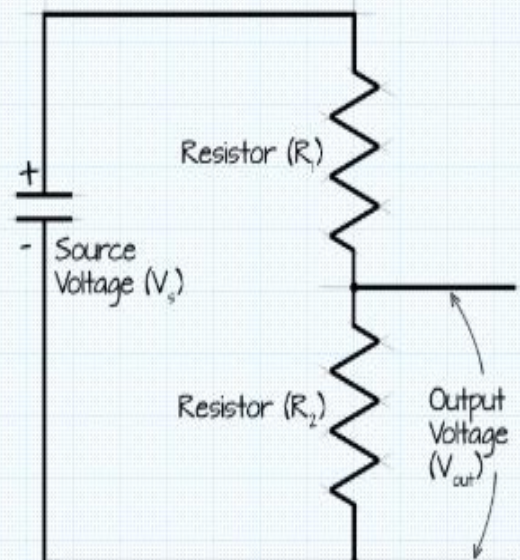- $V_s$  is the source voltage, measured in volts (V),
- $R_1$  is the resistance of the 1st resistor, measured in Ohms ( $\Omega$ ).
- $R_2$  is the resistance of the 2nd resistor, measured in Ohms ( $\Omega$ ).
- $V_{out}$  is the output voltage, measured in volts (V),



Enter any three known values and press 'Calculate' to solve for the other.

Voltage Source ( $V_s$ )

Volts (V)

Resistance 1 ( $R_1$ )

kilohms ( $k\Omega$ ) ▼

Resistance 2 ( $R_2$ )

kilohms ( $k\Omega$ ) ▼

Output Voltage ( $V_{out}$ )

Volts (V)

2.


## Voltage Divider Calculator

A voltage divider circuit is a very common circuit that takes a higher voltage and converts it to a lower one by using a pair of resistors. The formula for calculating the output voltage is based on Ohms Law and is shown below.

$$V_{out} = \frac{V_s \times R_2}{(R_1 + R_2)}$$

where:

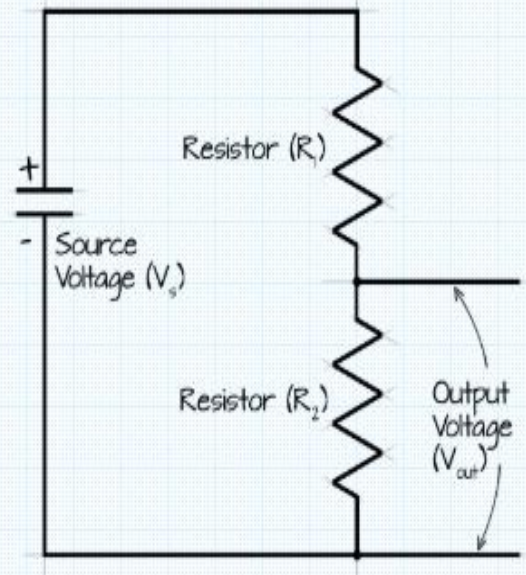- $V_s$  is the source voltage, measured in volts (V).
- $R_1$  is the resistance of the 1st resistor, measured in Ohms ( $\Omega$ ).
- $R_2$  is the resistance of the 2nd resistor, measured in Ohms ( $\Omega$ ).
- $V_{out}$  is the output voltage, measured in volts (V).



Enter any three known values and press "Calculate" to solve for the other.

Voltage Source ( $V_s$ )	<input type="text" value="5"/>	Volts (V)
Resistance 1 ( $R_1$ )	<input type="text" value="20"/>	kilohms ( $k\Omega$ ) ▼
Resistance 2 ( $R_2$ )	<input type="text" value="10"/>	kilohms ( $k\Omega$ ) ▼
Output Voltage ( $V_{out}$ )	<input type="text" value="1.667"/>	Volts (V)



3.


## Voltage Divider Calculator

A voltage divider circuit is a very common circuit that takes a higher voltage and converts it to a lower one by using a pair of resistors. The formula for calculating the output voltage is based on Ohms Law and is shown below.

$$V_{out} = \frac{V_s \times R_2}{(R_1 + R_2)}$$

where:

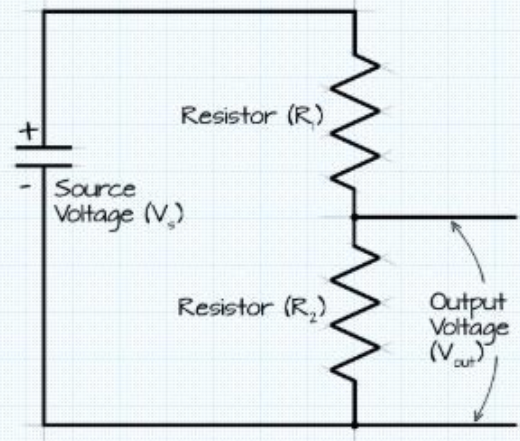- $V_s$  is the source voltage, measured in volts (V).
- $R_1$  is the resistance of the 1st resistor, measured in Ohms ( $\Omega$ ).
- $R_2$  is the resistance of the 2nd resistor, measured in Ohms ( $\Omega$ ).
- $V_{out}$  is the output voltage, measured in volts (V).



Enter any three known values and press "Calculate" to solve for the other.

Voltage Source ( $V_s$ )	<input type="text" value="5"/>	Volts (V)
Resistance 1 ( $R_1$ )	<input type="text" value="5"/>	kilohms (k $\Omega$ ) ▼
Resistance 2 ( $R_2$ )	<input type="text" value="30"/>	kilohms (k $\Omega$ ) ▼
Output Voltage ( $V_{out}$ )	<input type="text" value="4.286"/>	Volts (V)

## VERIFICATION OF CURRENT DIVIDER RULE:

1.



### Current Divider Calculator

This tool calculates the current flow through each of up to 10 parallel-connected resistances connected to a current source.

Current Source

A ▼

R1

k $\Omega$  ▼

= 2.32558

A ▼

R2

k $\Omega$  ▼

= 7.67442

A ▼

Add Resistor

Remove Resistor

FORMULA

$$I_n = I_s \frac{R_{total}}{R_n}$$

$R_{total}$  = The total equivalent parallel resistance of the resistor array across the current source.

2.



### Current Divider Calculator

This tool calculates the current flow through each of up to 10 parallel-connected resistances connected to a current source.

Current Source

10

A

R1

33

kΩ

= 1.68067

A

R2

10

kΩ

= 5.54622

A

R3

20

kΩ

= 2.77311

A

Add Resistor

Remove Resistor

FORMULA

$$I_n = I_s \frac{R_{total}}{R_n}$$

$R_{total}$  = The total equivalent parallel resistance of the resistor array across the current source.

3.



### Current Divider Calculator

This tool calculates the current flow through each of up to 10 parallel-connected resistances connected to a current source.

Current Source

10

A

R1

4.7

kΩ

= 5.15464

A

R2

5

kΩ

= 4.84536

A

Add Resistor

Remove Resistor

FORMULA

$$I_n = I_s \frac{R_{total}}{R_n}$$

$R_{total}$  = The total equivalent parallel resistance of the resistor array across the current source.