

Resonant Circuits


Contents:

- (1) Series and parallel resonance
- (2) Frequency response of series and parallel resonance
- (3) Quality factor of series and parallel circuit
- (4) Band width
- (5) Problem related to series and parallel circuit

Resonance:

- It means that interchange the energy in one form to another.
- Resonance describes the energy transformation between inductor (L) and capacitor (C).
- For occurrence of resonance in any system, two energy elements are required to store the energy in the form of electric field and magnetic field.

Example

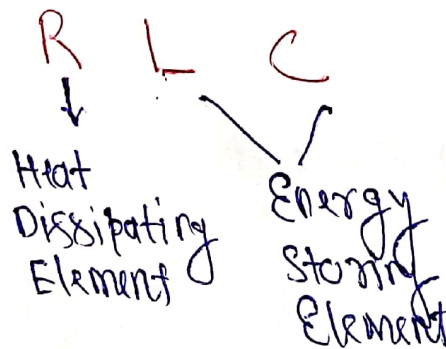

- The circuit is said to be resonance when source current and source voltage are in same phase. Which means the imaginary component of impedance is zero. The circuit behaves like a pure resistive network.

Example





$$Z = R + jX$$

↓ ↓
Real Imaginary
Part Part } → 0


Condition for resonance in series and parallel circuit

- ① R, L and C. should be present.
- ② $X_L = X_C$
- ③ $\phi = 0 \rightarrow$ in same phase
- ④ Pure resistive network
- ⑤ power factor unity
- ⑥ Two storing element like L and C
- ⑦ Applicable Only in AC circuit.

Types of Resonance

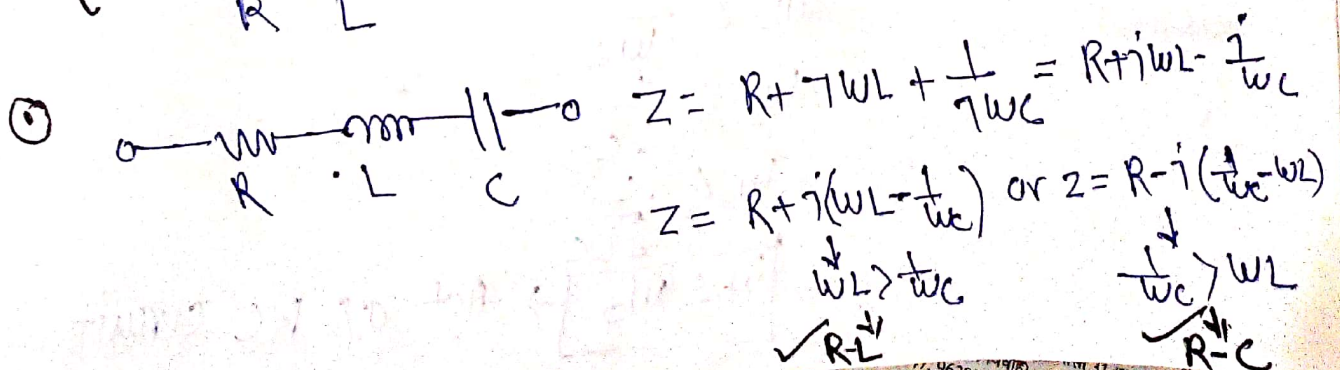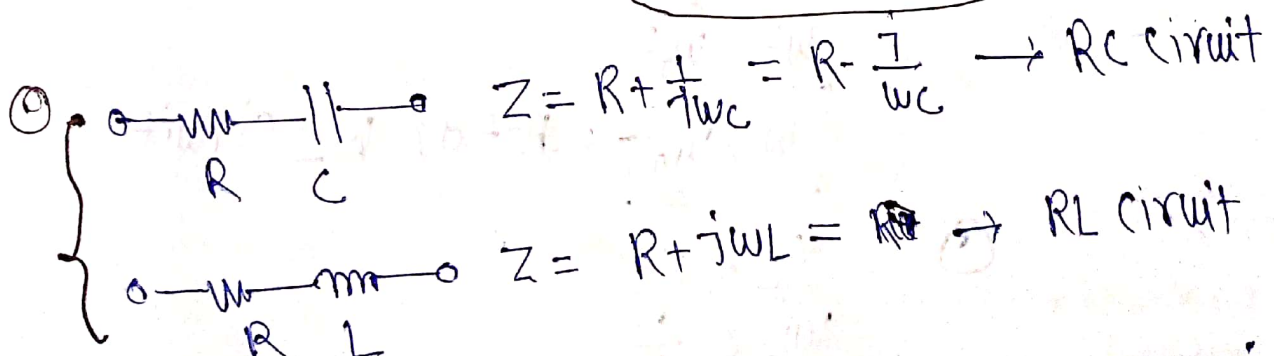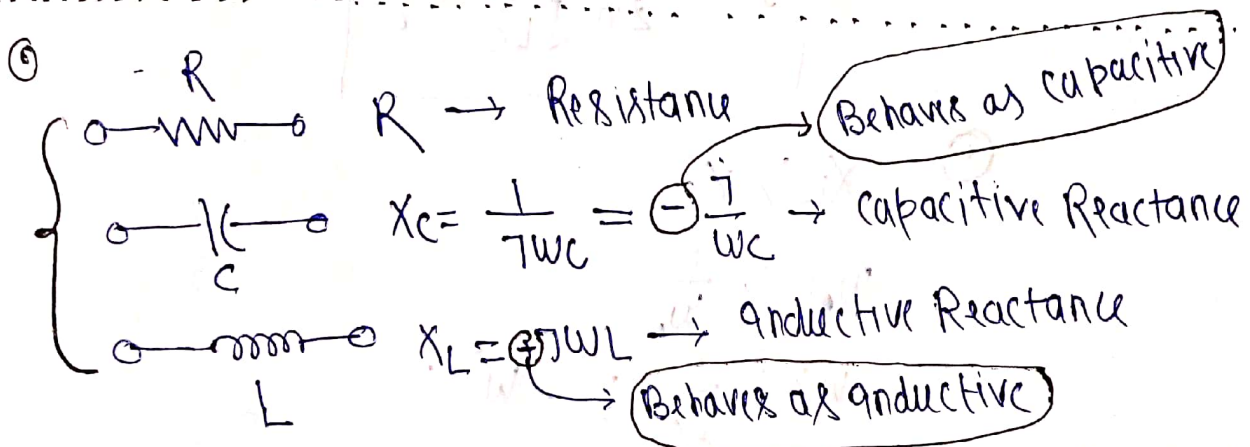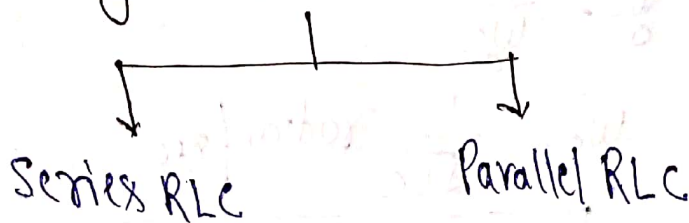

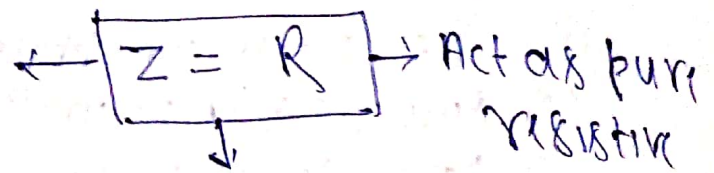$\text{---} \underset{R}{\text{---}} \underset{L}{\text{---}} \text{---} \underset{C}{\text{---}} \text{---}$ $Z = R + j(\omega L - \frac{1}{\omega C})$
 if $\omega L = \frac{1}{\omega C}$



This condition is called Resonant.

Therefore, (i) $X_L = X_C$ at resonant
 $\omega L = \frac{1}{\omega C}$
 $\omega_0 = \frac{1}{\sqrt{LC}}$ radian/sec

$f_0 = \frac{1}{2\pi \sqrt{LC}}$ Hz

(ii)

$X_L > X_C$

$\omega L > \frac{1}{\omega C}$

$\omega^2 > \frac{1}{LC}$; $\omega^2 > \omega_0^2$

$\omega^2 > \omega_0^2$

$\boxed{\omega > \omega_0} \rightarrow$ Act as RL circuit

(iii)

$X_L < X_C$


$\omega L < \frac{1}{\omega C}$

$\omega^2 < \frac{1}{LC}$


$\omega < \frac{1}{\sqrt{LC}}$

$\boxed{\omega < \omega_0} \rightarrow$ Act as RC circuit

Conclusion:-

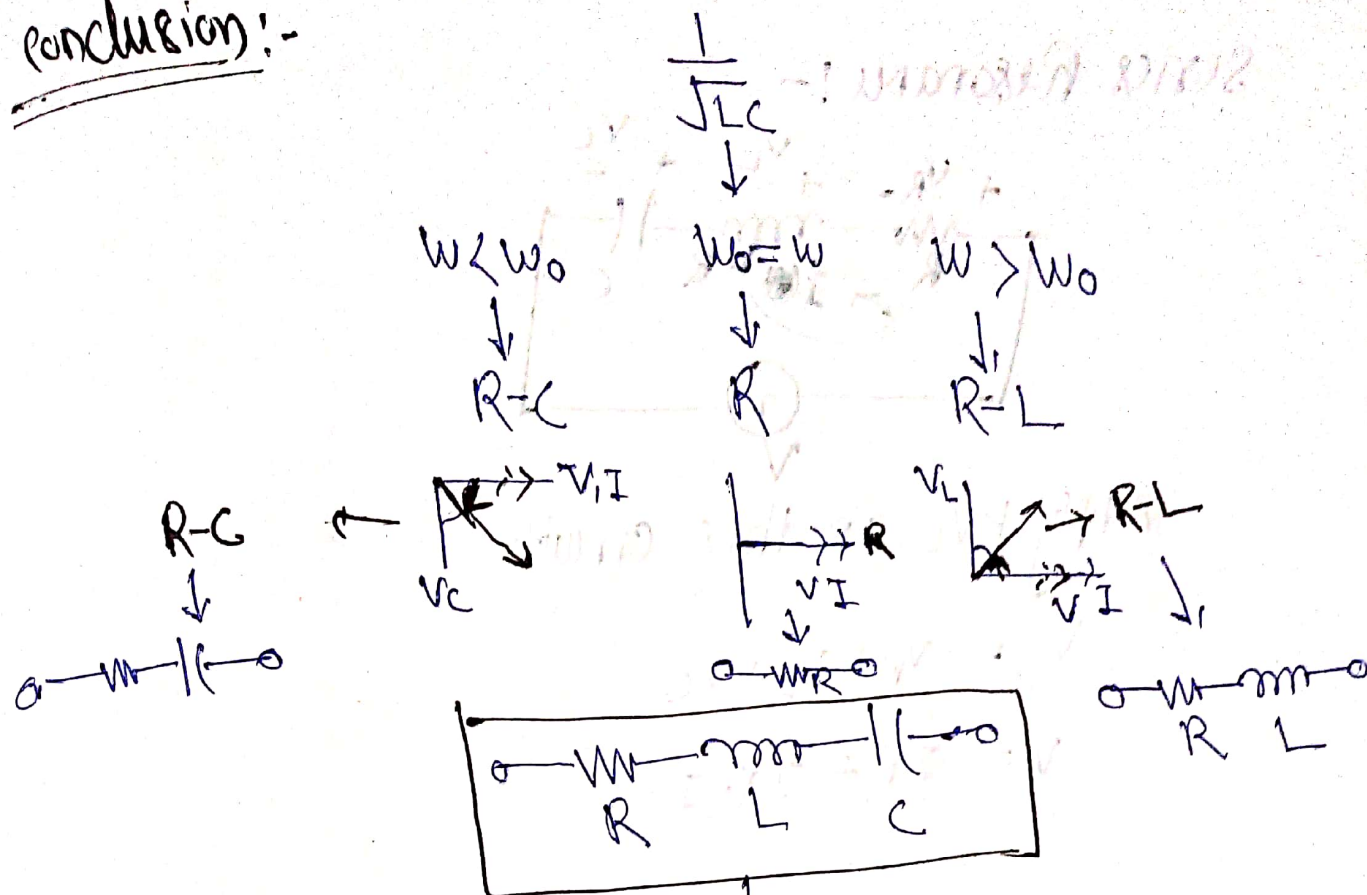

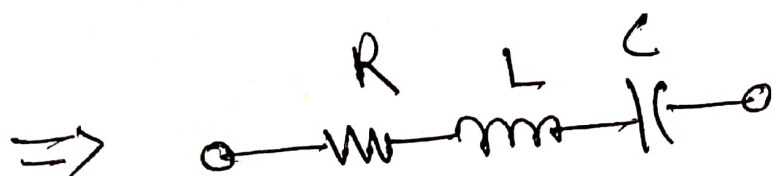
It behaves like either → R
 → R-L
 → R-C
 But not → RLC



$$V_R = IR$$

$$V = j\omega L I$$

$$V = -\frac{j}{\omega C} I$$


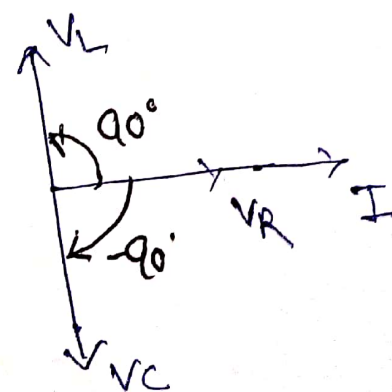


→ voltage and current in same phase → Resonance Condition

→ voltage lead by 90°

→ voltage lag by 90°

Series RLC Resonance circuit:

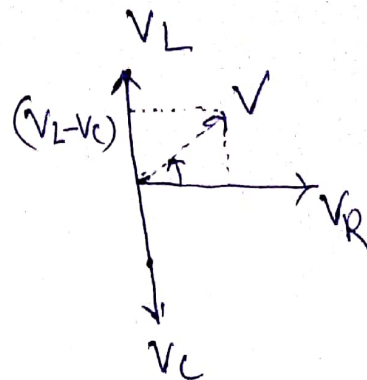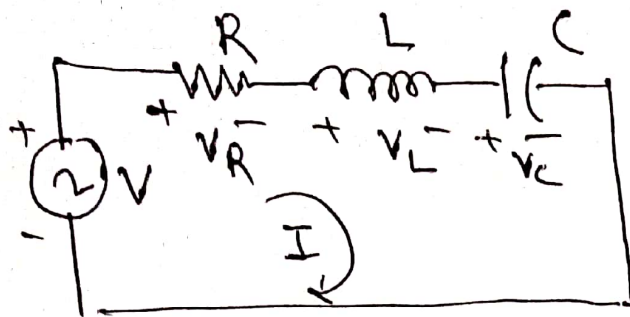

Apply KVL of given circuit

$$V = V_R + j(V_L - V_C)$$

$$V = IR + j(IX_L - IX_C)$$

$$\frac{V}{I} = R + j(X_L - X_C)$$






$$Z = R + j(\omega L - \frac{1}{\omega C})$$

$$|Z| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

At resonance frequency $\rightarrow \omega_0$

$$\omega_0 L = \frac{1}{\omega_0 C}$$
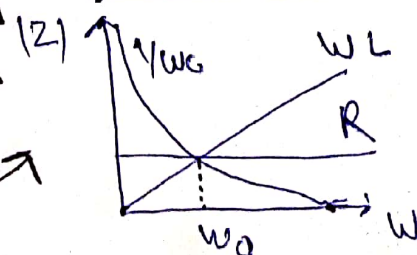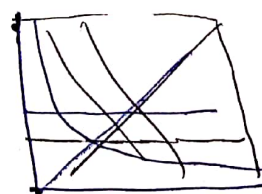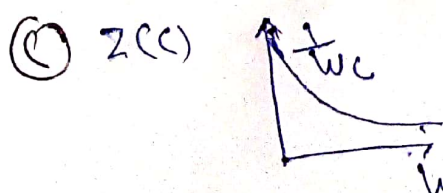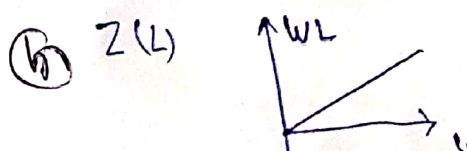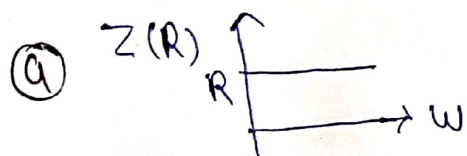
$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$



Combine of
(a), (b) and (c)

