


ELECTRICAL SCIENCE-II

(15B11EC211)

Content

- RL Circuit
- Time Constant
- Example

The Simple RL Circuit

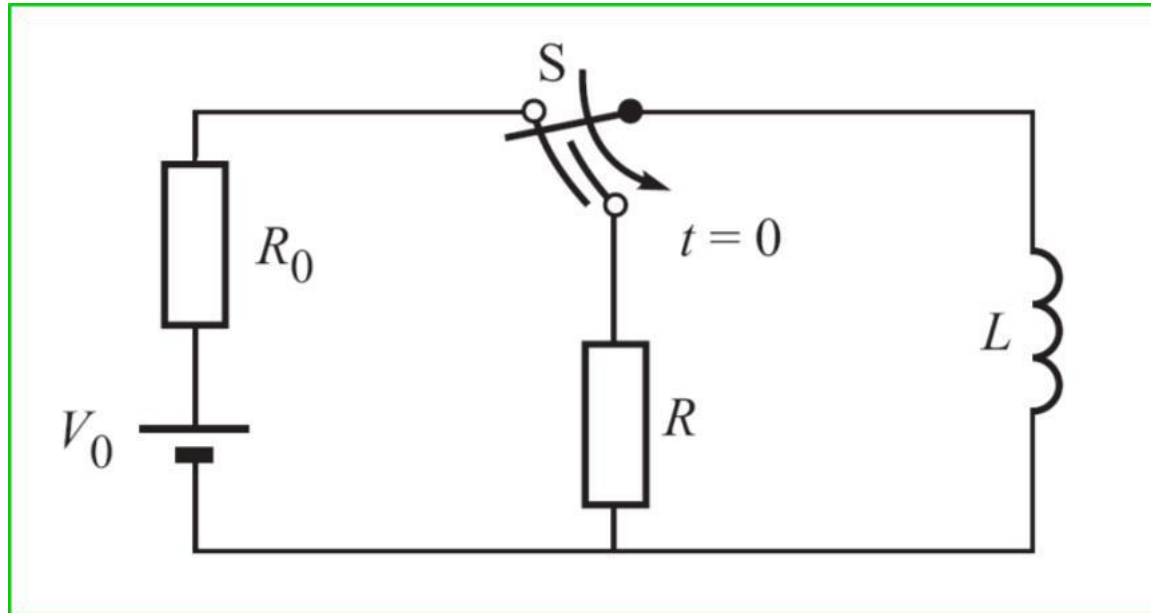

At $t = 0^-$, a steady current that has been flowing in the circuit,

$$I_0 = \frac{V}{R_0}$$

For $t > 0+$, applying KVL,


$$v_R + v_L = 0 \quad \text{or} \quad Ri + L \frac{di}{dt} = 0 \quad \text{or} \quad \frac{di}{dt} + \frac{R}{L}i = 0$$

Re-writing the equation to separate variables and then integrating,

$$\frac{di}{i} = -\frac{R}{L}dt$$
$$\int_{I_0}^{i(t)} \frac{1}{i} di = \int_0^t \left(-\frac{R}{L}\right) dt \quad \text{or} \quad \ln i \Big|_{I_0}^i = -\frac{R}{L}t \Big|_0^t$$

$$\text{or} \quad \ln i - \ln I_0 = -\frac{R}{L}(t - 0)$$

or $i(t) = I_0 e^{-Rt/L}$

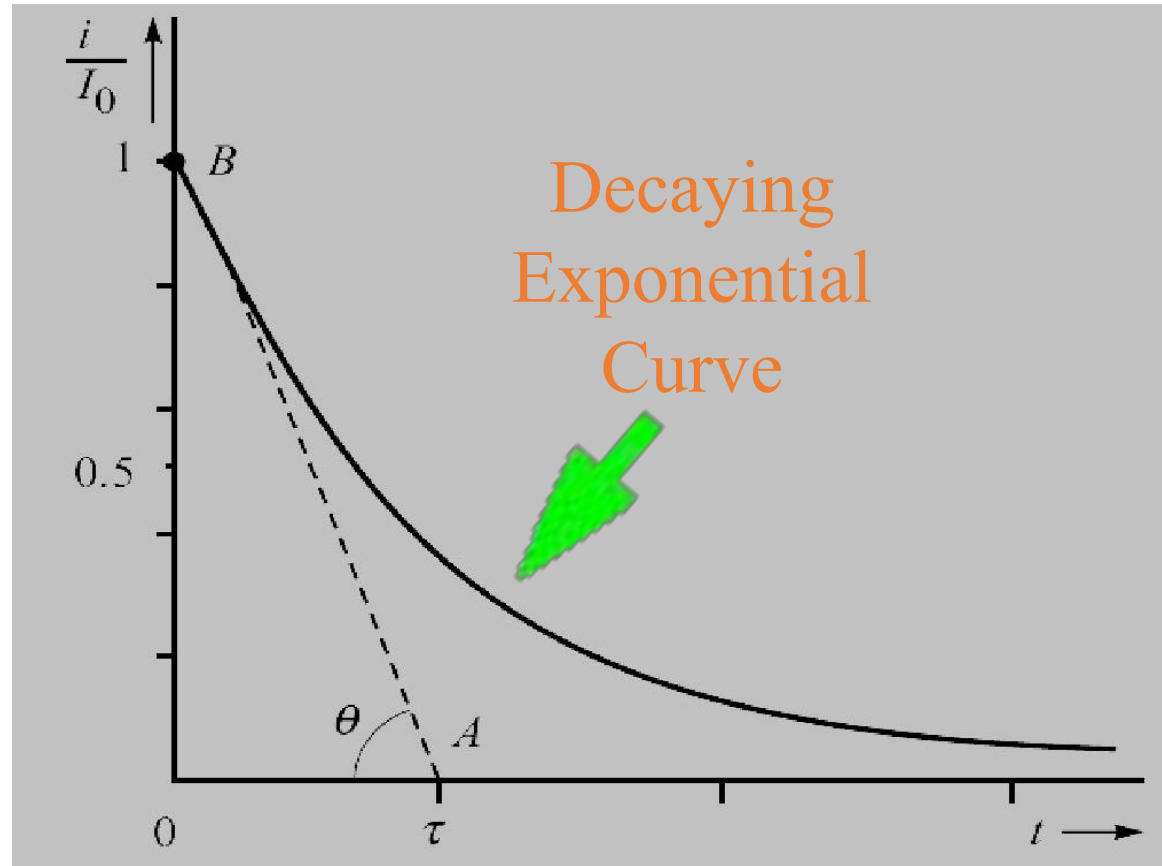

At $t = 0+$, the current is I_0 . As time increases, the current decreases and approaches zero.

Concept of Time Constant

- From equation, we see that with larger L/R ratio, the current takes longer to decay.
- By doubling L/R , the “width” of the curve also doubles.
- The “width” is proportional to L/R .
- Instead of “width”, we use the concept of “time constant (τ)”.

It is defined as the time taken for the current to drop to 37% of its initial value.

The initial rate of decay

= the slope of line AB

$$= \frac{d}{dt} (i / I_0) \Big|_{t=0} = -\frac{R}{L} e^{-Rt/L} \Big|_{t=0} = -\frac{R}{L}$$

From triangle OAB,

$$\tan \theta = \frac{1}{\tau} \quad \Rightarrow \quad \frac{1}{\tau} = \frac{R}{L} \quad \text{or} \quad \tau = \frac{L}{R}$$

- The ratio L/R must have the units of time.

Meaning of Time Constant

Determining the value of $i(t)/I_0$ at $t = \tau$, we have


$$\frac{i(\tau)}{I_0} = e^{-1} = 0.368 \quad \text{or} \quad i(\tau) = 0.368I_0$$

Thus, in one time constant the response drops to 36.8 % of its **initial value**. Hence,

$$i(2\tau) = 0.368i(\tau) = 0.368 \times 0.368I_0 = 0.1354I_0$$

How long does it take for the current to decay to zero ?

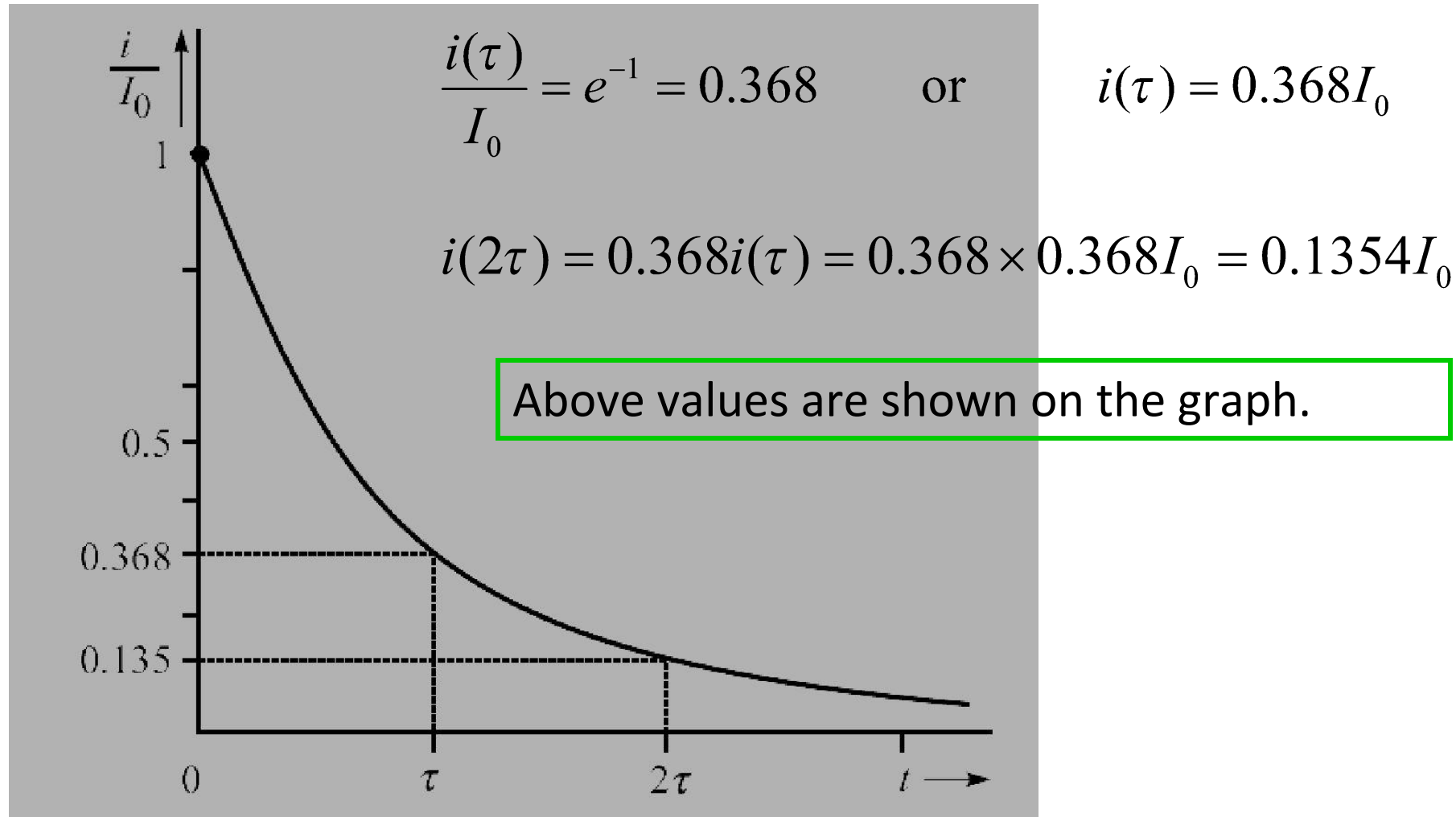Ans. : To answer this question, let us calculate



$$i(3\tau) = 0.0498I_0$$



$$i(4\tau) = 0.0183I_0$$

$$i(5\tau) = 0.0067I_0$$

... ..

- It takes about **five time constants** for the current to decay to zero.
- At the end of this time interval, the current is less than one percent of its original value.

RL Circuit

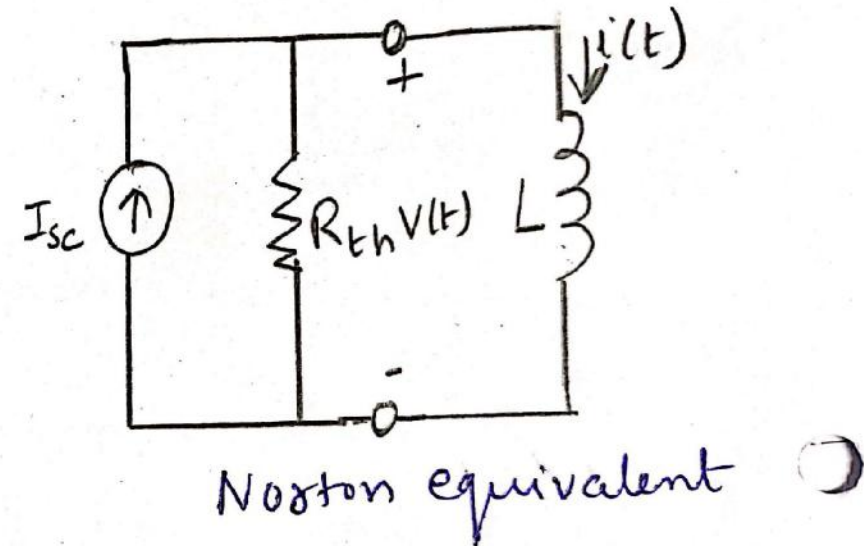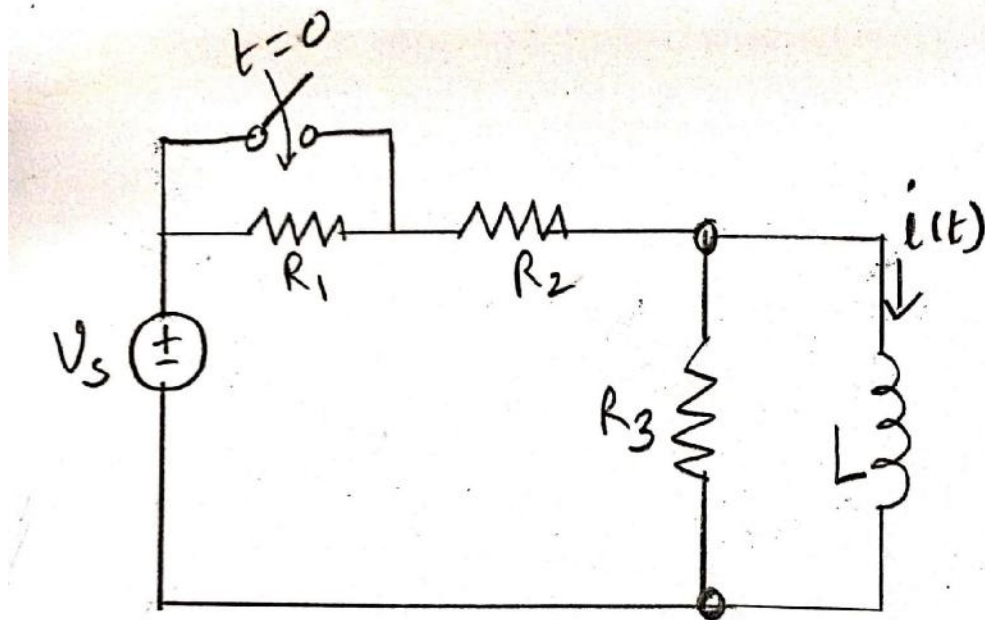

Norton's Equivalent

-

$$I_{sc} = \frac{V_s}{R_2}$$

$$R_t = \frac{R_2 R_3}{R_2 + R_3}$$

Inductor voltage is given as

$$v(t) = L \frac{di(t)}{dt}$$

- Apply KCL to the top node of Nortons equivalent

$$I_{sc} = i(t) + \frac{v(t)}{R_t}$$

After putting the value of v(t) in above equation

$$I_{sc} = i(t) + \frac{L \frac{di(t)}{dt}}{R_t}$$

$$\frac{d}{dt} i(t) + \frac{R_t}{L} i(t) = \frac{R_t}{L} I_{sc}$$

- Compare with the differential equation

- $\frac{d}{dt}x(t) + \frac{x(t)}{\tau} = K$

- $\frac{d}{dt}i(t) + \frac{R_t}{L}i(t) = \frac{L}{R_t}I_{sc}$

Here

$$x(t) = i(t), \tau = \frac{L}{R_t}, \text{ and } K = \frac{L}{R_t}I_{sc}$$

Making substitution in equation

- $x(t) = x(\infty) + (x(0) - x(\infty))e^{-t/\tau}$

In RL circuit

- $i(\infty) = I_{sc}$

- $i(t) = I_{sc} + (i(0) - I_{sc})e^{\frac{-R}{L}t}$

So Complete response $i(t)$ is sum of natural response and forced response

- Natural response = $(i(0) - I_{sc})e^{\frac{-R}{L}t}$
- Forced response = I_{sc}