

EC211 – ELECTRICAL SCIENCES-2

Tutorial Sheet – 4

1. Convert the following numbers to decimal:
(a) $1F3_{16}$ (b) $A0F_{16}$ (c) 372_8 (d) 156_8 (e) $(0.1011)_2$ (f) $(0.2143)_8$
2. Convert the following decimal number to the bases indicated.
a) 65477 to octal b) 65477 to hexadecimal c) 1231 to binary
3. Perform the following operations using 2's complement method –
(a) $48 + 23$, (b) $48 - 23$, (c) $23 - 48$, (d) $-48 - 23$
4. Subtract the following decimal numbers using 9's complement method –
(a) $72532 - 3250$, (b) $3250 - 72532$
5. Subtract the following unsigned binary numbers using 1's complement method –
(a) $1010100 - 1000100$, (b) $1000100 - 1010100$
6. Simplify the following Boolean Expressions -
 $A'BC + B'CD + AC + A'B'CD' \rightarrow C$
 $[AB'(C+BD) + A'B']C \rightarrow B'C$
7. Prove that
a) $A + A'B = A+B$
b) $(A+B)(A+C) = A+BC$
c) $A(A' + C)(A'B + C') = 0$
8. Simplify the following Boolean expressions
a) $AB + A(B+C) + B(B+C)$
b) $ABC + A'B'C' + ABC' + A'BC$
c) $A'BC + B'CD + AC + A'B'CD'$
9. Reduce the following expressions
a) $A + B(C + (DE)')'$
b) $((AB)' + A' + AB)'$
10. Implement the original and minimized Boolean expression for the given functions
a) $f = A'B'C + BC' + A'BC + ABC$
b) $F = BC'D' + A'BD + ABD + BCD' + B'CD + A'B'C'D + AB'C'D$
11. Express the following functions in a sum of minterms and a product of maxterms form
a) $F(A, B, C, D) = D(A' + B) + B'D$
b) $F(w, x, y, z) = y'z + wxy' + wxz' + w'x'z$
c) $F(A, B, C, D) = (A + B' + C)(A + B')(A + C' + D')$
d) $F(A, B, C) = (A' + B)(B' + C)$
12. Obtain the simplified expressions in product of sums:
a) $F(x, y, z) = \Pi M(0, 1, 4, 5)$
b) $F(A, B, C, D) = \Pi M(0, 1, 2, 3, 4, 10, 11)$

$$c) F(w, x, y, z) = \prod M(1, 3, 5, 7, 13, 15)$$

13. Simplify each of the following functions and implement them with NAND gates

$$a) F = ac' + ace + ace' + a'cd' + a'd'e'$$

$$b) F = AB' + A'B$$

14. Implement the following gates using Universal gates

a) XOR

b) XNOR

c) AND

d) OR

e) NOT

15. Use Karnaugh maps to simplify the following expressions

$$a) f(A, B, C, D) = A'BC + B'CD + AC + A'B'CD'$$

$$b) f(A, B, C, D) = ABC + BCD + AC + BC$$

16. Find out the minimal Boolean expression for the function given below by K-map

$$a) f(A, B, C, D) = \sum m(1, 3, 6, 7, 9, 13, 14, 15)$$

$$b) f(W, X, Y, Z) = \sum m(0, 1, 2, 3, 4, 7, 8, 11, 12, 14, 15)$$

17. Find out the minimal Boolean expression for the function given below by K-map

$$a) f(A, B, C, D) = \prod M(4, 6, 12, 13, 14, 15)$$

$$b) f(A, B, C, D) = \prod M(0, 1, 2, 3, 4, 7, 8, 11, 12, 14, 15)$$

18. Implement Sum and carry function of

a) Half Adder b) Full adder using NAND gates.

19. Realize a full Subtractor using NAND gates only.

20. Implement the four Boolean functions using three half-adder circuits.

$$D = A \oplus B \oplus C, \text{ where } \oplus \text{ is XOR gate.}$$

$$E = A'BC + AB'C$$

$$F = ABC' + (A' + B')C$$

$$G = ABC$$