


Complex power (Due to both Real and Imaginary part)

⊙ The product of the rms voltage<sup>phasor</sup> and the complex conjugate of the rms current phasor is known as complex power.

→ rms voltage phasor →  $\overline{V_{rms}}$

→ complex conjugate of rms current phasor →  $\overline{I_{rms}}$

Example

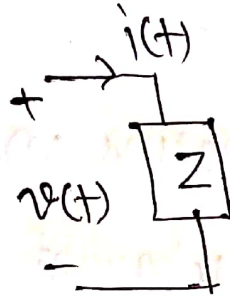

→  $v(t) \Rightarrow V_{rms}, \theta_v$  ← phase angle

$$\overline{V_{rms}} = V_{rms} \angle \theta_v$$

→  $i(t) \Rightarrow I_{rms}, \theta_i$  ✓

$$\overline{I_{rms}} = I_{rms} \angle \theta_i$$

$$\overline{I_{rms}}^* = I_{rms} \angle -\theta_i$$

Therefore,

$$\text{Complex power } (\overline{S}) = \overline{V_{rms}} \cdot \overline{I_{rms}}^*$$

$$\overline{S} = V_{rms} \angle \theta_v \cdot I_{rms} \angle -\theta_i$$

amp

$$\overline{S} = V_{rms} \cdot I_{rms} \angle (\theta_v - \theta_i)$$

Formula for average power:

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$P = \text{Real} \left\{ \frac{1}{2} V_m I_m e^{j(\theta_v - \theta_i)} \right\}$$


$$P = \text{Real} \left\{ \frac{V_m}{\sqrt{2}} e^{j\theta_v} \cdot \frac{I_m}{\sqrt{2}} e^{-j\theta_i} \right\}$$

$$P = \text{Real} \left\{ \underbrace{V_{rms} \angle \theta_v \cdot I_{rms} \angle -\theta_i}_{\text{Complex}} \right\}$$

$$\boxed{\bar{S} = \bar{V}_{rms} \bar{I}_{rms}^*} \quad \text{Proof}$$

Hint: complex power always measured in Volt Ampere.

→ Also called as apparent power.

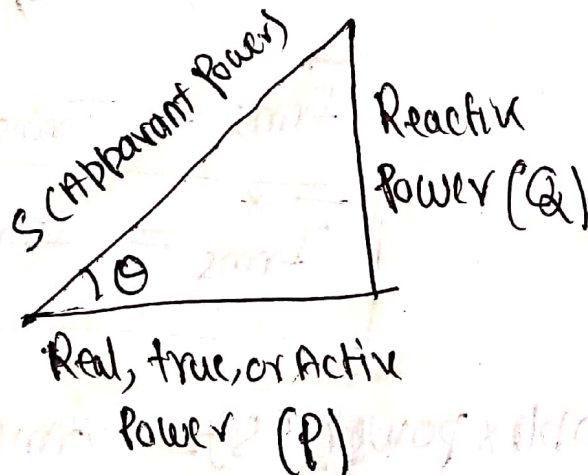

$$S = P + jQ$$

$$\boxed{|S| = \sqrt{P^2 + Q^2}}$$

Summary:

$$\text{Complex Power } (S) = V_{rms} \cdot I_{rms}^* \angle \theta_v - \theta_i$$

$$\boxed{\text{Example: } \theta_v < \theta_i}$$

$$\boxed{S = V_{rms} I_{rms} [\cos(\theta_v - \theta_i) + j \sin(\theta_v - \theta_i)]}$$

$$\boxed{S = P \angle \theta}$$