
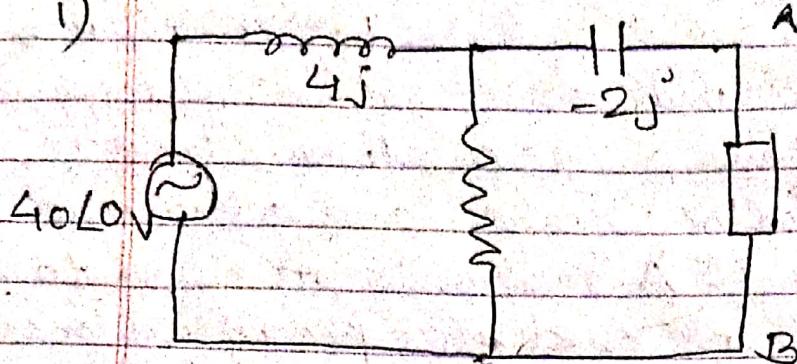


Assignment - 2

1)

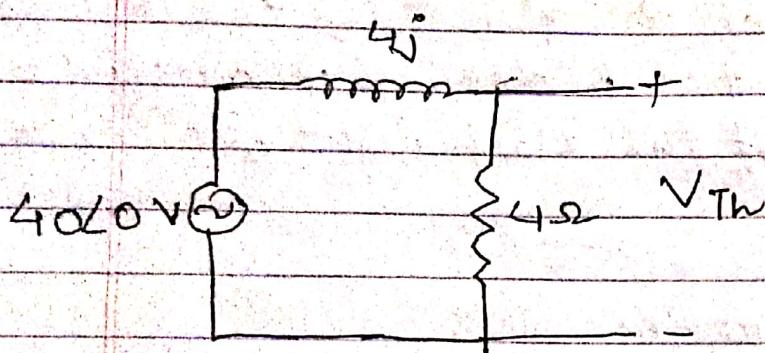

$$P_{max} = \frac{|V_{max}|^2}{8 R_{th}}$$



$$i = 40 / 4 + 4j^\circ$$


$$V_{th} = 4 \left(\frac{40}{4 + 4j^\circ} \right) = 40 / (4 + j^\circ)$$

$$= 40 \cdot \frac{(1-j)}{2} = 20 - 20j^\circ = 20\sqrt{2} \angle 135^\circ$$

$$Z_{th} = \frac{16j^\circ}{4 + 4j^\circ} + (-2j^\circ) = \frac{16j^\circ - 8j^\circ + 8}{4 + 4j^\circ} = 2$$


$$P_{max} = \frac{(20\sqrt{2})^2}{3 \times 2} = 100W \quad [P_{max} = 100W]$$

2)

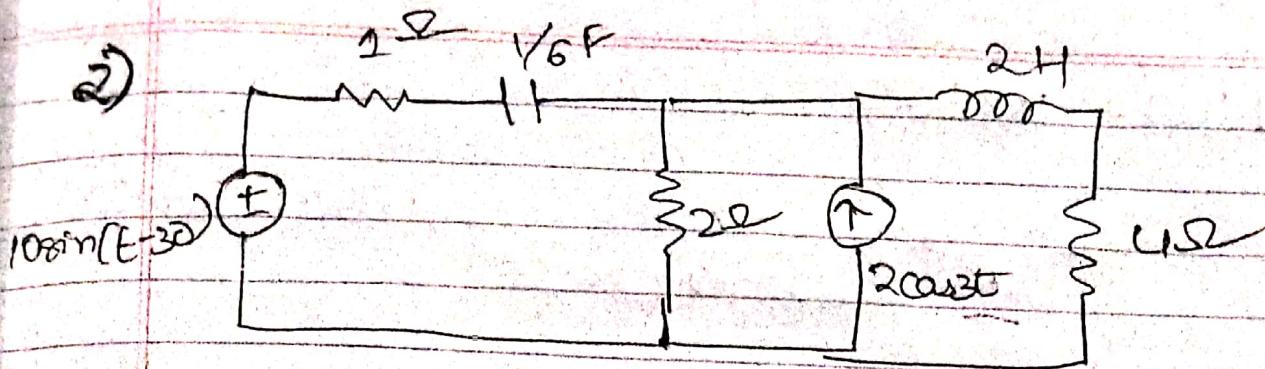

Applying superposition theorem

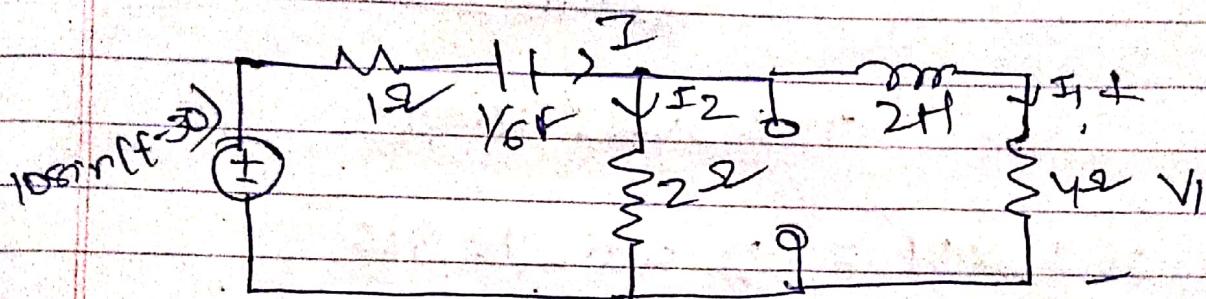When $10\sin(t-30)$ voltage source is active



$$R = (1 - j6) + \frac{2(4 + j2)}{2 + 4 + j2}$$

$$R = 1 - j6 + \frac{8 + j4}{6 + j2}$$

$$R = 1 - j6 + \frac{4 + j2}{3 + j}$$

$$R = \frac{3 - j18 + j4 + 4 + j^2}{3 + j}$$

$$R = \frac{13 - j15}{3 + j} = \frac{\sqrt{(13)^2 + (-15)^2}}{\sqrt{(3)^2 + 1^2}} \angle \left(\tan^{-1} \frac{-15}{13} - \tan^{-1} \frac{1}{3} \right)$$

$$= \frac{19.899}{3.162} \angle (49.085^\circ - 18.435^\circ)$$

$$R = 6.277 \angle 30.65^\circ$$

$$V(\omega) = 10 \angle 60^\circ$$


$$\therefore I = V(\omega) = \frac{10 \angle 60^\circ}{R} = \frac{10 \angle 60^\circ}{6 + j2} = 1.593 \angle 29.35^\circ$$

there $I_1 = \frac{I \times 2}{2 + (4 + j2)} = \frac{1.593 \angle 29.35^\circ \times 2}{6 + j2}$

$$= \frac{1.593 \angle 29.35^\circ - 18.435}{3.162} \approx 0.504 \angle 10.915^\circ$$

$$V_1 = I_1 \times 4 = 2.016 \angle 10.915^\circ$$

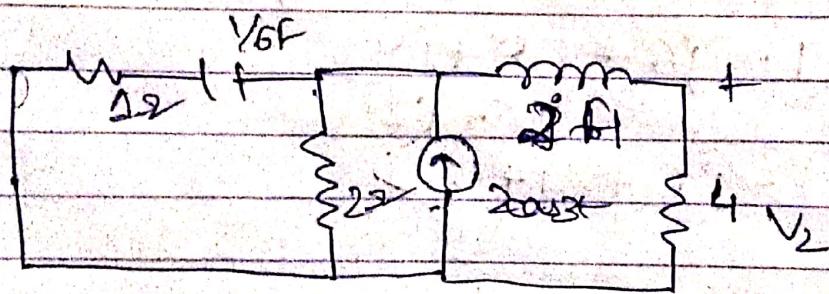Now when 2 const current source is active




$$R_C = \frac{1}{\omega C} = -j2 \rightarrow R_L = j\omega L = j6$$

No CO

$$R' = \frac{(1-j2) \times 2}{3-2j} = \frac{2-j4}{13} (3+2j)$$
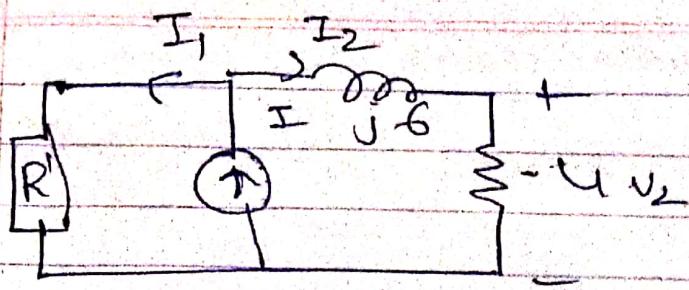
$$= \frac{6+4j-12j+8}{13} = \frac{14-8j}{13}$$



$$\text{Here } I_2 = \frac{I \times R'}{R' + (4 + 6j)} = \frac{2 \times 2}{\frac{2}{13}(7 - 4j) + 2(2 + 3j)}$$

$$I_2 = \frac{\frac{11}{13}(8.062) \angle -29.745^\circ}{\frac{12}{13}(7.4j + 26 + 39j)}$$



$$\text{Hence } I_2 = 0.335 \angle -32.423^\circ$$

$$\therefore V_2 = I_2 \times 4 = 1.34 \angle -32.423^\circ$$

$$\therefore V_{42} = V_1 + V_2 = 2.016 \angle 10.915^\circ + 1.34 \angle -32.423^\circ$$

$$V_{42} = 2.016 \cos(t + 10.915) + 1.34 \cos(3t - 32.423)$$


3)

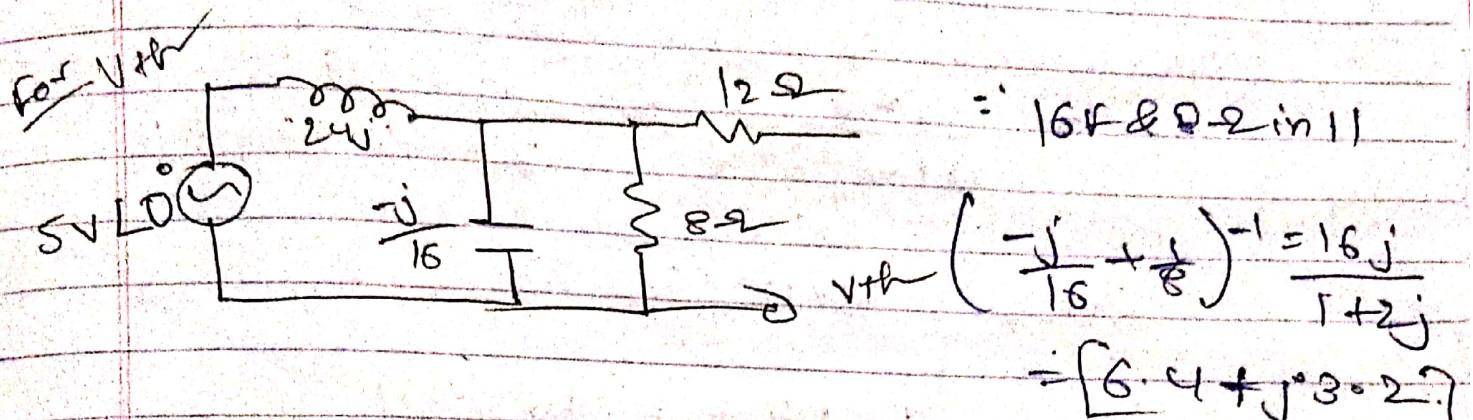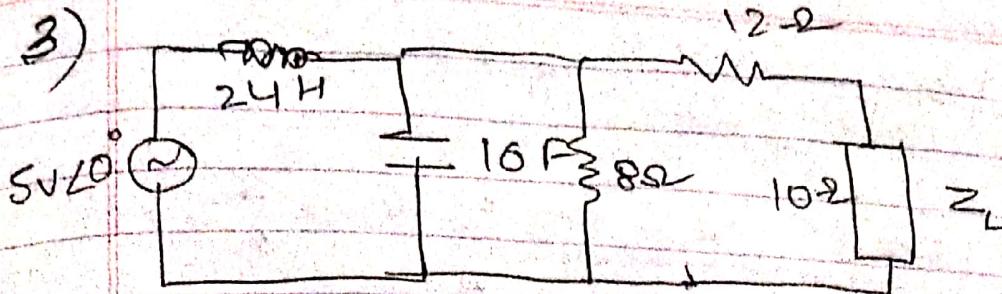

$$V_{th} = \frac{5 \times (6.4 + j^3.2)}{j24 + (6.4 + j^3.2)}$$

$$= \frac{32 + 16j}{6.4 + j^27.2} = \frac{35.77}{27.94} \angle 2.70 - 13.73$$

$$V_{th} = 1.28 \angle -11.03$$

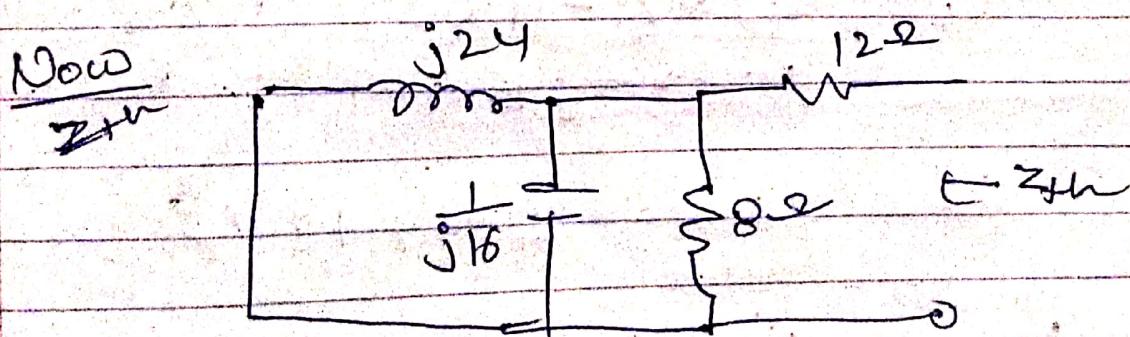

$$Z_{th} = j24 || (6.4 + j^3.2) + 12$$

$$= \frac{24j(6.4 + j^3.2)}{j24 + 6.4 + j^3.2} + 12$$

$$Z_{th} = \frac{153.6j - 76.8}{6.4 + j27.2} + 12$$


$$= \frac{153.6j - 46.8 + 76.8 + j326.4}{6.4 + j27.2}$$

$$= \frac{480j}{6.4 + j27.2} = \frac{480 \angle 90^\circ}{27.94 \angle 23.73^\circ}$$

$$Z_{th} = 17.18 \angle 76.27^\circ$$

$$Z_{th} = 4.078 + j16.689$$

Equivalent circuit

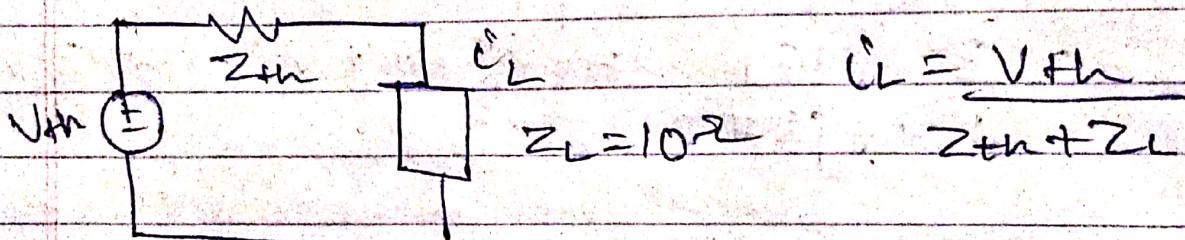


$$i_L = \frac{V_{th}}{Z_{th} + Z_L}$$

$$i_L = \frac{1.28 \angle -11.03^\circ}{4.078 + j16.689} = \frac{1.28 \angle -11.03^\circ}{21.83 \angle 63.14^\circ}$$

$$i_L = 0.058 \angle -19.179^\circ$$

$$\begin{aligned} P_{max} &= \frac{V^2}{Z_L} \\ &= (0.058)^2 \cdot 10 \end{aligned}$$

$$(P_{max} = 0.0337 \text{ watt})$$

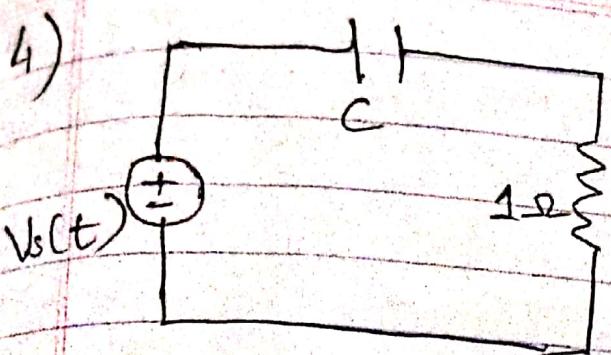

$$V_s(t) = 4.68 \cos(2t + 47^\circ)$$

$$V_o(t) = 1.59 \cos(2t + 125^\circ)$$

$$i_o(t) = 1.59 \cos(2t + 125^\circ)$$

$$i_o(t) = 1.59 \angle 125^\circ A$$

$$X_C = \frac{-j^\circ}{2 \times C} = \frac{-0.5 j^\circ}{C}$$

$$V_s(t) = I_o(t) \times Z$$

$$\frac{4.68 \angle 47^\circ}{1.59 \angle 125^\circ} = 1 - j \frac{0.5}{C}$$

$$4.03 \angle -78^\circ = 1 - j \frac{0.5}{C}$$

$$4.03 \angle -78^\circ = \sqrt{1 + \frac{0.25}{C^2}} \tan^{-1} \left(\frac{-j 0.5}{\frac{0.25}{C^2}} \right)$$

On comparison

$$4.83 = \sqrt{1 + \frac{0.25}{C^2}}$$



$$22.32 = 1 + \frac{0.25}{C}$$

$$22.32 C^2 = 0.25$$

$$C^2 = \frac{0.25}{22.32}$$

$$C = \sqrt{\frac{0.25}{22.32}} = \sqrt{0.011} = 0.1088 F$$

5)

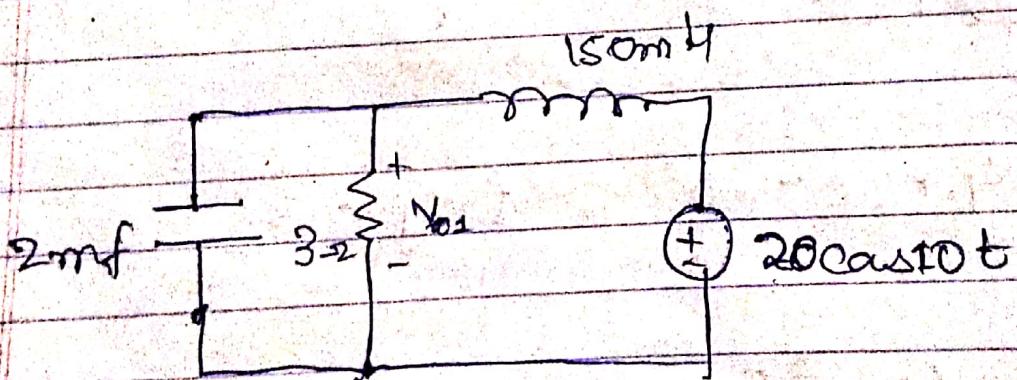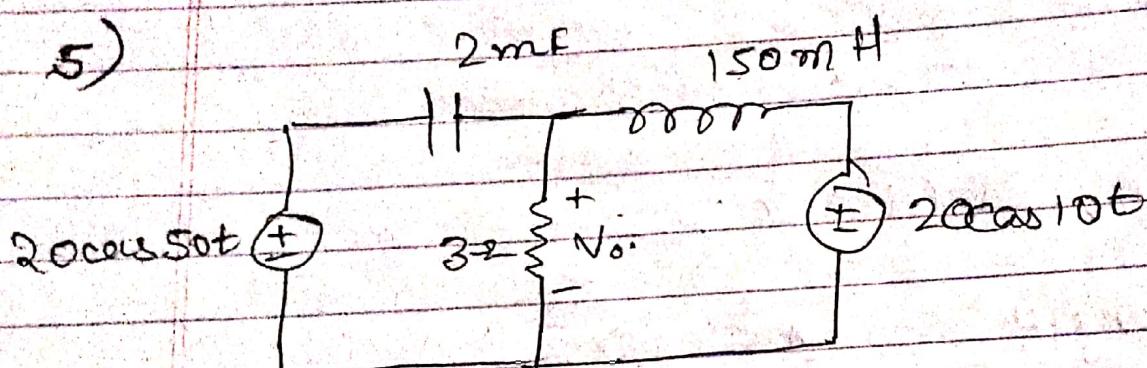

$$X_C = \frac{-j}{10 \times 2 \times 10} = -j 50$$

$$\begin{aligned}
 Z_{\text{net}} &= \frac{-j400}{8-j50} + j1.5 = \frac{-j400 + 12j + 7.5}{8-j50} \\
 &= \frac{45 - j^388}{8-j50} = \frac{39.5 - 18}{50.63} / \angle -119.8 + 11.10^\circ
 \end{aligned}$$

$$Z_{\text{net}} = 4.80 \angle 9.908^\circ$$


$$\begin{aligned}
 \text{Now, } V_{\text{source}} &= \frac{V \times 1.5 \angle 90^\circ}{Z_{\text{net}}} = \frac{20 \angle 0^\circ \times 1.5 \angle 90^\circ}{7.80 \angle 9.908^\circ} \\
 &= \frac{30}{7.80} \angle 90 - 9.908^\circ \\
 &= 3.846 \angle 80.092^\circ
 \end{aligned}$$

$$V_{01} = V - V_{\text{source}}$$

$$V_{01} = 20 \angle 0^\circ - 3.846 \angle 80.092^\circ$$

$$V_{01} = 2 \cos 0t - 3.846 \cos(10t + 80.092^\circ)$$

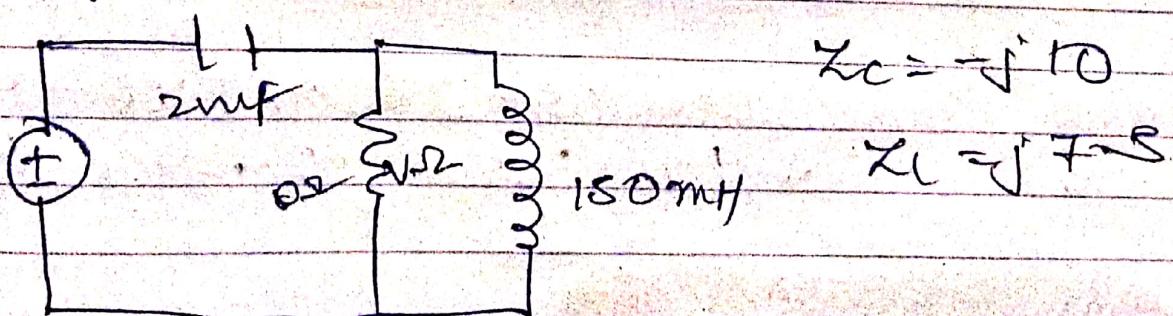Where $2 \cos 0t$ voltage source is active



$$Z_{\text{net}} = \frac{j7.5 \times 8 - j10}{8 + j7.5}$$

$$Z_{\text{net}} = \frac{60j - j80 + 7.5}{8 + j7.5} = \frac{45 - 20j}{8 + j7.5}$$

$$Z_{net} = \frac{47.62}{10.97} \angle -1.16 - 11.05^\circ$$

$$[Z_{net} = 4.08 \angle -12.21^\circ]$$

$$No. \ V_{2mp} = \frac{V - X \cdot j^{\circ} 10}{Z_{net}}$$

$$= \frac{20 \angle 0}{4.08 \angle -12.21} \times 10 \angle -90$$

$$= \frac{200}{4.08} \angle -90 + 12.21$$

$$= 28.24 \angle -77.79$$

$$V_{o_2} = V - V_{2mp}$$

$$= 20 \angle 0 - 28.24 \angle -77.79$$

$$= 20 \cos 0t - 28.24 \cos(50t - 77.79)$$

$$V_o = V_{o_1} + V_{o_2}$$

$$V_o = [20 \cos 10t - 3.85 \cos(10t + 80.09)]$$

$$+ [20 \cos 50t - 28.24 \cos(50t - 77.79)]$$