

Steady State and Transient Response

Content

- Steady State response
- Transient response
- Types of circuit excitation
- First order circuit
 - RC Circuit
 - RL Circuit


Steady State

- Both the inductance and capacitance are energy-storing elements.
- When connected to a dc source, energy starts flowing to these elements.
- Initially the rate of flow of energy is high, but as more and more energy is stored, the rate of flow decreases.
 - When maximum possible energy has been stored, the flow of energy stops altogether. We say that the circuit has reached its ‘**steady state**’.


Transient Response

- If we switch off the source, or switch over the network to another source, the circuit starts attaining another ‘steady state’.
- The time taken by the circuit to change over from one steady-state condition to another steady-state condition is called *transient time*.
- The response of the circuit during this time is known as *transient response*.


Types of Circuit Excitation

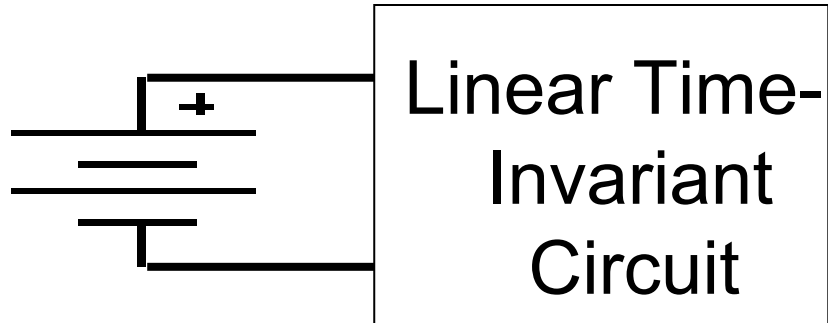

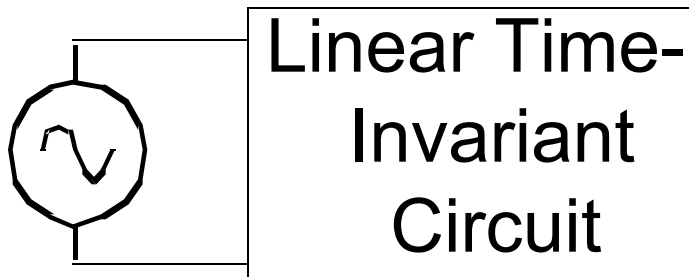
**Steady-State Excitation
(DC Steady-State)**



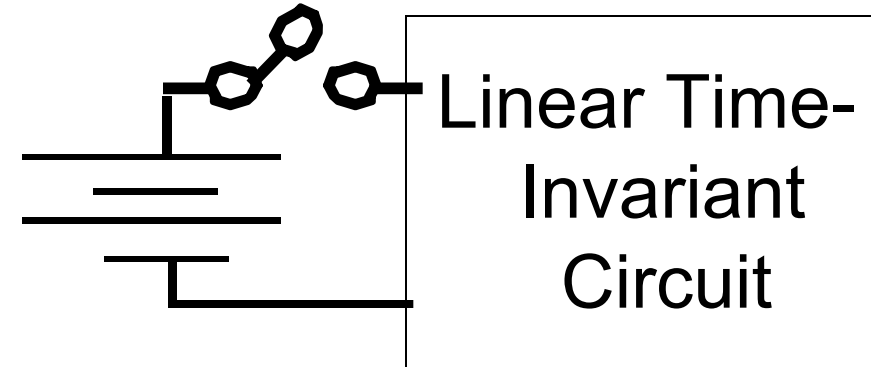Sinusoidal (Single-Frequency) Excitation
☐ **AC Steady-State**





OR

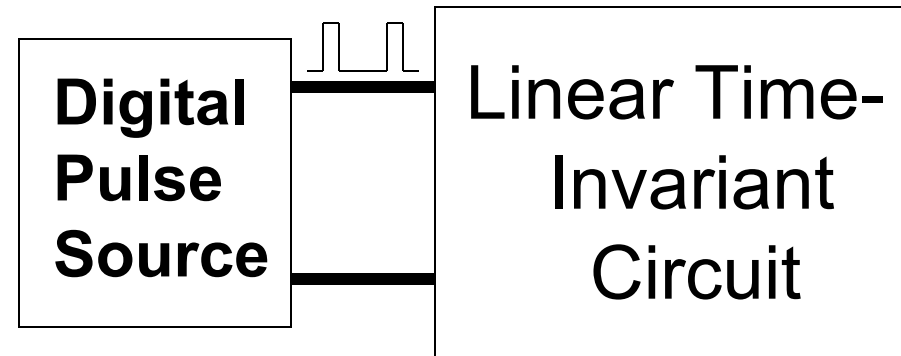

Transient Excitation


First-Order Circuits

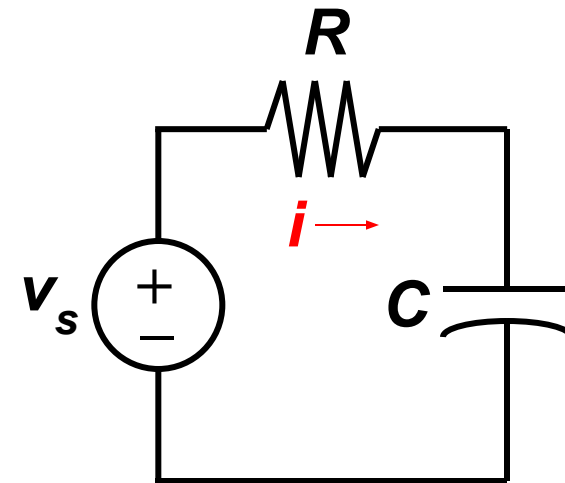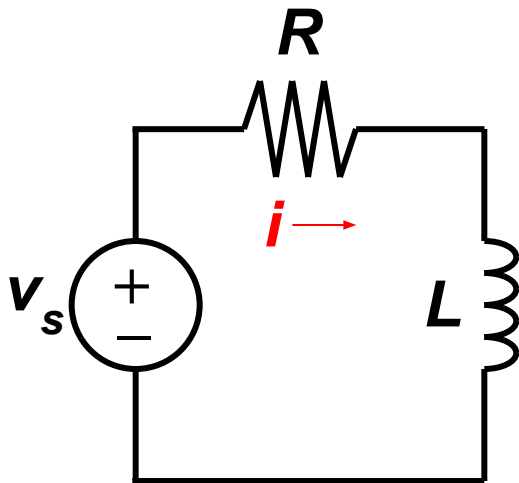- A circuit that contains only sources, resistors and an inductor is called an ***RL circuit***.
- A circuit that contains only sources, resistors and a capacitor is called an ***RC circuit***.
- RL and RC circuits are called first-order circuits because their voltages and currents are described by first-order differential equations.



Review (Conceptual)

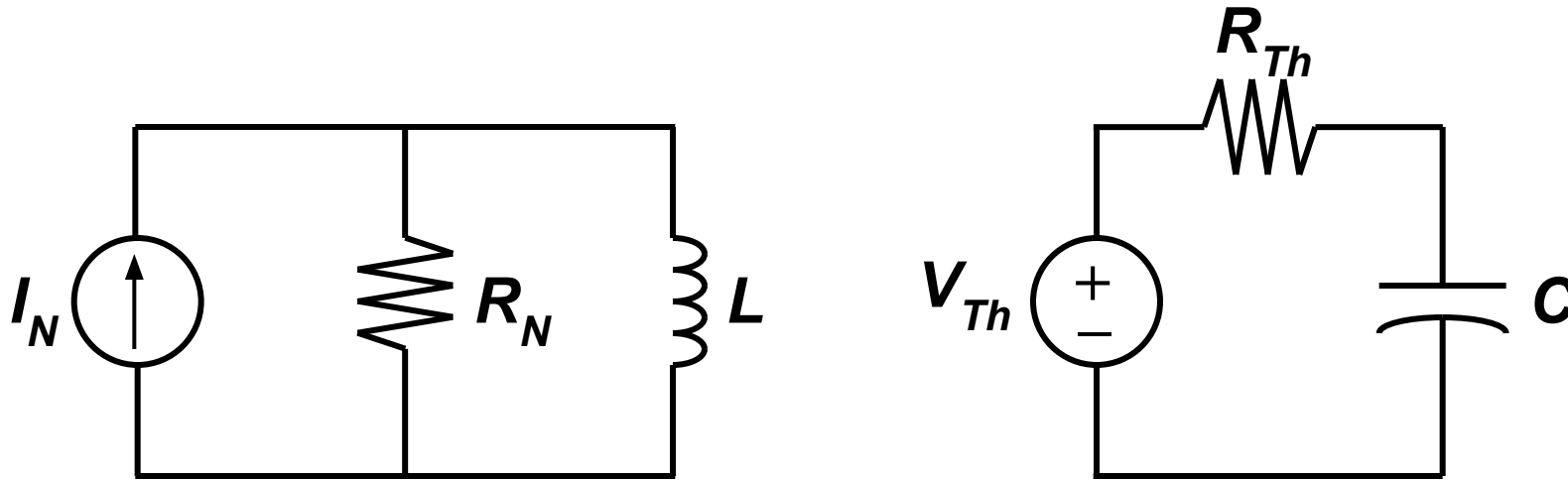- Any first-order circuit can be reduced to a Thévenin (or Norton) equivalent connected to either a single equivalent inductor or capacitor.



- In steady state, an inductor behaves like a short circuit
- In steady state, a capacitor behaves like an open circuit


Complete response of a circuit

Complete response = natural response + forced response

- The **natural response** is the general solution of the differential equation representing the first-order circuit, when the input is set to zero.
- The ***step response*** of an RL or RC circuit is its behavior when a voltage or current source **step** is applied to the circuit, or immediately after a switch state is changed.

Response of first order circuit to a constant input

- RC Circuit

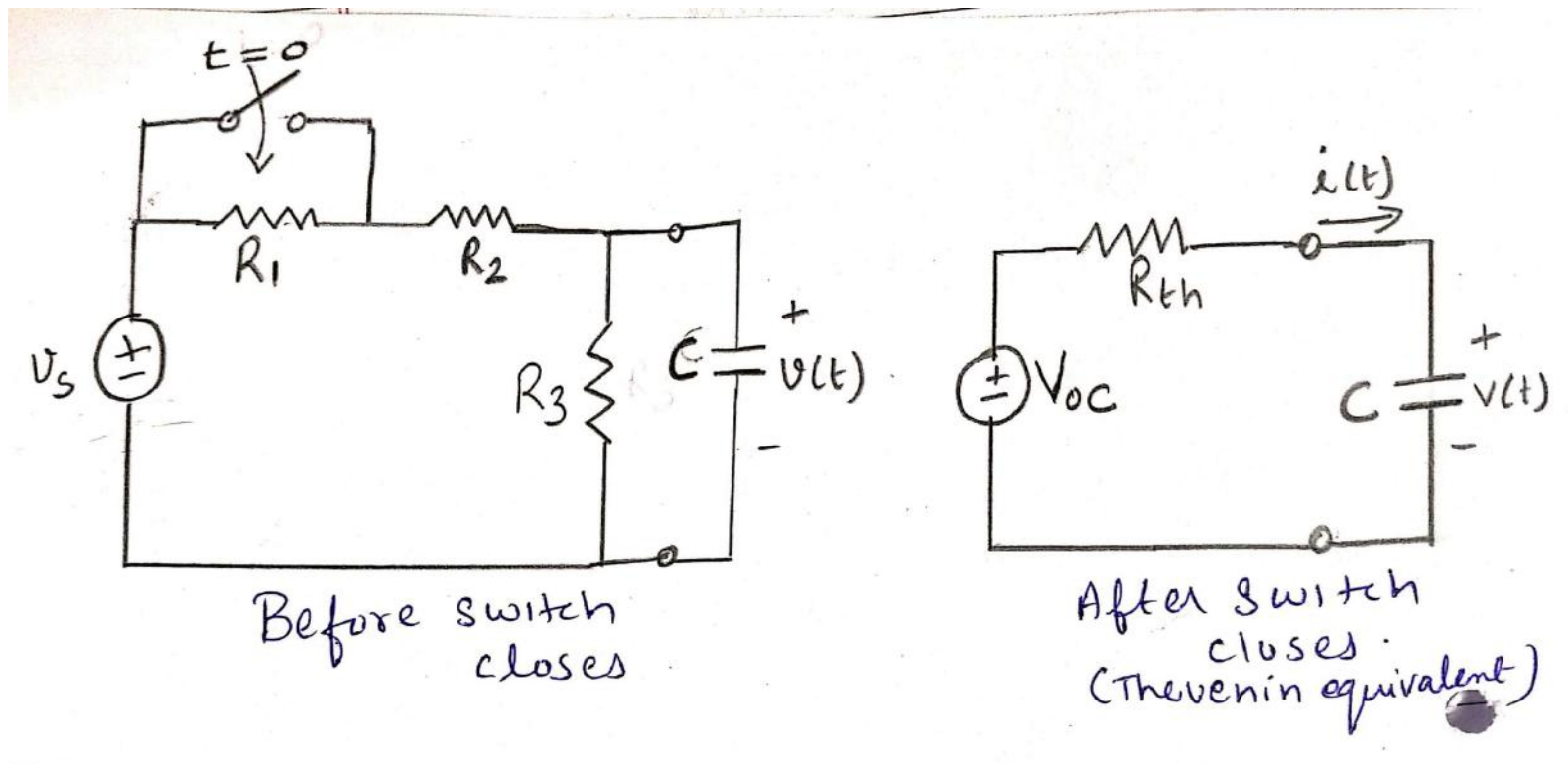

- Thevenins Equivalent

$$V_{oc} = \frac{R_3}{R_2 + R_3} V_s$$

$$R_t = \frac{R_2 R_3}{R_2 + R_3}$$

- Capacitor Current

$$i(t) = C \frac{d}{dt} v(t)$$

Apply KVL to Thevenin equivalent

$$V_{oc} = R_t i(t) + v(t)$$

Putting value of $i(t)$

$$V_{oc} = R_t C \frac{d}{dt} v(t) + v(t)$$

$$\frac{d}{dt}v(t) + \frac{v(t)}{R_t C} = \frac{V_{oc}}{R_t C}$$

- The highest-order derivative in this equation is first order, so this is a first-order differential equation.

Equation has form

$$\frac{d}{dt} x(t) + \frac{x(t)}{\tau} = K$$

where τ = time constant

To solve the above equation the variables are separated and then integrated

we write the equation as

$$\frac{dx}{dt} = \frac{K\tau - x}{\tau}$$

$$\text{or } \frac{dx}{K\tau - x} = -\frac{dt}{\tau}$$

forming the indefinite integral, we have

$$\int \frac{dx}{K\tau - x} = -\frac{1}{\tau} \int dt + D$$

where D is constant of integration

$$\ln(K\tau - x) = -\frac{t}{\tau} + D$$

Solving for x gives -

$$x(t) = k\tau + Ae^{-t/\tau} \quad - (1)$$

where $A = e^D$, which is determined from initial condn, $x(0)$

To find A , let $t = 0$, then.

$$x(0) = k\tau + Ae^{-0/\tau} = k\tau + A$$

$$A = x(0) - k\tau$$

Now putting value of A in eq (1)

$$x(t) = k\tau + [x(0) - k\tau]e^{-t/\tau} \quad - (2)$$

Similarly in eq (1)

$$x(\infty) = \lim_{t \rightarrow \infty} x(t) = k\tau$$

Equation (2) can be written as.

$$x(t) = x(\infty) + [x(0) - x(\infty)]e^{-t/\tau}$$

Taking the derivative of $x(t)$ with respect to t will give time constant

$$\frac{d}{dt} x(t) = -\frac{1}{\tau} [x(0) - x(\infty)]e^{-t/\tau} \quad - (3)$$

Now let $t = 0$ in eq (3)

$$\left. \frac{d}{dt} x(t) \right|_{t=0} = -\frac{1}{\tau} [x(0) - x(\infty)]$$

$$\tau = \frac{x(\infty) - x(0)}{\left. \frac{d x(t)}{dt} \right|_{t=0}}$$

Differential equation for RC circuit was

$$\frac{d V(t)}{dt} + \frac{V(t)}{R C} = \frac{V_{oc}}{R C}$$

Comparing with eq

$$\frac{d x(t)}{dt} + \frac{x(t)}{\tau} = K$$

We see that

$$x(t) = V(t), \tau = R C \text{ and } K = \frac{V_{oc}}{R C}$$

Making these substitution

$$V(t) = V_{oc} + [V(0) - V_{oc}] e^{-t/R C}$$

$$V(t) = V_{oc} + [V(0) - V_{oc}] e^{-t/R C} \quad (4)$$

The second term on RHS dies as t increases. This is transient or natural response.

$$\text{At } t = 0, \text{ in eqn (4), } e^{-0} = 1$$

so

$$V(0) = V(0) \text{ as required.}$$

$$\text{When } t = 5 \tau, e^{-5} = 0.0067 \approx 0$$

so at $t = 5 \tau$

$$V(5 \tau) = 0.9933 V_{oc} + 0.0067 V(0)$$

$$V(5 \tau) \approx V_{oc}$$

This is steady state or forced response.

Complete response = NR + FR

$$NR = [V(0) - V_{oc}] e^{-t/(R_{tc})}$$

$$FR = V_{oc}$$

So

Complete response is

$$V(t) = V_{oc} + [V(0) - V_{oc}] e^{-t/R_{tc}}$$

RL Circuit

