
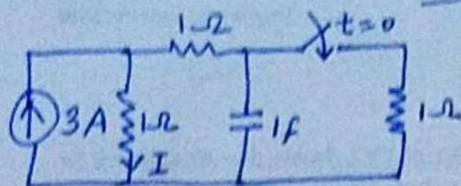


# Solution tut 1

①

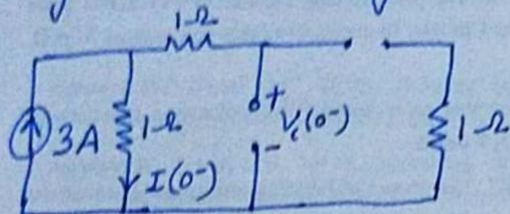


Finding initial voltage + current



$$I(0^-) = 3A$$

$$V(0^-) = 3V$$

For  $t = 0^+$

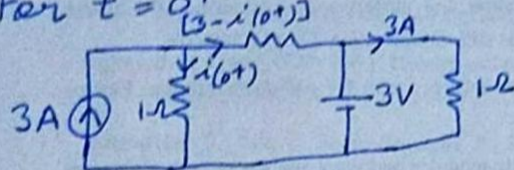

$$3 = -1[3 - i(0^+)] + 1 \cdot i(0^+)$$

$$3 = -3 + 2i(0^+)$$

$$i(0^+) = \frac{6}{2} = \underline{\underline{3A \text{ Ans}}}$$


② The situation at  $t = 0^-$  inductor is S.C.

So,  $20\Omega$  will get S.C.

Then,  $30\Omega$  parallel with S.C.

Hence  $i_L(0^-) = i_L(0^+) = 2A$  [means whole current passes through SC path]

Now, to find  $V(0^+)$  the circuit

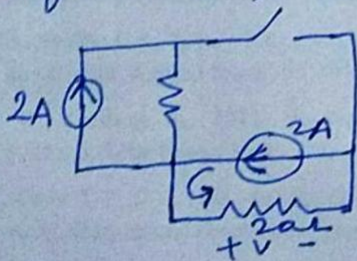


⇒ means 2A current flows through  $20\Omega$  resistance

$$\text{So, } V(0^+) = 2 \times 20 = 40V$$




③ At  $t=0^-$

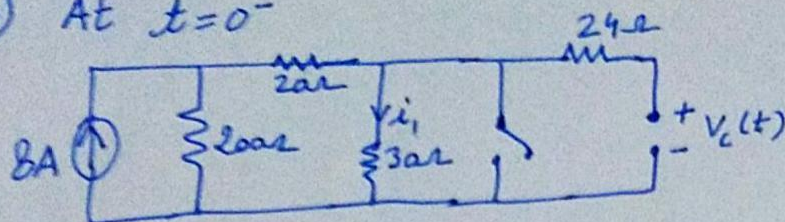

Means  $V_c(0^-)$  is same as across  $30\Omega$

So,  $i_1 = \frac{8 \times 200}{200+50} = \frac{32}{5} \text{ A}$ ,  $V_c(0^-) = 30 \times \frac{32}{5} = 192 \text{ V}$

Now, at  $t=0^+$

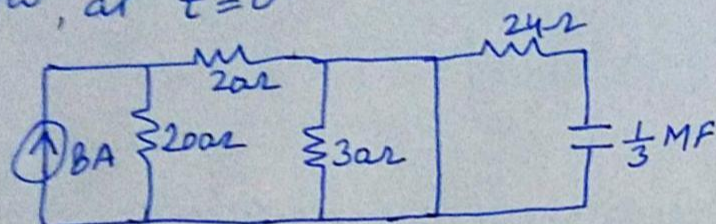

So, cap<sup>r</sup> starts discharging through S.C. path

$$V(t) = V_0 e^{-t/RC} = 192 e^{-t/24 \times \frac{1}{3} \times 10^{-3}}$$

$$= 192 e^{-125t}$$


or

$$V(\infty) = 0$$


So,  $V(t) = 0 - [(0-192)] e^{-t/24 \times \frac{1}{3} \times 10^{-3}}$

$$= 192 e^{-125t} \text{ Ans}$$

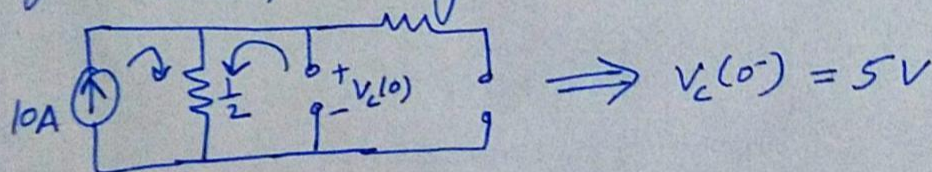④ To find initial voltage across cap<sup>r</sup>



For  $t > 0$

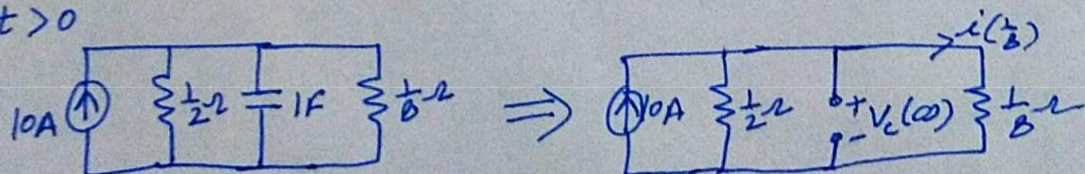

So,  $i(\frac{1}{8}) = \frac{10 \times \frac{1}{2}}{\frac{1}{2} + \frac{1}{8}} = 8 \text{ A}$ ,  $V_c(\infty) = \frac{1}{8} \times 8 = 1 \text{ V}$ ,  $R_{th} = \frac{1/2 \parallel 1/8}{1} = \frac{1}{10}$

Now,  $V_c(t) = 1 - (1-5) e^{-t/R_{th}} = 1 + 4 e^{-10t} \text{ Ans}$

