

Natural and Step Responses of RLC Circuits


EE3301

Kamran Kiasaleh

Learning Objectives


1. Be able to determine the natural responses of parallel and series RLC circuits
2. Be able to determine the step responses of parallel and series RLC circuits
3. Be able to determine the responses (both natural and transient) of second order circuits with op amps

Parallel *RLC* circuit

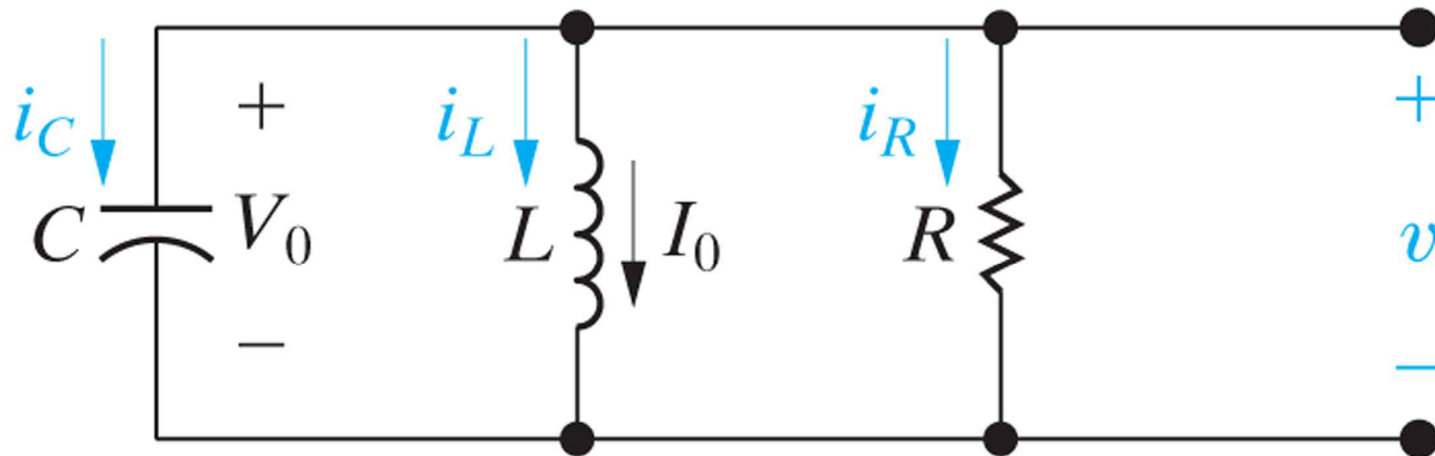


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

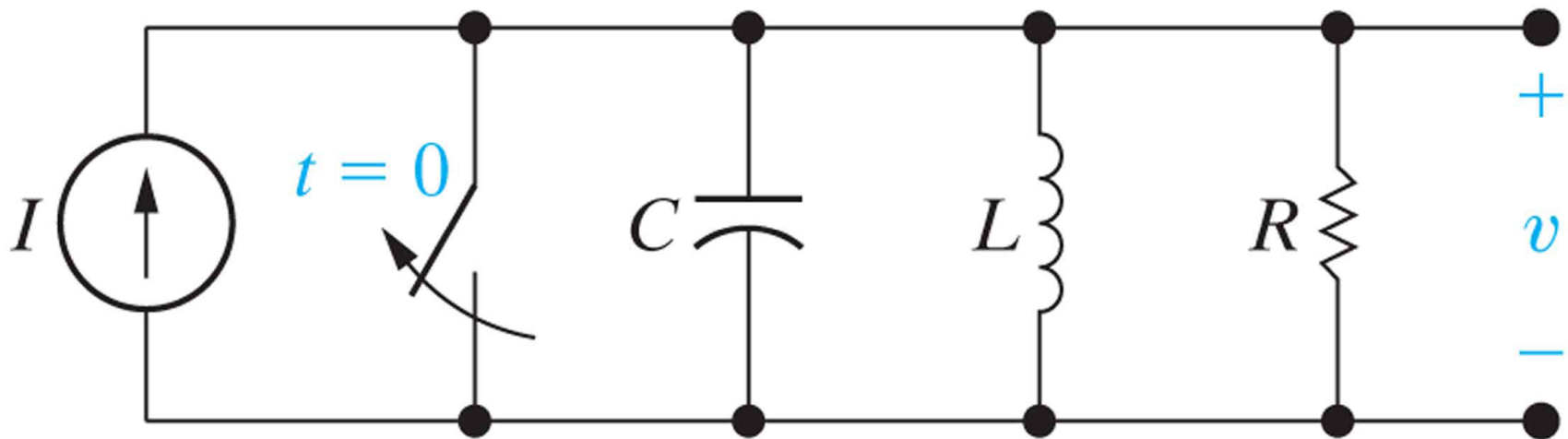
The step response of a parallel RLC circuit.



A series *RLC* circuit.

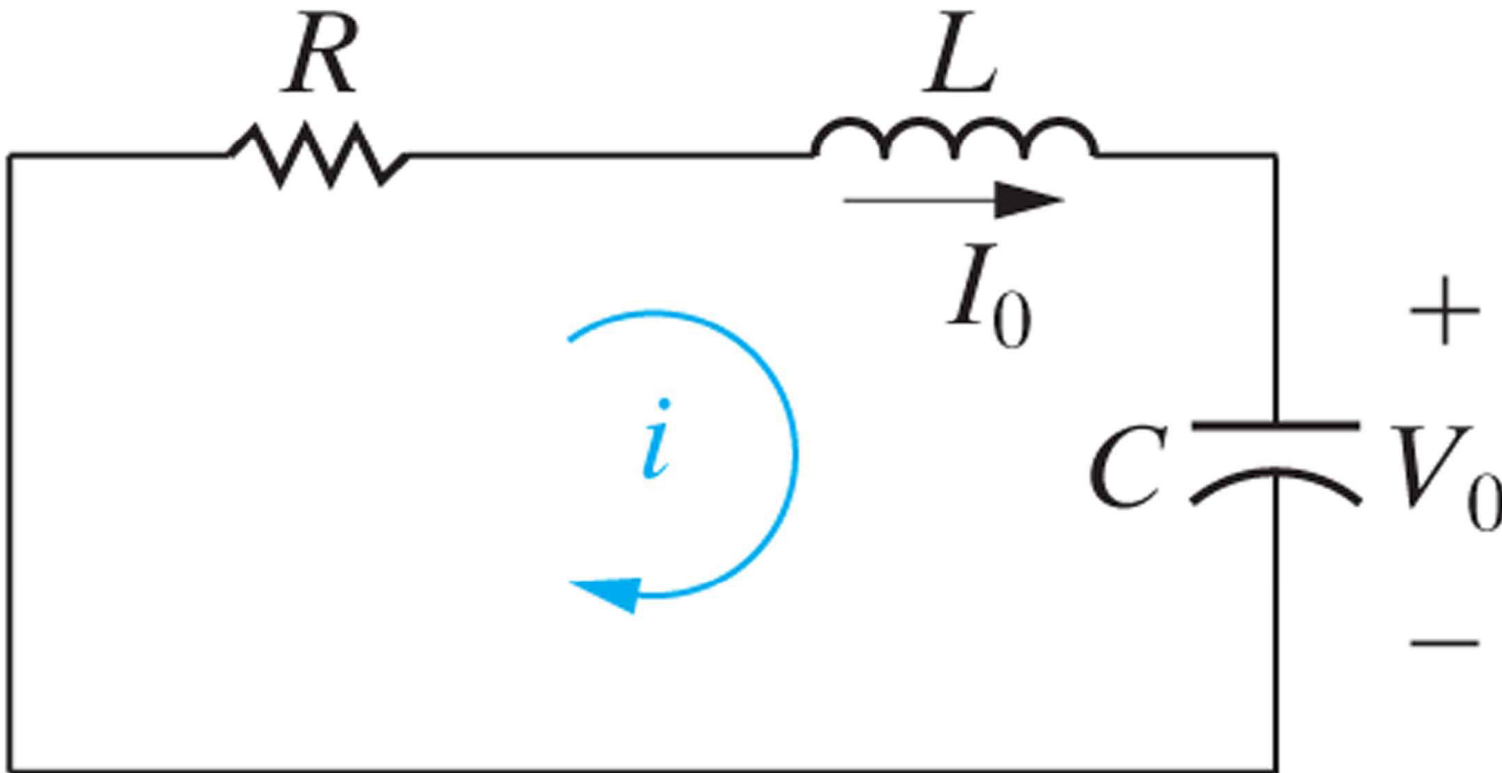

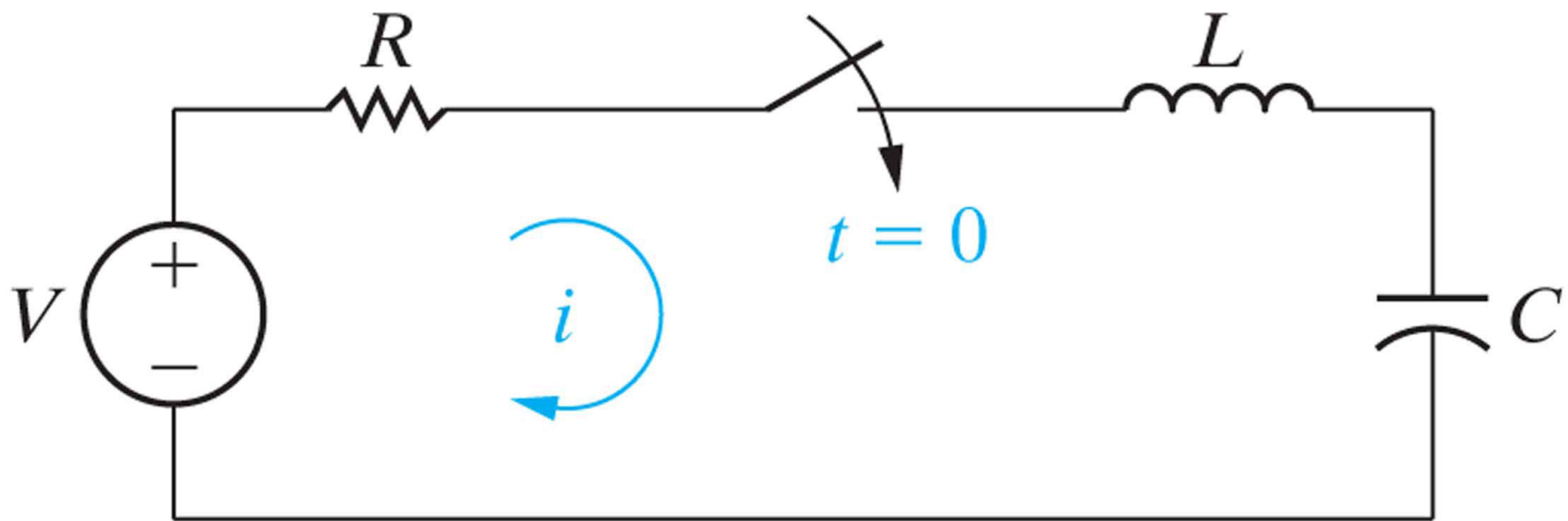
The step response of a series *RLC* circuit.



The Natural Response of a Parallel RLC

1. Using KCL,

This will disappear



$$v(t)/R + \frac{1}{L} \int_0^t v(s) ds + C \frac{dv(t)}{dt} + I_0 = 0$$

$$\frac{d^2 v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{v(t)}{LC} = 0$$

The Natural Response of a Series RLC

1. Using KVL,

This will disappear

$$Ri(t) + \frac{1}{C} \int_0^t i(s) ds + L \frac{di(t)}{dt} + V_0 = 0$$


$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{i(t)}{LC} = 0$$

The Natural Response of a Parallel/Series RLC

$$v(t) = Ae^{st} \Leftarrow \text{parallel}$$

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0 \Rightarrow$$

$$s = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$i(t) = Ae^{st} \Leftarrow \text{series}$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \Rightarrow$$

$$s = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

The Natural Response of a Parallel/Series RLC

There are 3 distinct cases.

Let

Neper frequency $\alpha = \frac{1}{2RC}$ or $\alpha = \frac{R}{2L}$

Then,

Resonant radian frequency $\omega_0 = \frac{1}{\sqrt{LC}}$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

1) $\alpha = \omega_0$ Critically-damped

2) $\alpha < \omega_0$ Under-damped

3) $\alpha > \omega_0$ Over-damped

The Natural Response of a Parallel RLC

There are 3 distinct cases.

$$1) \alpha = \omega_0 \Rightarrow s_1 = s_2 = -\alpha$$

Critically-damped

$$2) \alpha < \omega_0 \Rightarrow \begin{cases} s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} \\ s_2 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2} \end{cases}$$

Under-damped

$$3) \alpha > \omega_0 \Rightarrow \begin{cases} s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \end{cases}$$

Over-damped

The Natural Response of a Parallel/Series RLC

How does the response look like?

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \Leftarrow \text{parallel}$$

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \Leftarrow \text{series}$$



Initial conditions must be used
to evaluate

How do we solve for the unknowns for over-damped (parallel)?

$$v(0^+) = A_1 + A_2$$

Two equations with two unknowns

$$\frac{dv(0^+)}{dt} = A_1 s_1 + A_2 s_2 \Rightarrow$$

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{1}{C} \left[-\frac{v(0^+)}{R} - I_0 \right]$$

Initial voltage across the capacitor

Initial current through the inductor

How do we solve for the unknowns for the over-damped case(series)?

$$i(0^+) = A_1 + A_2$$

Two equations with two unknowns


$$\frac{di(0^+)}{dt} = A_1 s_1 + A_2 s_2 \Rightarrow$$

$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{1}{L} [-Ri(0^+) - V_0]$$


Initial current through the inductor

Initial voltage across the capacitor

Example 8.9

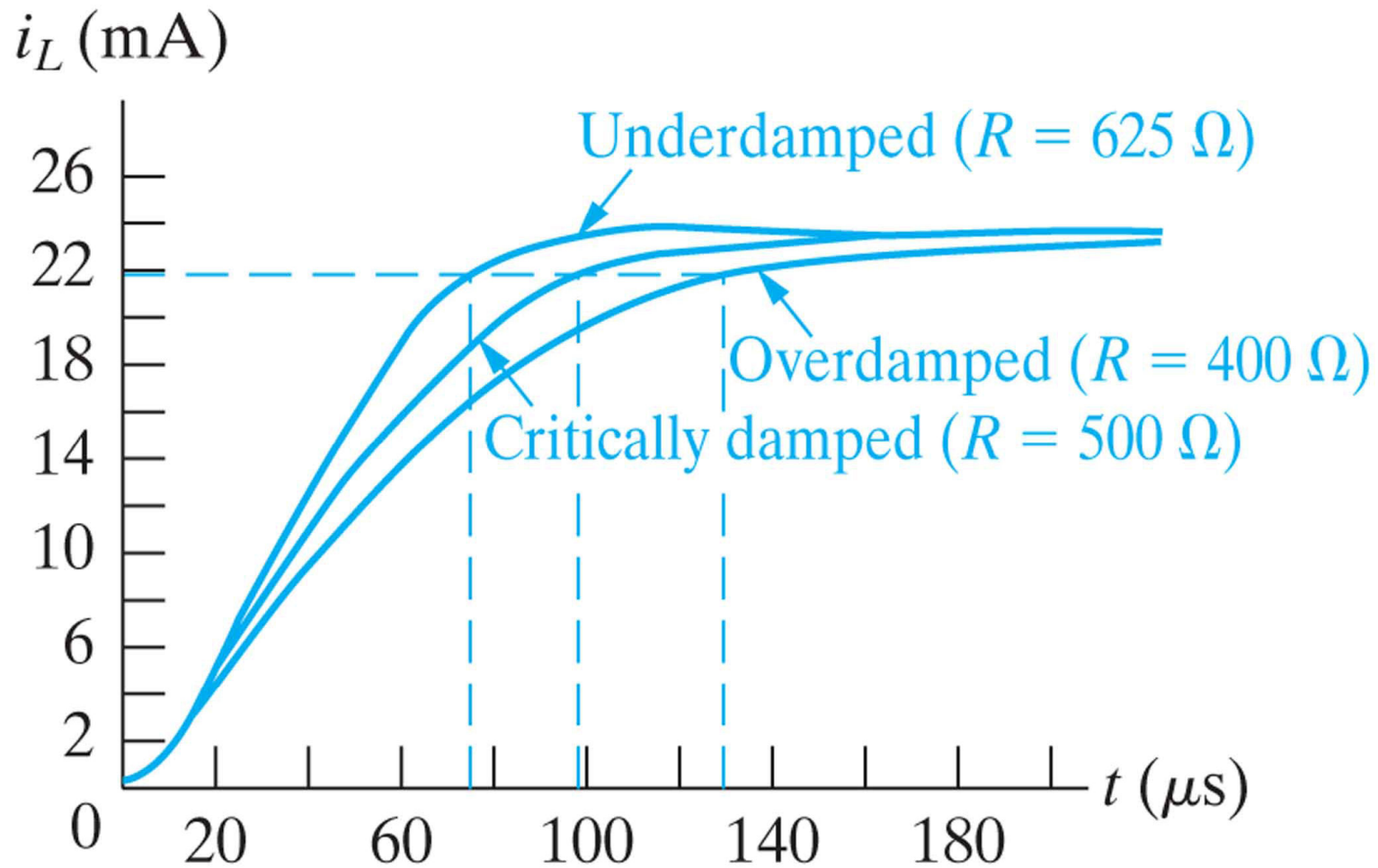

The circuit for Example 8.2.

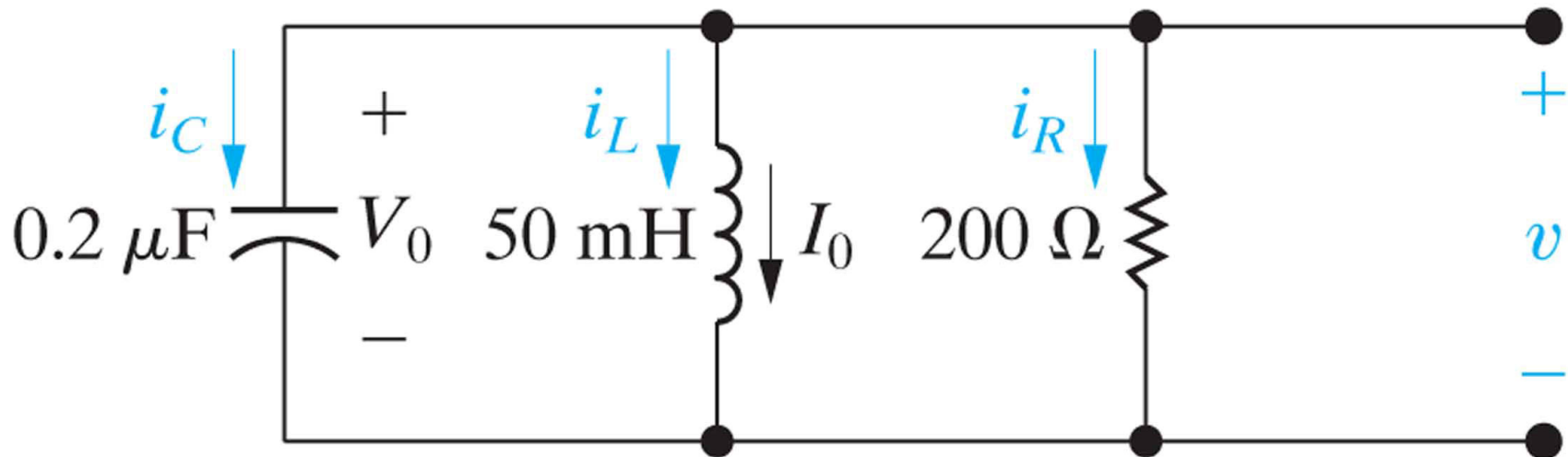


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

$$I_0 = 30 \text{ mA};$$

$$v(0^+) = 12$$

Figure 8.7 Example 8.2.

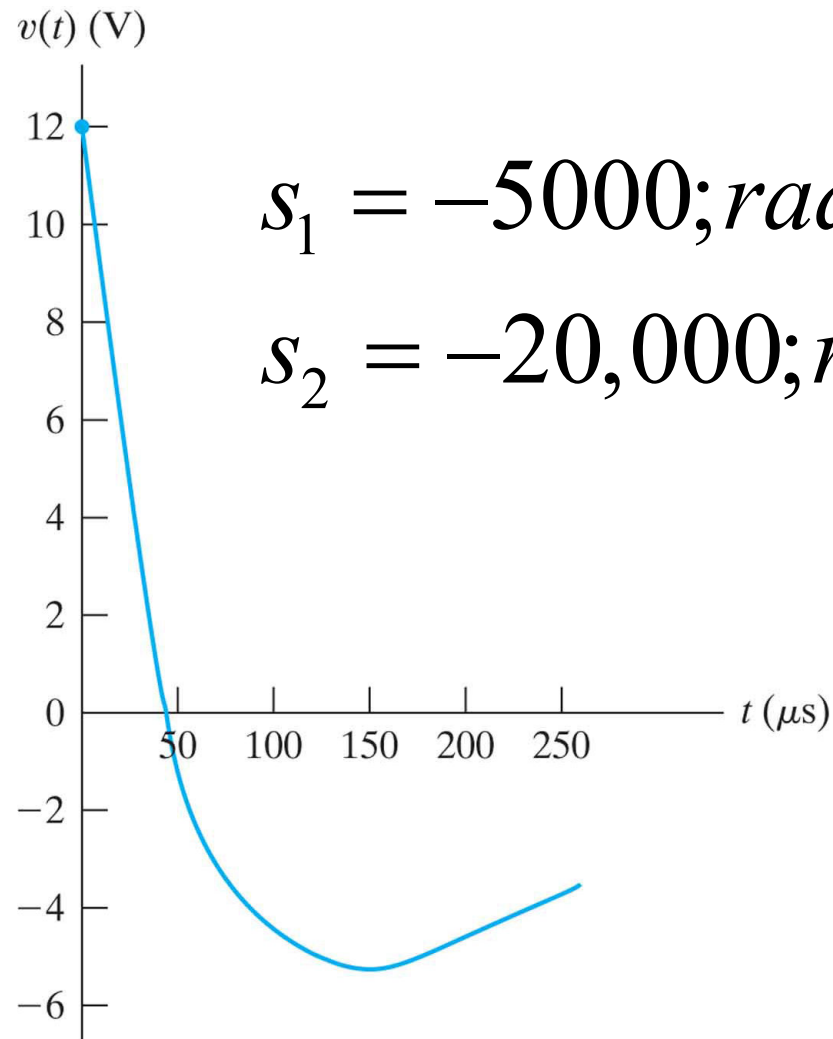

$$s_1 = -5000; rad/sec$$

$$s_2 = -20,000; rad/sec$$

The Natural Response of an under-damped Parallel/Series RLC

How does the response look like?

$$v(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t) \Leftarrow \text{parallel}$$

$$i(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t) \Leftarrow \text{series}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$



Initial conditions must be used
to evaluate

How do we solve for the unknowns for under-damped (parallel)?

$$v(0^+) = B_1$$

$$\frac{dv(0^+)}{dt} = \omega_d B_2 - \alpha B_1 \Rightarrow$$

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{1}{C} \left[-\frac{v(0^+)}{R} - I_0 \right]$$

Two equations with two unknowns

Initial voltage across the capacitor

Initial current through the inductor

How do we solve for the unknowns for under-damped (series)?

$$i(0^+) = B_1$$

$$\frac{di(0^+)}{dt} = \omega_d B_2 - \alpha B_1 \Rightarrow$$


$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{1}{L} [-Ri(0^+) - V_0]$$

Two equations with two unknowns

Initial current through the inductor

Initial voltage across the capacitor

The circuit for Example 8.4

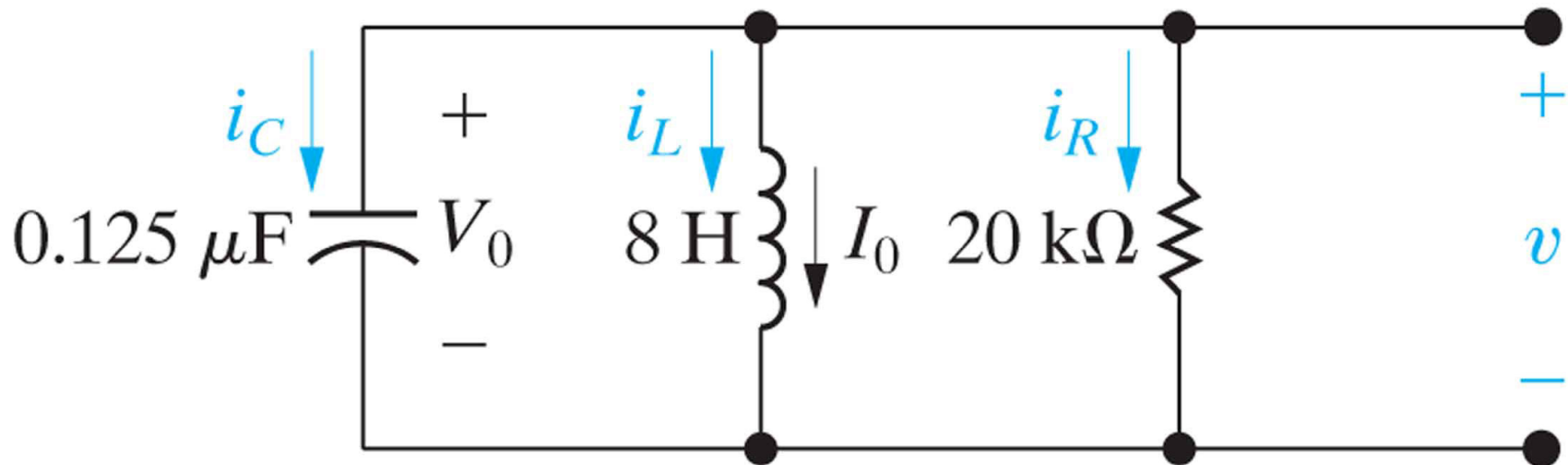


Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

$$I_0 = -12.25 \text{ mA};$$

$$v(0^+) = 0$$

The voltage response for Example 8.4

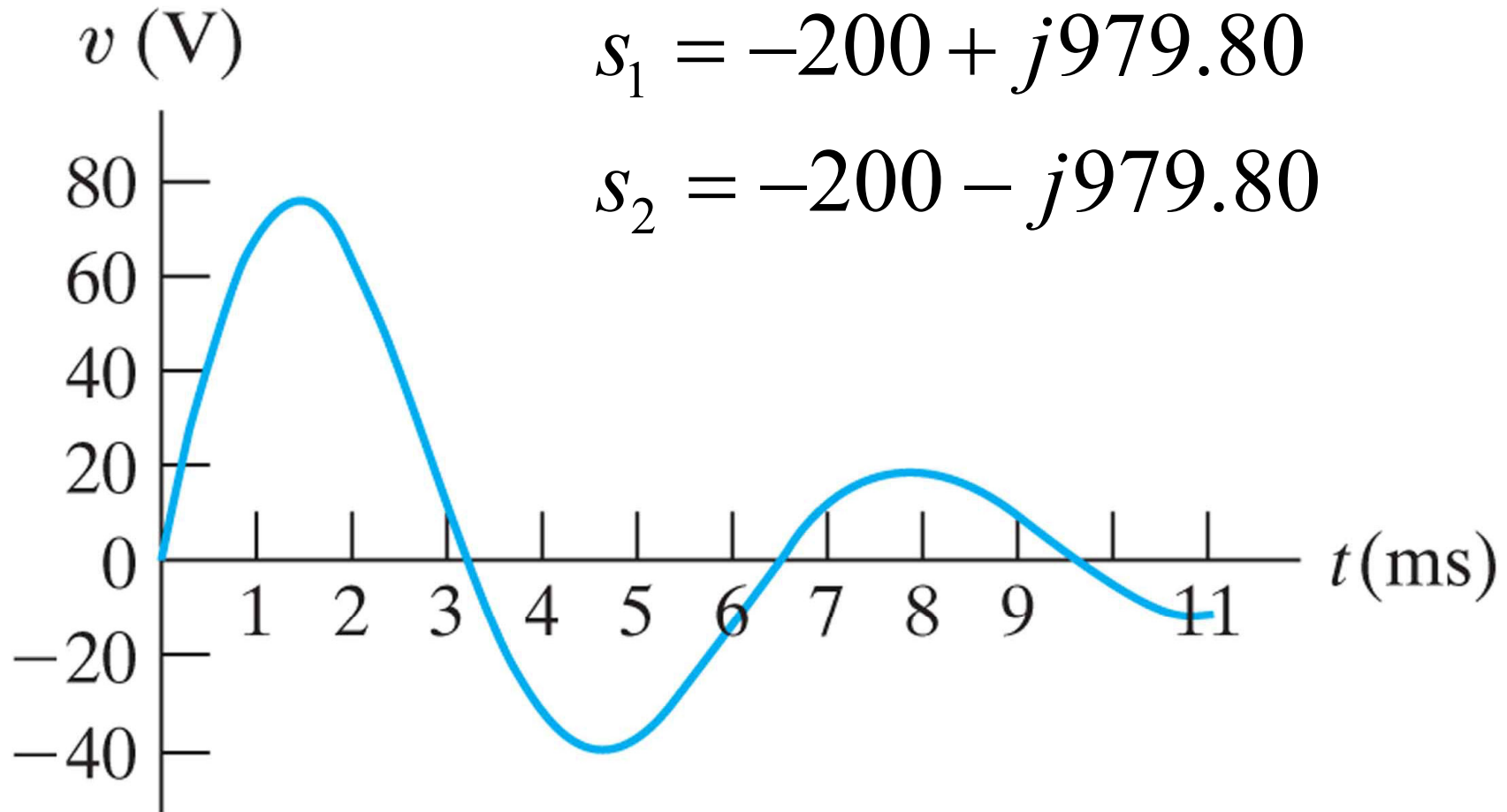

The Natural Response of a Critically Damped Parallel/Series RLC

How does the response look like? $s_1 = s_2 = s$

$$v(t) = D_1 t e^{st} + D_2 e^{st}$$



Initial conditions must be used
to evaluate

How do we solve for the unknowns for critically-damped (parallel)?

$$v(0^+) = D_2$$

$$\frac{dv(0^+)}{dt} = D_1 - \alpha D_2 \Rightarrow$$

$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{1}{C} \left[-\frac{v(0^+)}{R} - I_0 \right]$$

Two equations with two unknowns

Initial voltage across the capacitor

Initial current through the inductor

How do we solve for the unknowns for the critically-damped (series)?

$$i(0^+) = D_2$$

Two equations with two unknowns


$$\frac{di(0^+)}{dt} = D_1 - \alpha D_2 \Rightarrow$$

$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{1}{L} [-Ri(0^+) - V_0]$$


Initial current through the inductor

Initial voltage across the capacitor

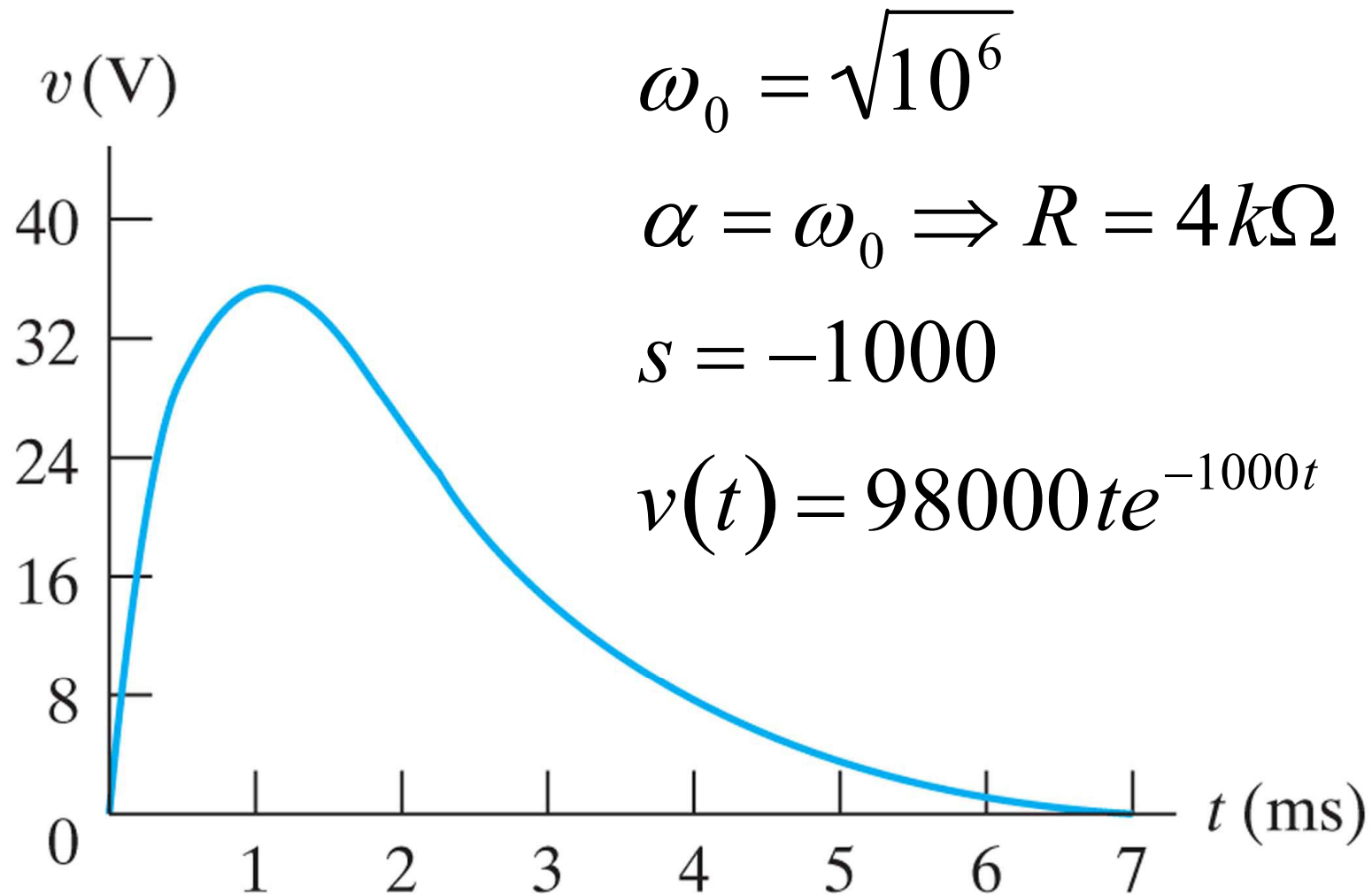Example 8.5 (critically-damped)-R has been changed to make this happen



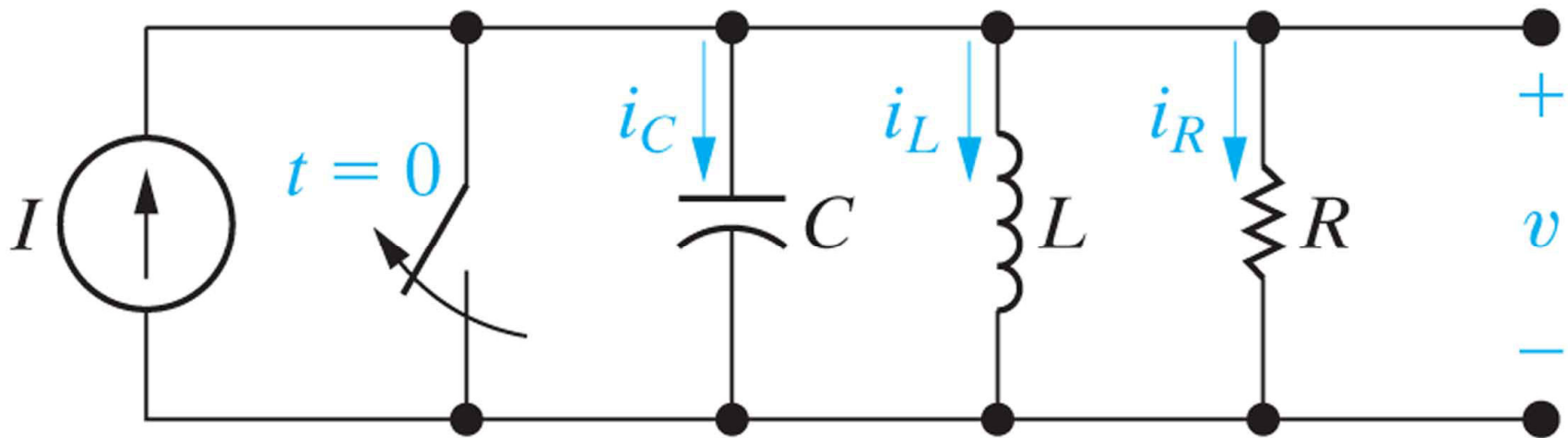A circuit used to describe the step response of a parallel *RLC* circuit



The Step Response of a Parallel RLC

1. Using KCL,

$$\frac{v_L(t)}{R} + i_L(t) + C \frac{dv_L(t)}{dt} = I$$

$$\frac{L}{R} \frac{di_L(t)}{dt} + i_L(t) + LC \frac{d^2 i_L(t)}{dt^2} = I$$

$$\frac{d^2 i_L(t)}{dt^2} + \frac{1}{RC} \frac{di_L(t)}{dt} + \frac{1}{LC} i_L(t) = \frac{I}{LC}$$

The Step Response of a Parallel RLC (direct method)

1. First find the natural response
2. Add to the natural response the final value
3. Use the initial conditions to solve for coefficients

$$\frac{d^2 i_{L,n}(t)}{dt^2} + \frac{1}{RC} \frac{di_{L,n}(t)}{dt} + \frac{1}{LC} i_{L,n}(t) = 0$$

$$i_L(t) = I_f + i_{L,n}(t)$$

The Step Response of a Parallel RLC (direct method)


$$i_L(0^+) \frac{di_L(0^+)}{dt} \Leftarrow \text{known}$$

$$i_L(t) = I_f + A_1' e^{s_1 t} + A_2' e^{s_2 t}$$

$$i_L(t) = I_f + B_1' e^{-\alpha t} \cos(\omega_d t) + B_2' e^{-\alpha t} \sin(\omega_d t)$$

$$i_L(t) = I_f + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t}$$

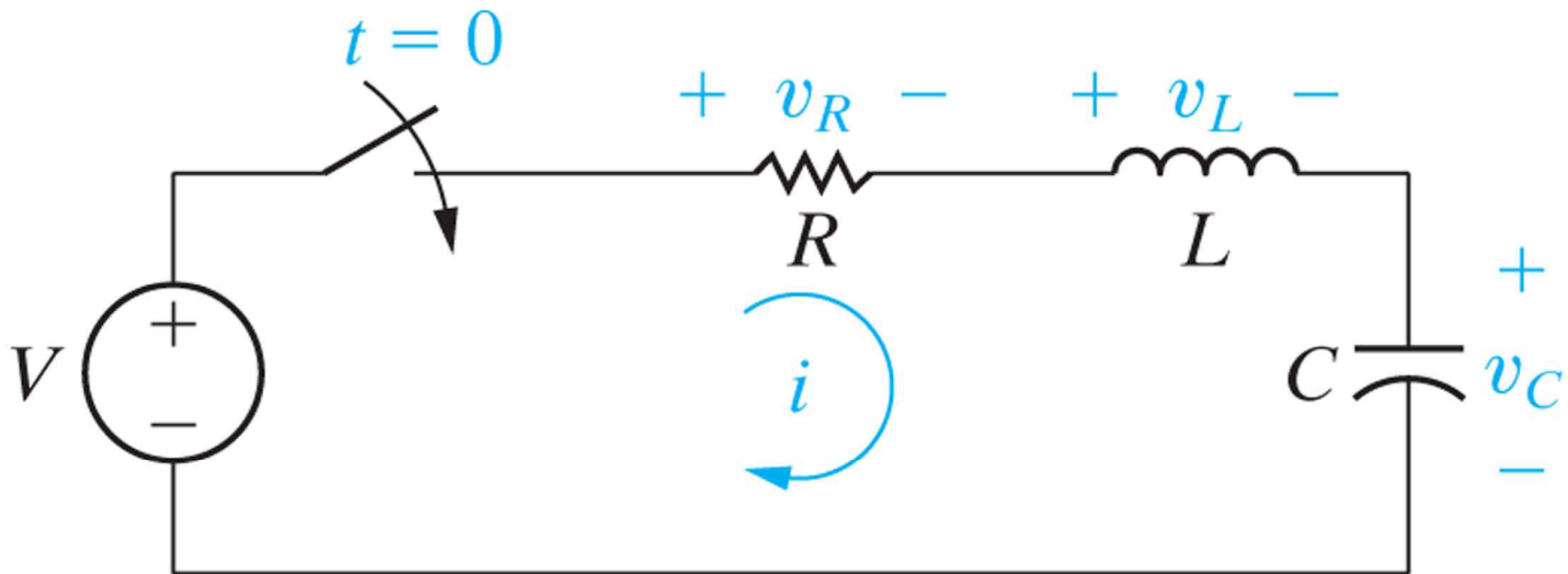A circuit used to illustrate the step response of a series *RLC* circuit.



The Step Response of a Series RLC

1. Using KVL,

$$RC \frac{dv_c(t)}{dt} + v_c(t) + LC \frac{d^2 v_c(t)}{dt^2} = V$$

$$L \frac{di_L(t)}{dt} + Ri_L(t) + \frac{1}{C} \int^t i_L(t') dt' = V$$

$$\frac{d^2 v_c(t)}{dt^2} + \frac{R}{L} \frac{dv_c(t)}{dt} + \frac{1}{LC} v_c(t) = \frac{V}{LC}$$

The Step Response of a Series RLC (direct method)

$$v_c(0^+) \frac{dv_c(0^+)}{dt} \Leftarrow \text{known}$$

$$v_c(t) = V_f + A_1' e^{s_1 t} + A_2' e^{s_2 t}$$

$$v_c(t) = V_f + B_1' e^{-\alpha t} \cos(\omega_d t) + B_2' e^{-\alpha t} \sin(\omega_d t)$$


$$v_c(t) = V_f + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t}$$

The circuit for Example 8.12


$$v_c(0^+) = 0, \frac{dv_c(0^+)}{dt} = 0$$

$$v_c(t) = 48 + B_1' e^{-\alpha t} \cos(\omega_d t) + B_2' e^{-\alpha t} \sin(\omega_d t)$$

$$\alpha = -1400; \omega_d = 4800$$

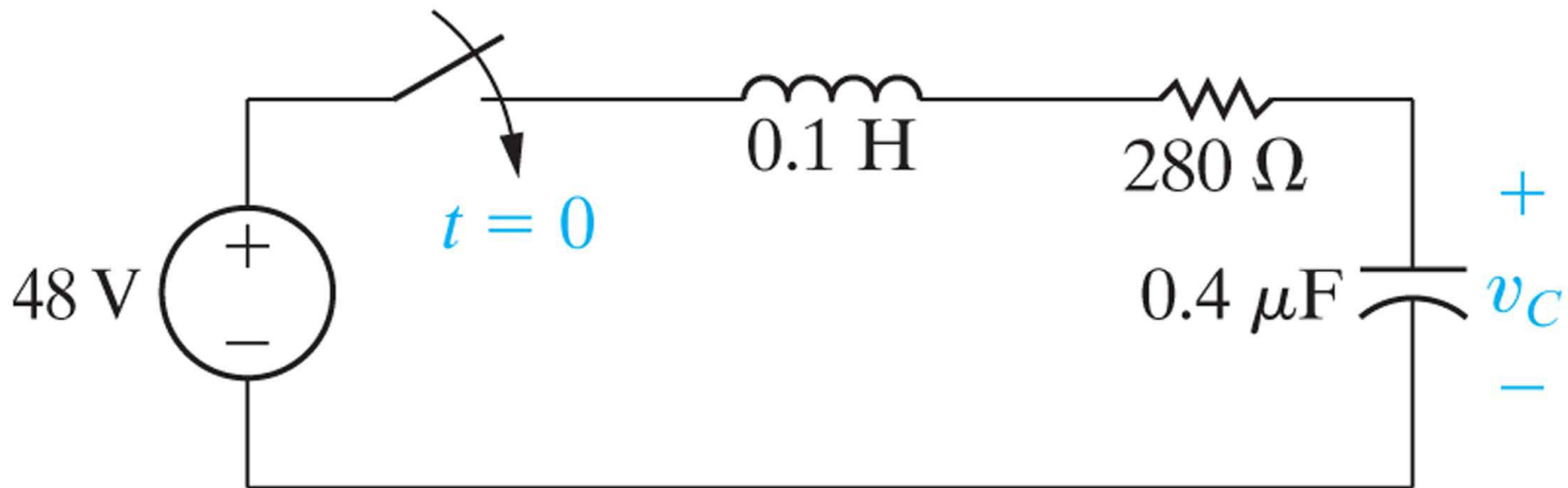

Second order circuits with op amps

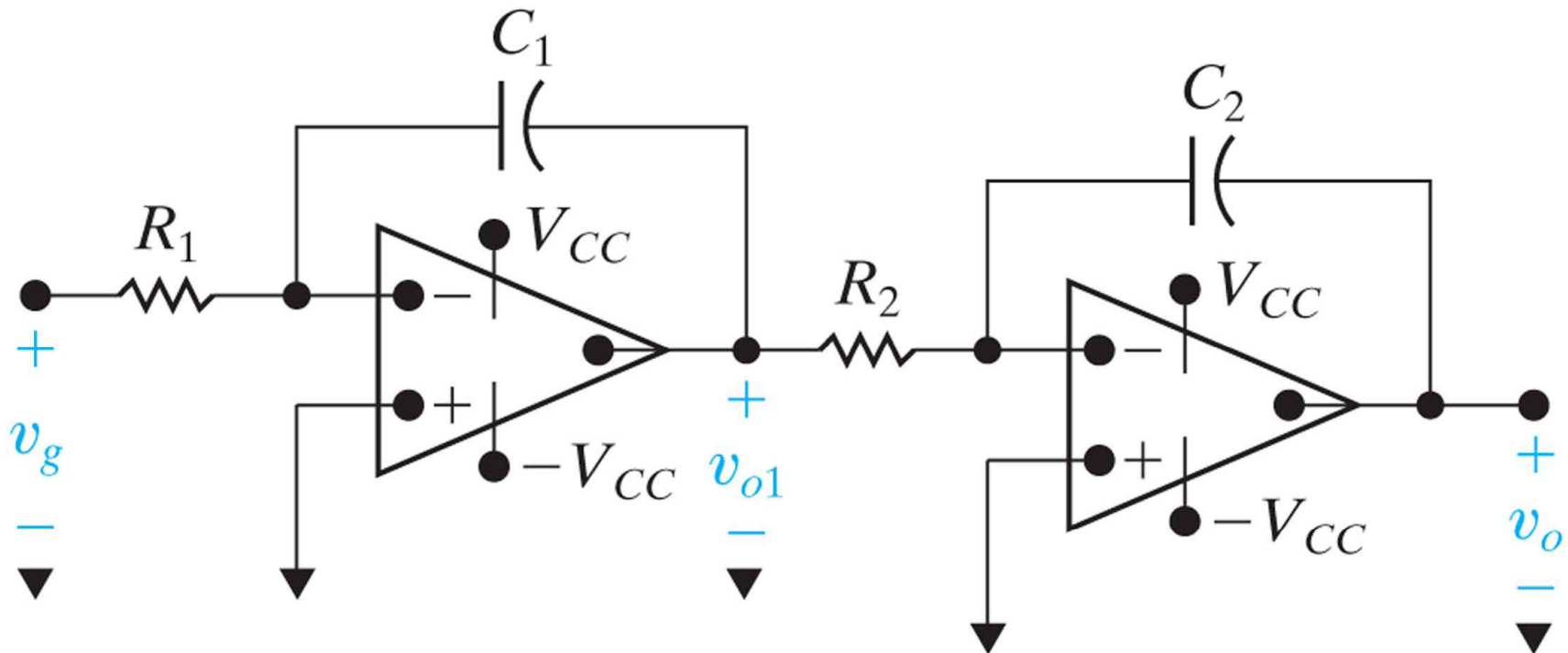

Copyright © 2011 Pearson Education, Inc. publishing as Prentice Hall

$$\frac{d^2 v_o(t)}{dt^2} = \frac{1}{R_1 C_1} \frac{1}{R_2 C_2} v_g(t)$$


Second order circuits with op amps

- This is a variation of the second order system
- The output is the double integration of the input
- Depending on the initial charges on the capacitors, the response will vary
- For a constant input, the output will increase indefinitely


$$\frac{d^2 v_0(t)}{dt^2} = \frac{1}{R_1 C_1} \frac{1}{R_2 C_2} v_g(t)$$

$$v_g(t) = V_0$$

Trouble
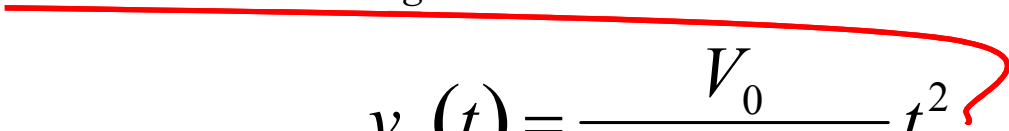
$$v_0(t) = \frac{V_0}{2R_1 C_1 R_2 C_2} t^2$$

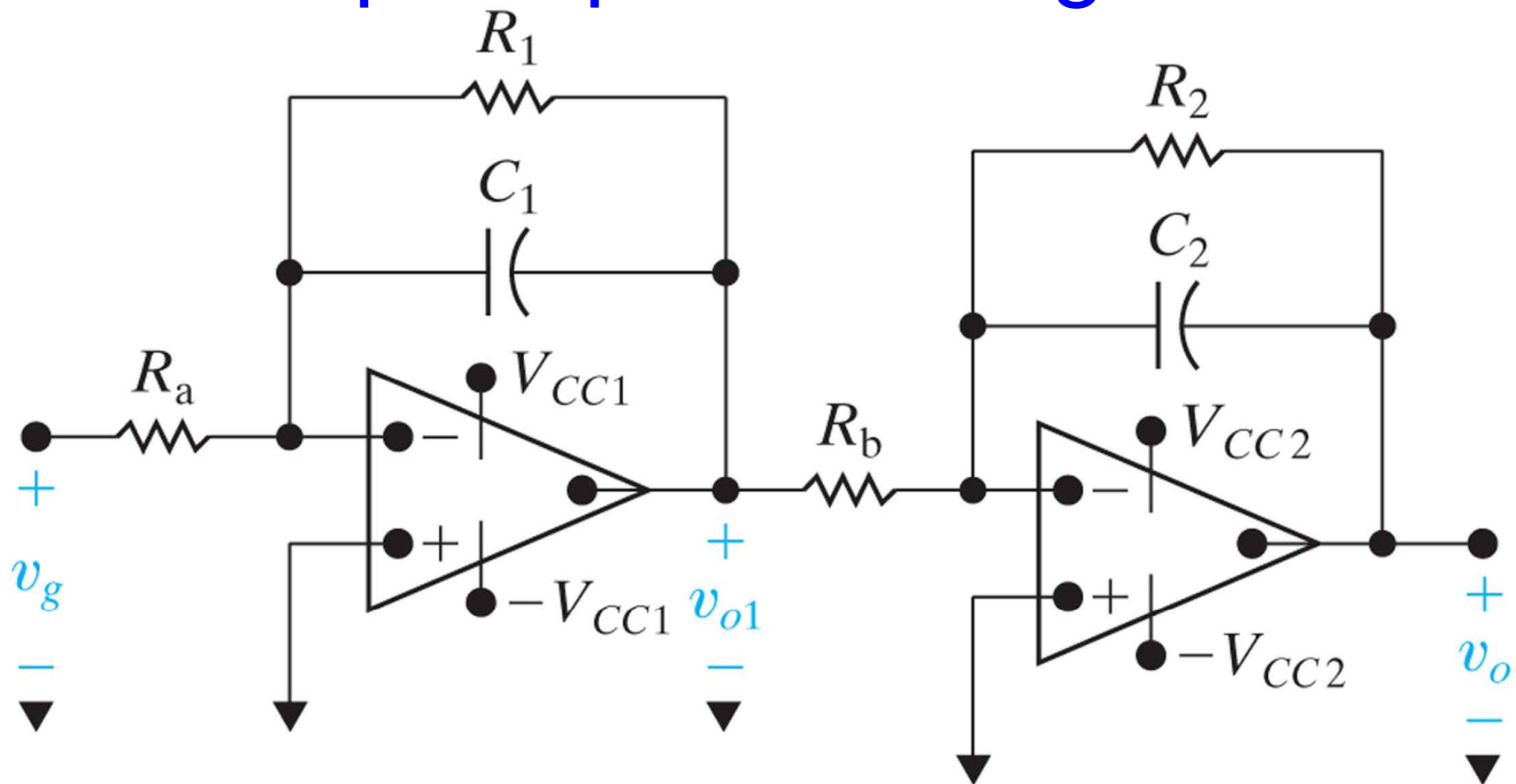
Second order circuits with op amps-imperfect integrator



$$v_{01}(t) = -R_b C_2 \frac{dv_0(t)}{dt} - \frac{R_b C_2}{\tau_2} v_0(t)$$

$$v_g(t) = -R_a C_1 \frac{dv_{01}(t)}{dt} - \frac{R_a C_1}{\tau_1} v_{01}(t)$$

$$\tau_1 = R_1 C_1; \tau_2 = R_2 C_2$$

$$\frac{d^2 v_0(t)}{dt^2} + \left(\frac{1}{\tau_1} + \frac{1}{\tau_2} \right) \frac{dv_0(t)}{dt} + \left(\frac{1}{\tau_1 \tau_2} \right) v_0(t) = \frac{v_g(t)}{R_a C_1 R_b C_2}$$

$$s_1 = \frac{-1}{\tau_1}; s_2 = \frac{-1}{\tau_2}$$

$$v_g(t) = V_0 U(t)$$

$$v_0(t) = V_f + A_1 e^{s_1 t} + A_2 e^{s_2 t} \Leftrightarrow v_0(0^+) = \frac{dv_0(0^+)}{dt} = 0$$

$$V_f = \frac{V_0 \tau_1 \tau_2}{R_a C_1 R_b C_2} = \frac{R_1 R_2 V_0}{R_a R_b}$$

If it is less than the supply voltage