

# Topic: Ohm meter



ohm meter: It is used for measure the medium resistance

Medium resistance value —  $1\text{ohm} - 100\text{ohm}$

There are two types of ohmmeter

Series type ohmmeter

Parallel (Shunt) type ohmmeter

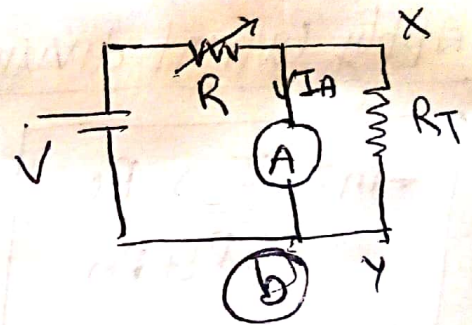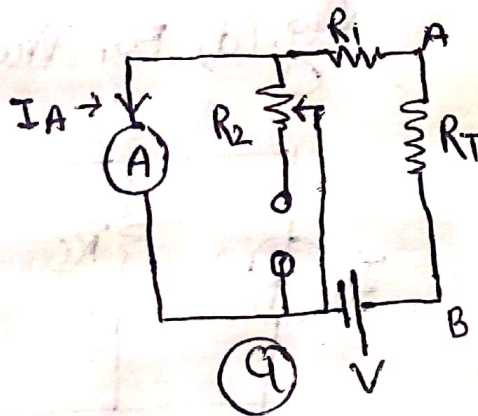

Where, (A)  $\rightarrow$  Ammeter

DC Source  $\rightarrow V \rightarrow$  Battery (Fixed)

$R_T \rightarrow$  Test resistance

$I_A \rightarrow$  Current

$R_2 \rightarrow$  Variable resistance

$R_1 \rightarrow$  Limiting resistance to control burning

Where,




$V \rightarrow$  DC Source

$R_T \rightarrow$  Test resistance

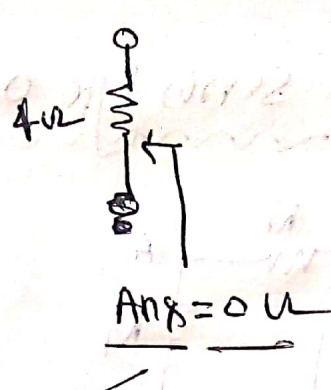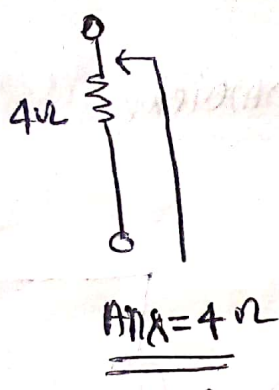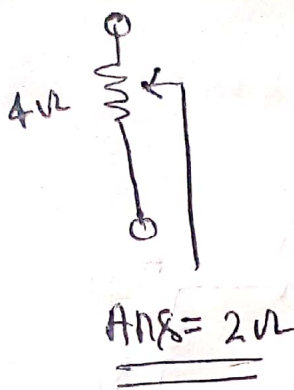(A)  $\rightarrow$  Ammeter

$R \rightarrow$  Variable resistance

Note: Battery (V), Ammeter (A) and  $R_1$  (limiting resistance) are connected in series. Hence, it called series type ohm meter




Concept of Potentiometer


It is used to measure the variable resistance.

Sometimes it is also represented by in this way

(a)

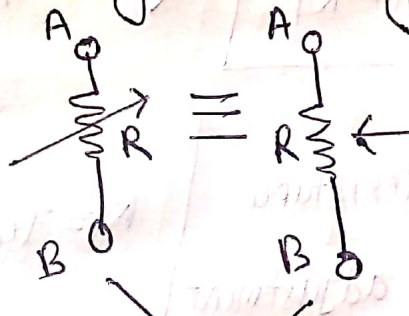

(b)

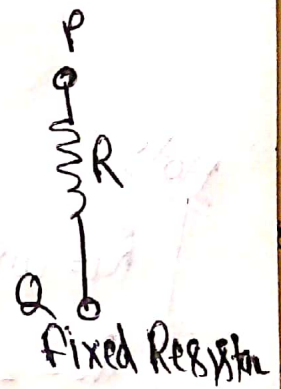


Both are behaves like variable resistance.

Note: (a) When Ammeter (A) is connected <sup>in series</sup> with test resistance ( $R_T$ ). This is named as series type ohm meter as shown in Fig. (a)

(b) When Ammeter (A) is connected with test in parallel with test resistance ( $R_T$ ). This is called as parallel type or shunt type ohm meter as shown in Fig. (b)



# working of series type ohmmeter

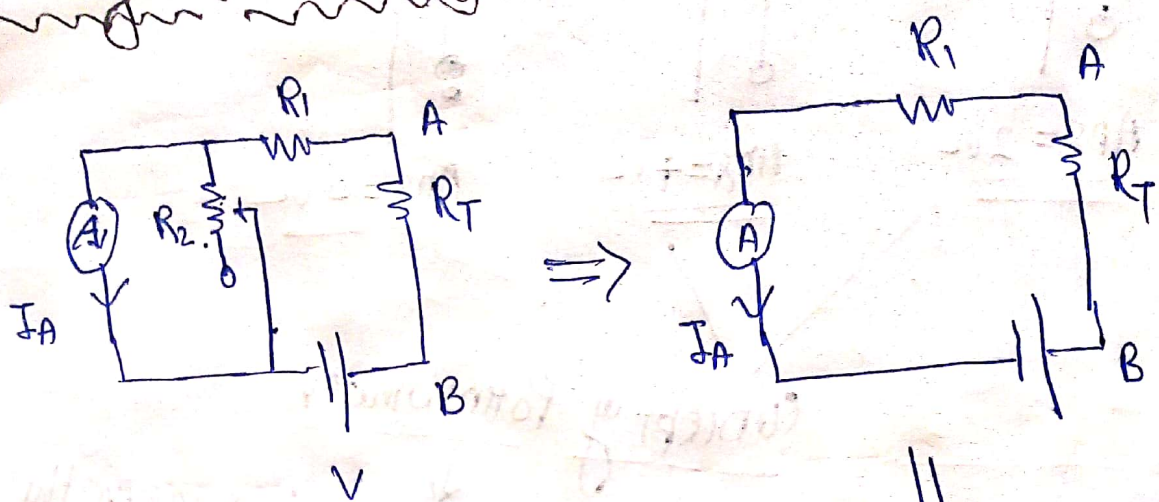

$$I_A = \frac{V}{R_1 + R_T}$$

Note

$R_1$  = current limiting resistance

$R_2$  = Zero resistance adjustment

$R_T$  = Test resistance

① Ammeter is used here to measure the current.


② if no current flow in the circuit, the deflection will be zero

③ if current start to flow, in the circuit, the deflection will be happened.
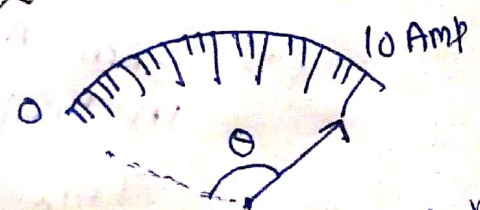
# what is the meaning of deflection



$I = 0$  i.e. deflection = 0 or movement = 0




$I = 10 \text{ Amp}$   
max<sup>m</sup> deflection

i.e. Deflection  $\propto$  Current

$$\boxed{\theta \propto I} \quad \text{or} \quad \theta = KI$$

$$\text{if } \theta = 0 \quad I = 0$$
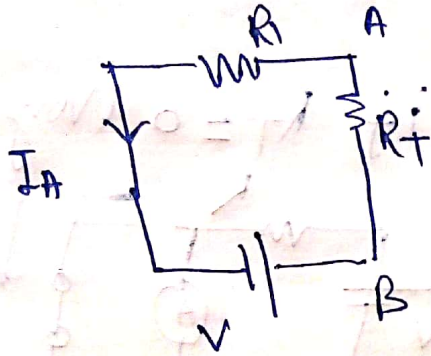
$$\text{if } \theta \neq 0 \quad I \neq 0$$






$$\boxed{I = \frac{V}{R + R_T}}$$

Case-1 if  $R_T = 0$ ;  $I_A = \frac{V}{R + 0} = \frac{V}{R}$

i.e.  $I \rightarrow \text{increases} \{ I_{\text{max flow}} \}$


Case-2 if  $R_T \rightarrow \infty$ ;  $I_A = \frac{V}{R + \infty} = 0$

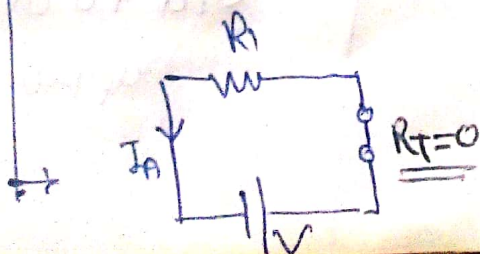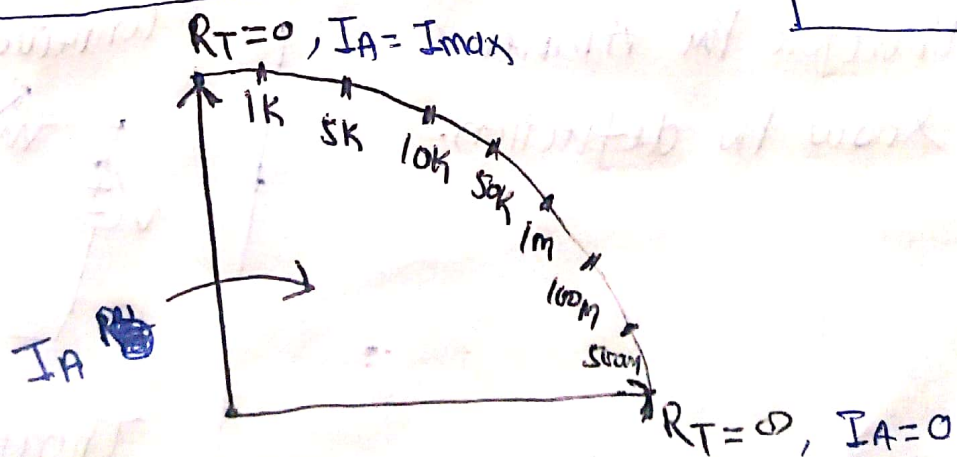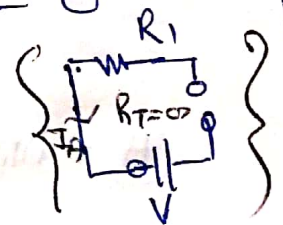i.e.  $I \rightarrow \text{decreases} \rightarrow 0$




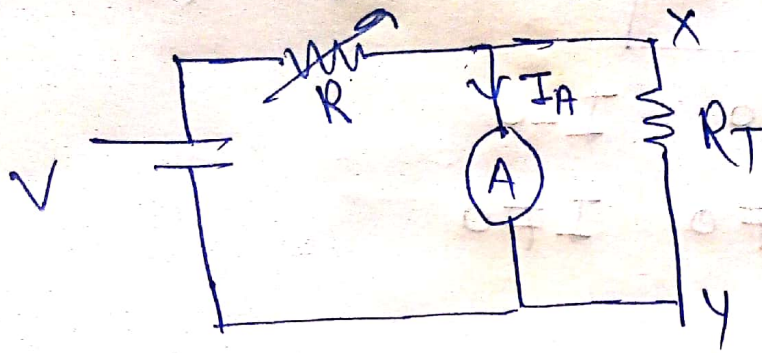
# Working Operation of Parallel type ohmmeter




if  $R_T = \infty$



$$I_A = \frac{V}{R}$$


Ⓐ Ammeter show the current  
Therefore the Ammeter  
show the deflection.

if  $R_T = 0$  (Very small value)

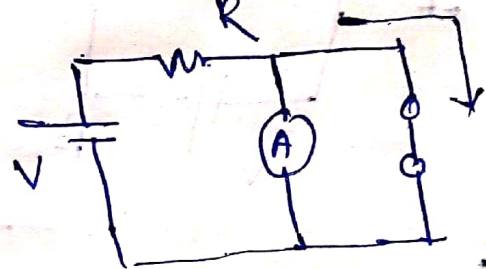


$$I_A = 0$$

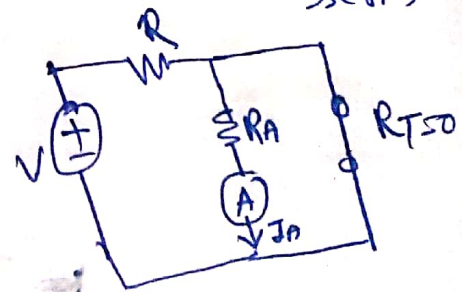Since Ⓐ Ammeter  
having internal  
resistance which is  
connected in ~~parallel~~ series



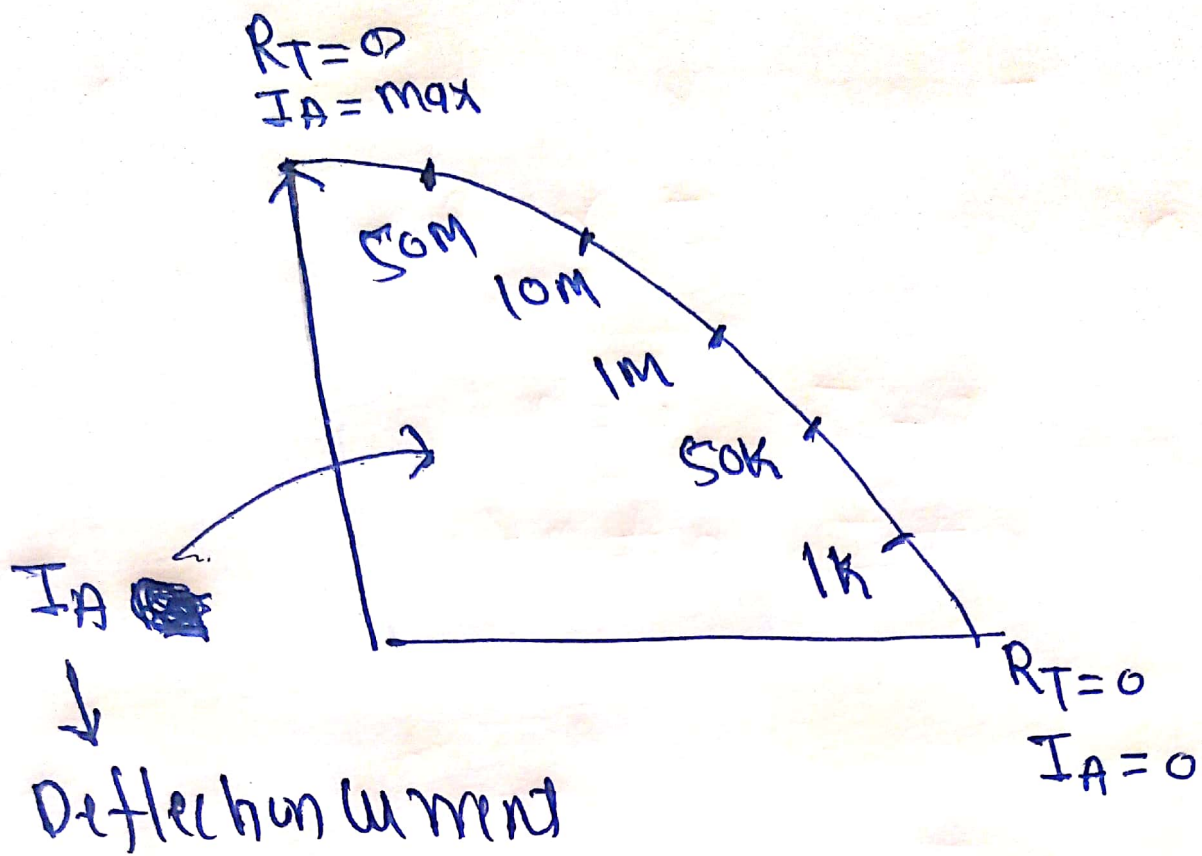Therefore  $I_A = 0$   
and no deflection  
happen



$\theta \propto I_A$

$Q = K I_A$