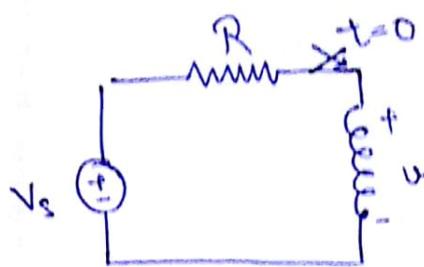


Step Response of RL circuit



Let the response of the circuit be the sum of transient response & steady state response

$$i = i_t + i_{ss} \quad \text{--- (1)}$$

The transient response is a decaying exponential

$$i_t = A e^{-t/\tau} \quad \text{--- (2)} \quad \text{where } \tau = \frac{L}{R}$$

Now during steady state, inductor is going to behave like short-circuit \therefore Voltage is zero

$$\therefore i_{ss} = \frac{V_s}{R} \quad \text{--- (3)}$$

so in eqⁿ (1)

$$i = A e^{-\frac{t}{\tau}} + \frac{V_s}{R} \quad \text{--- (4)}$$

Finding the value of A

Let I_0 be the initial current through the inductor

$$\therefore i_0 = i_{st} = I_0$$

Now at time $t=0$

$$I_0 = A + \frac{V_s}{R}$$

$$\therefore A = I_0 - \frac{V_s}{R}$$


Substituting value of A in eqⁿ (4)

$$\boxed{\therefore i = \left(I_0 - \frac{V_s}{R} \right) e^{-t/\tau} + \frac{V_s}{R}}$$

$$\dot{i}(t) = [i(0) - i(\infty)] e^{-t/\tau} + i(\infty)$$

general eqn

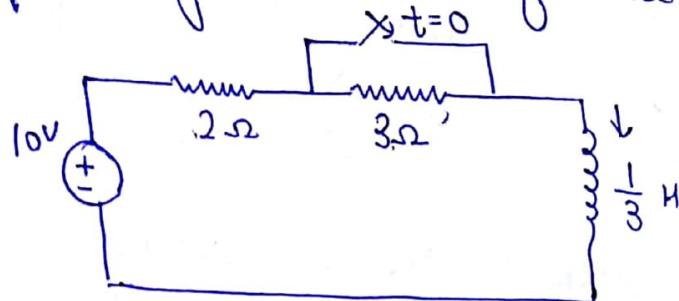Eg. Find $\dot{i}(t)$ for $t > 0$. Assume the switch is closed for long duration of time.





$$\dot{i}(t) = [i(0) - i(\infty)] e^{-t/\tau} + i(\infty)$$

At $t = 0$

$$\dot{i}(t) = \frac{V_0}{R} =$$

$$i(\infty) = \frac{10}{2} = 5 \text{ A}$$

for $t < 0$

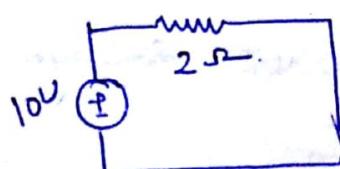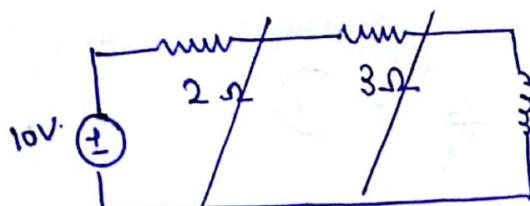


$$\therefore i = 5 \text{ A}$$

The current through the inductor at $t = 0^-$

$$i(0^-) = 5 \text{ A}$$

$$i(0^-) = i(0^+) = 5 \text{ A}$$

Now for $t > 0$

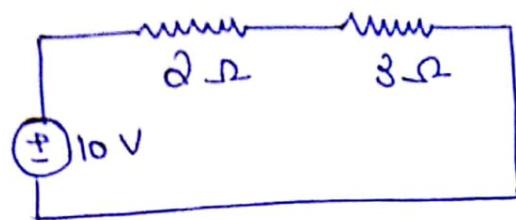

$$i = \frac{10}{5} = 2 \text{ A}$$

$$i(\infty) = 2 \text{ A}$$

$$\begin{aligned} i(t) &= (5 - 2)e^{-t/\tau} + 2 \\ &= 3e^{-t/\tau} + 2 \end{aligned}$$

$$\tau = \frac{L}{R}$$

$$R_{TH} = 5 \Omega$$

$$\therefore \tau = \frac{1}{15} \text{ s}$$


$$\therefore i(t) = 3 e^{-15t} + 2 \text{ A}$$

Initial & final currents

for capacitor,
 $v(0^+) = v(0^-)$

for inductor,

$$i(0^+) = i(0^-)$$

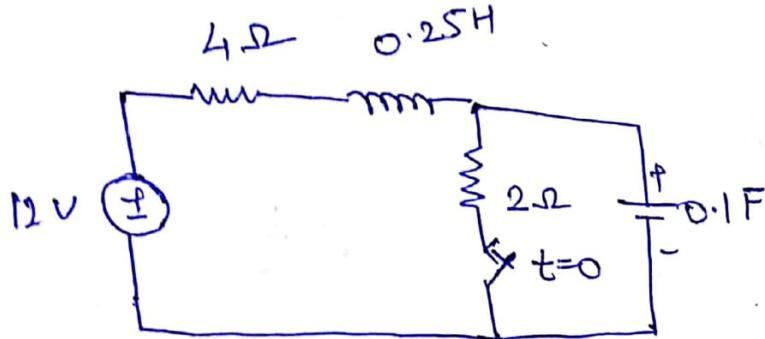


- Switch has been closed for a long time and
- it is opened at $t=0$. Find $i(0^+), v(0^+)$

$$\frac{di(0^+)}{dt}, \frac{dv(0^+)}{dt}, i(\infty), v(\infty)$$

Ans.

As the switch was closed for long time

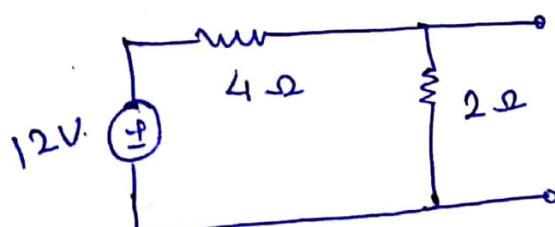

$$\therefore i(0^-) = \frac{12}{6} = 2 \text{ A}$$

a) $\therefore v(0^-) = 4 \text{ V}$ (across 2 ohm)

$$i(0^+) = i(0^-) = 2 \text{ A}$$

$$v(0^+) = v(0^-) = 4 \text{ V}$$

b) at time $t=0^+$ (switch is open)

$$i_c(0^+) = 2 \text{ A}$$


$$\frac{dV}{dt} = i_c$$

$$\frac{dV(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{2}{0.1} = 20 \text{ V/s}$$

Similarly we know,

$$\frac{L \frac{di}{dt}}{dt} = v_L$$
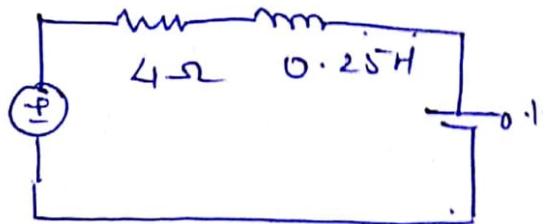
$$\frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L}$$



Now to obtain voltage across inductor, applying KVL.


$$12 - 4i(0^+) - v_L(0^+) - v_c(0^+) = 0$$

$$\therefore v_L(0^+) = 0$$

$$\therefore \frac{di(0^+)}{dt} = 0$$

c) $i(\infty) = 0$

$$v(\infty) = 12$$

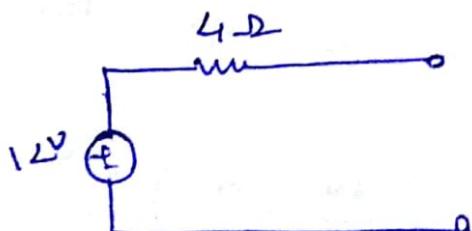

$i(\infty) \rightarrow$ across inductor
 $v(\infty) \rightarrow$ across capacitor

* The response of first order circuit to a non constant source:

The general form of RL & RC circuit is represented by

$$\frac{dx(t)}{dt} + ax(t) = y(t) \quad (1)$$

where, $y(t)$ is a const. for a const. voltage or current source and $a = \frac{1}{T}$ the reciprocal of time const.

To make LHS a perfect derivative we use a method called as (IF method).

Let us consider, a derivative of product of two terms.

$$\frac{d(xe^{at})}{dt} = \frac{du e^{at}}{dt} + aue^{at}$$

$$\frac{d(xe^{at})}{dt} = e^{at} \left(\frac{du}{dt} + au \right) \rightarrow (2)$$

RHS of eqⁿ (2) is same as LHS of eqⁿ (1)

\therefore multiplying e^{at} on both the sides then LHS can be represented by the perfect derivative, $\frac{d(e^{at}x)}{dt}$

$$\left(\frac{du}{dt} + au \right) e^{at} = ye^{at}$$

Integrating both the sides we have

$$xe^{at} = \int ye^{at} dt + k \quad (3)$$

where, k is a const.

Solving for $x(t)$, multiply by e^{-at} on both sides
of eqⁿ ③

$$x = e^{-at} \int y e^{at} dt + k e^{-at}$$

where $y(t)$ is source can be represented by M

$$x = M e^{-at} \int e^{at} dt + k e^{-at}$$

$$\boxed{x = \frac{M}{a} + k e^{-at}}$$

$$\boxed{x = x_f + x_n}$$

forced
response

Natural
response

Natural response
forced response

$$x_n = k e^{-at}$$

$$x_f = e^{-at} \int y(t) e^{at} dt$$

If $y(t)$ is exponential function then

$$y(t) = e^{bt} \quad \& \quad a+b \neq 0$$

$$\begin{aligned} x_f &= e^{-at} \int e^{bt} e^{at} dt \\ &= e^{-at} \int e^{(a+b)t} dt \\ &= \frac{1}{a+b} e^{at} e^{(a+b)t} \end{aligned}$$

$$\boxed{x_f = \frac{1}{a+b} e^{bt}}$$


Forced response of a forcing function

Forcing function
 $y(t)$

forced response
 $v_f(t)$


- ① Constant $y(t) = M$ $v_f = H$ a const.
- ② Exponential $y(t) = M e^{bt}$ $v_f = M e^{bt}$
- ③ Sinusoidal
 $y(t) = M \sin(\omega t + \theta)$ $v_f = A \sin(\omega t + \theta) + B \cos(\omega t + \theta)$

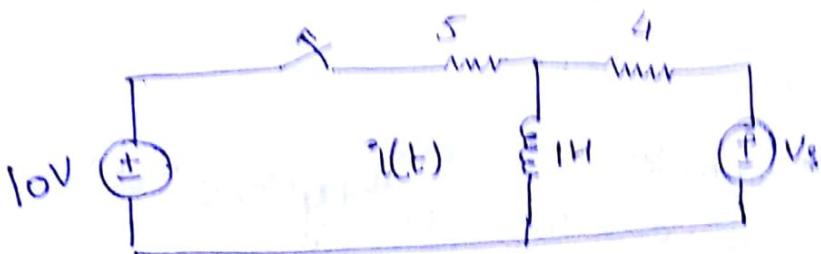Ex. Find the current i for the circuit shown
Resonance for $t > 0$ when the value of $V_s(t) = 10e^{-2t}$



Since the forcing function is an exponential
so the forced response shall be of the form
 $v_f = B e^{-2t} \quad \text{--- (1)}$

for $t > 0$ with working KVL.

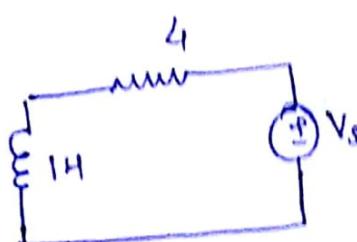

$$V_s - 4v_f - v_L = 0$$

$$10e^{-2t} - 4v_f - v_L = 0$$

$$L \frac{di}{dt} + 4v_f = 10e^{-2t} \quad \text{--- (1)}$$

Forced response of a forcing function

Forcing function
 $y(t)$

- ① Constant $y(t) = M$
- ② Exponential $y(t) = M e^{-bt}$
- ③ Sinusoidal
 $y(t) = M \sin(\omega t + \theta)$


forced response
 $x_f(t)$

$$x_f = N \text{ a const.}$$

$$x_f = N e^{-bt}$$


$$x_f = A \sin \omega t + B \cos \omega t$$

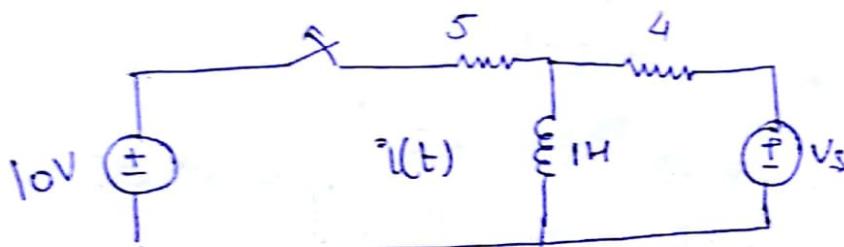Ex. Find the current i for the circuit shown here for $t > 0$ when the value of $V_s(t) = 10e^{-2t}$



Since the forcing function is an exponential, the forced response shall be of the form.
 $i_f = B e^{-2t} \quad \text{--- (1)}$

for $t > 0$ ~~not~~ writing KVL.

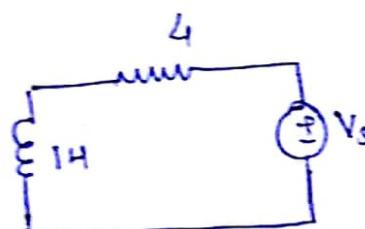

$$V_s - 4i(t) - V_L = 0$$

$$10e^{-2t} - 4i(t) - V_L = 0$$

$$L \frac{di}{dt} + 4i = 10e^{-2t} \quad \text{--- (1)}$$

$$\frac{di}{dt} + \frac{4i}{L} = 10e^{-2t}$$

taking $i = i_0$ if
for time $t > 0$ substituting the value of i_0 in
eqn ②


$$\frac{d(Be^{-2t})}{dt} + 4Be^{-2t} = 10e^{-2t}$$

$$-2Be^{-2t} + 4Be^{-2t} = 10e^{-2t}$$

$$\begin{array}{l} 2B = 10 \\ \hline B = 5 \end{array}$$

$$\therefore \boxed{i_0 = 5e^{-2t}}$$

for natural response $i < 0$

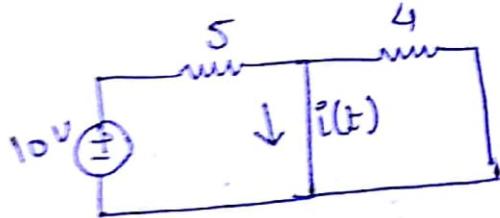

$$R_L = 4 \Omega$$

$$\begin{aligned} i_0 &= 2A \\ i_n &= Ae^{-\left(\frac{R_L}{L}\right)t} \end{aligned}$$

$$\tau = \frac{L}{R} = \frac{1}{4}$$

$$i = Ae^{-4t} + 5e^{-2t}$$

$$\text{for inductor } i(0^+) = i(0^-) = i(0)$$


$$0 = A + 5$$

$$\boxed{A = 3}$$

$$\therefore \boxed{i = 3e^{-4t} + 5e^{-2t} A}$$

Second Order Ckt

① Series RLC Ckt

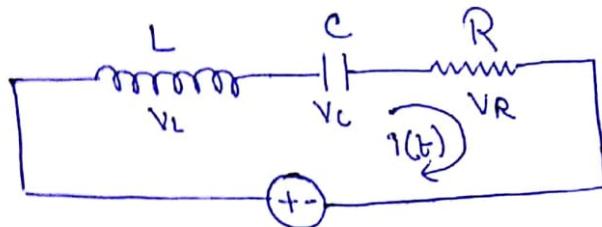

Apply KVL in the ckt

$$V_s(t) = V_L + V_C + V_R \\ = L \frac{di^o(t)}{dt} + \frac{1}{C} \int_0^t i(t) dt + V_C(0) + R i^o(t)$$

differentiating w.r.t. time t

$$\frac{dV_s(t)}{dt} = L \frac{d^2 i^o(t)}{dt^2} + \frac{1}{C} i^o(t) + \frac{dR i^o(t)}{dt}$$

$$\frac{dV_s}{dt} = L \frac{d^2 i}{dt^2} + R \frac{di^o(t)}{dt} + \frac{1}{C} i^o(t)$$

$$\frac{L}{L} \frac{dV_s(t)}{dt} = \frac{d^2 i^o}{dt^2} + \frac{R}{L} \frac{di^o(t)}{dt} + \frac{1}{LC} i^o(t) \quad \text{--- (1)}$$

general 2nd order diff eqn

$$\frac{d^2 u(t)}{dt^2} + 2\alpha \frac{du(t)}{dt} + \omega_0^2 u(t) = f(t) \quad \text{--- (2)}$$

Comparing eqn ① & ②

$$2\alpha = \frac{R}{L}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\Rightarrow \boxed{\alpha = \frac{R}{2L}}$$

$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

damping
coeff. factor

Resonant frequency of

$$f(t) = \frac{1}{L} \frac{dVs(t)}{dt}$$

forcing function.

we know that,

$$x(t) = x_f + x_n$$

To calculate natural response, Let us assume that

sol^m of diff^o in

$$\underline{x_n(t) = k e^{\alpha t}}$$

$$\frac{d^2 k e^{\alpha t}}{dt^2} + 2\alpha \frac{d k e^{\alpha t}}{dt} + \omega_0^2 k e^{\alpha t} = 0$$

$$k s^2 e^{\alpha t} + 2\alpha s k e^{\alpha t} + \omega_0^2 k e^{\alpha t} = 0$$

$$\underbrace{k e^{\alpha t}}_{\text{where } \neq 0} (s^2 + 2\alpha s + \omega_0^2) = 0$$

$$\therefore s^2 + 2\alpha s + \omega_0^2 = 0$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

where, $\omega_0 \rightarrow$ resonant frequency or undamped natural frequency

s_1 & s_2 are natural frequencies

These can have 3 types of sol^m depending upon the value of α

$$\left. \begin{array}{l} \alpha > \omega_0 \\ \alpha < \omega_0 \\ \alpha = \omega_0 \end{array} \right\}$$

$v_m(t)$

The natural response of RLC circuit where k_1 & k_2 are const. & are determined by

Initial values of $i(0)$, $\frac{di(0)}{dt}$


$$x_m = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

Case 1: When $\alpha > \omega_0$

∴ The response is over damped


So the roots are real & distinct

$$\therefore x_m = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

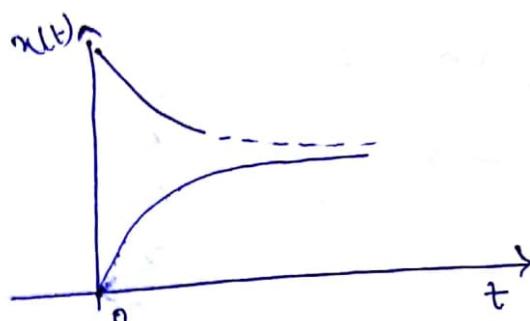

Case 2: When $\alpha = \omega_0$

∴ The response is critically damped

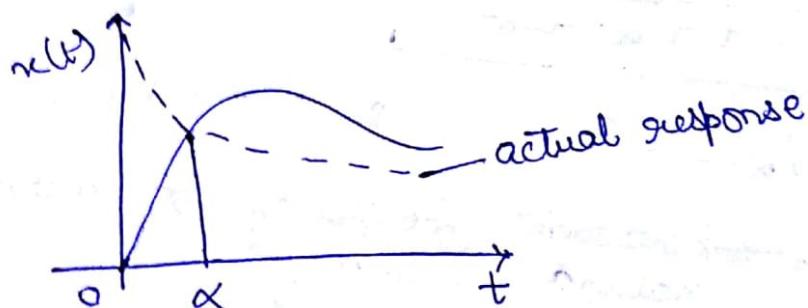


roots of real & equal

$$\therefore x_m = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$= k_3 e^{s_1 t}$$

$$k_3 = k_1 + k_2$$

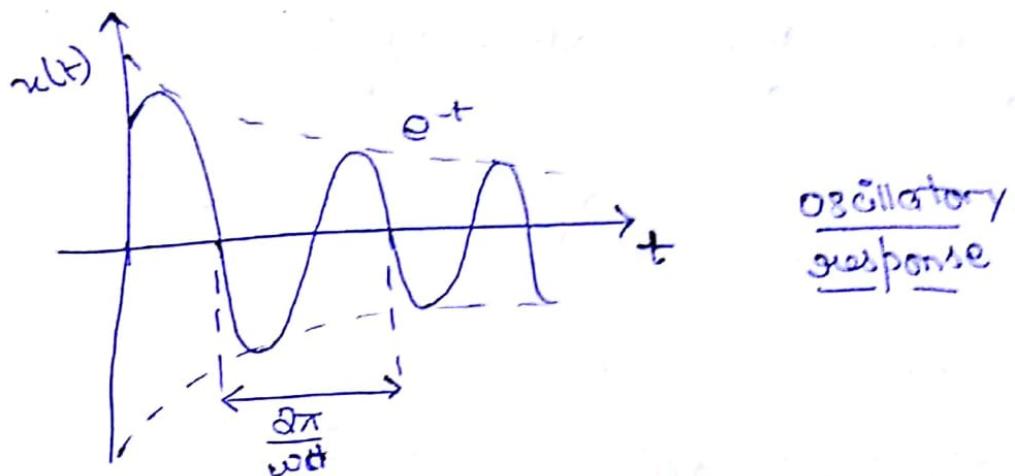Case 3: When $\alpha < \omega_0$
 \therefore The response is underdamped



If the roots are imaginary

$$u_n(t) = A \cos \omega_d t + B \sin \omega_d t$$

$$A = k_1 e^{s_1 t}$$


$$B = k_2 e^{s_2 t}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

damped natural frequency

$$u_n(t) = k_1 e^{s_1 t} \cos(\omega_d t) + k_2 e^{s_2 t} \sin(\omega_d t)$$

② Parallel RLC Circuit

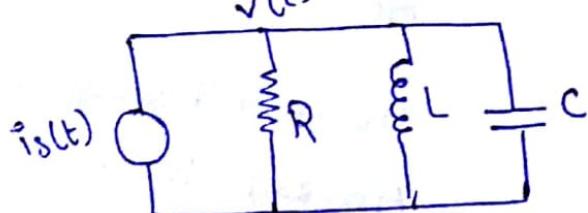

Applying KCL

$$i_s(t) = i_R + i_C + i_L$$

- (t-2)

(t-0)

(t-1)

$t > 0$
 $t > 0$

$$i_s(t) = \frac{v(t)}{R} + \frac{1}{L} \int_0^t v(t) dt + i_s(0) + \frac{cdv(t)}{dt}$$

On diff. w.r.t t

$$\frac{dis(t)}{dt} = \frac{1}{R} \frac{dv(t)}{dt} + \frac{1}{L} v(t) + cd \frac{d^2v(t)}{dt^2}$$

$$cd \frac{dis(t)}{dt} = d \frac{d^2v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{1}{LC} v(t) \quad -\textcircled{3}$$

General Eqn

$$d \frac{d^2v(t)}{dt^2} + 2\alpha \frac{dv(t)}{dt} + \omega_0^2 v(t) = f(t) \quad -\textcircled{4}$$

Comparing eqn $\textcircled{3}$ & $\textcircled{4}$

$$2\alpha = \frac{1}{RC}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

Forced Response (for RLC)

Input. $f'' = f(t)$

① K

kt

② ke^{bt} where
 $b \neq s_1, s_2$

③ $kd \sin \omega t$

④ $k \cos \omega t$

Forced Response (nf)


A

$At + B$

Ae^{bt}


$A \sin \omega t + B \cos \omega t$

$A \cos \omega t + B \sin \omega t$


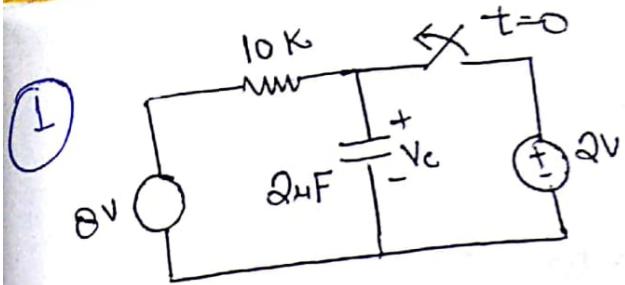


- a) Find V_c when switch is open
 b) Value of capacitor voltage after 50 ms of switch opens

$t < 0$

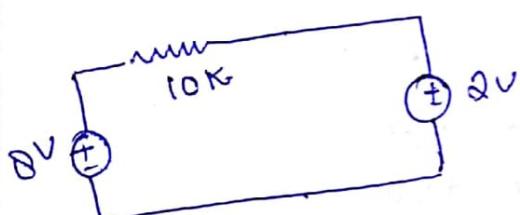
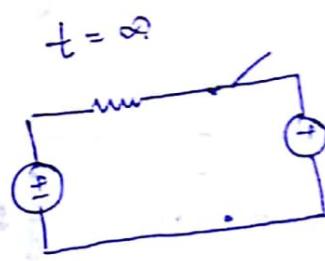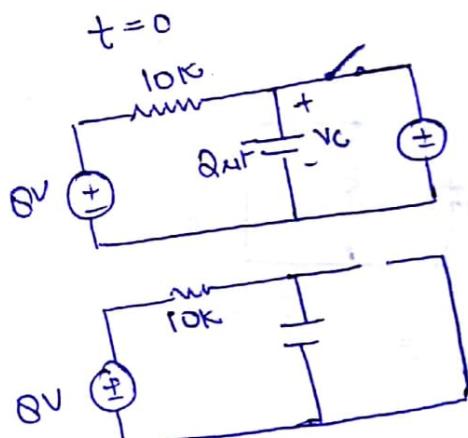
$$i(0^-) = \frac{8-2}{10k} = \frac{6}{10k}$$



$$8 - 10 \times \frac{6}{10k} = V_c$$

a)

$$2 \cancel{V} = V_c$$

b)

$$V = V_o e^{-t/RC}$$

$$\alpha = \frac{8-2}{10 \times 2 \times 10^3} = 1.5 \times 10^{-3}$$


$$= 1.5 \times 10^{-3} e^{-2.5}$$

$$V(0) = 8 - 6e^{-2.5}$$

$$V(t) = 8 + (2-8) e^{-t/20}$$


$$2 = 1.5 \times 10^{-3} e^{-2.5} V$$





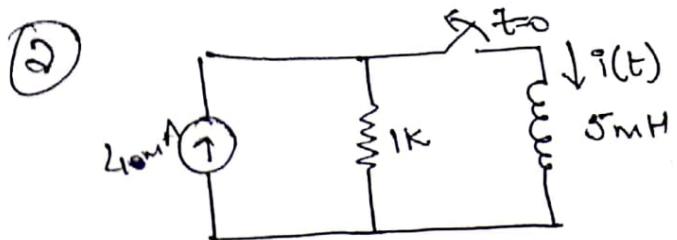


a) Find Inductor current after the switch is closed

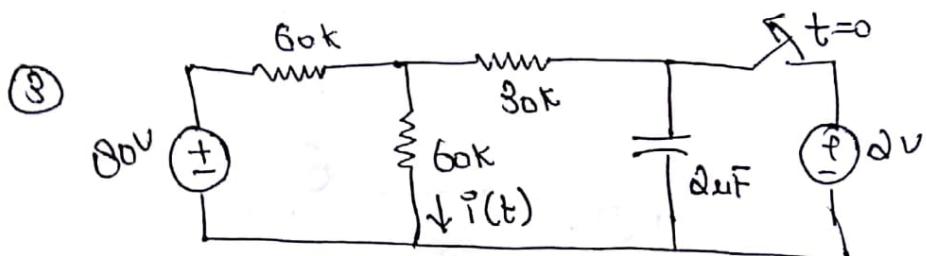b) Find time to reach 2mA across the inductor.



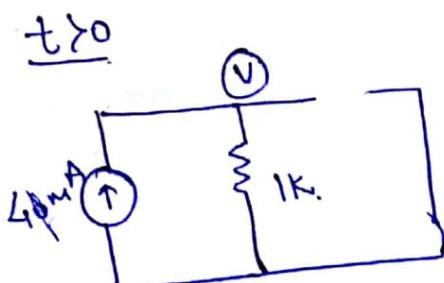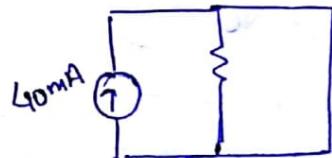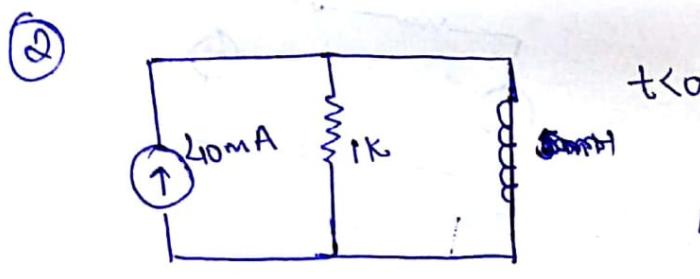Find the current $i(t)$ for $t > 0$
Let it be in steady state for $t < 0$




$$i =$$

$$V(0^+) = 40 \text{ V}$$

$$V(0^-) = 40 \text{ V}$$
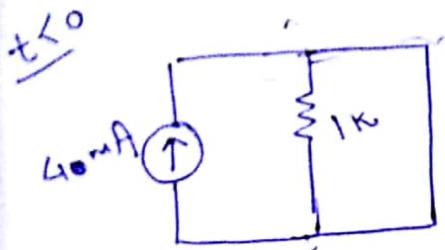
$$v(t) = v(\infty) + [v(0) - v(\infty)] e^{-t/\tau}$$



$$v(0^-) = 4 \text{ V}$$

~~$v(0^+) = 4 \text{ V}$~~

$$(1 - e^{-\frac{R}{L} t})$$

at $t=0$

$$i(0) = 0$$

$$\tau = \frac{L}{R}$$

$$= 5 \text{ ms}$$

$$i = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$= 4 \text{ mA} + [0 - 4] e^{-t/5}$$

$$i/\text{mA} = [4 - 4e^{-t/5 \text{ ms}}]$$



$$1 - \frac{1}{2} = e^{-t/5 \text{ ms}}$$

$$\frac{1}{2} = e^{-t/5}$$

$$e^{t/5} = 2$$

$$\frac{t}{5} = \ln 2$$

$$t = 5 \ln 2 \text{ ms}$$

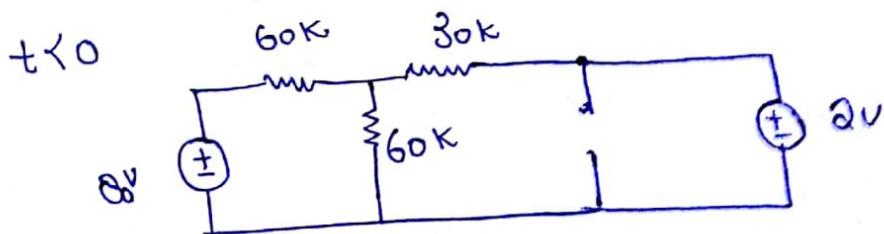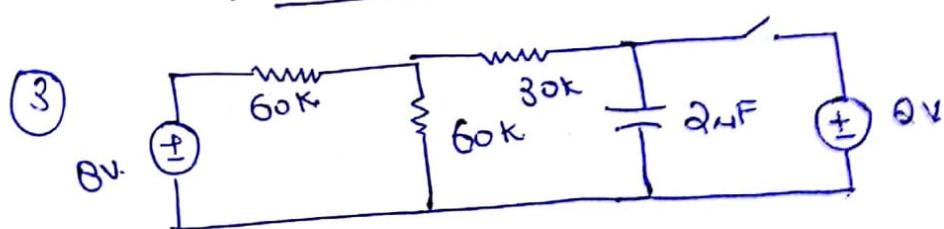


$$R = 60 \text{ k}$$


$$\tau = RC = 60 \times 2 = 120 \times 10^3 \times 10^{-6}$$

$$= 120 \text{ ms}$$

for $t=0$

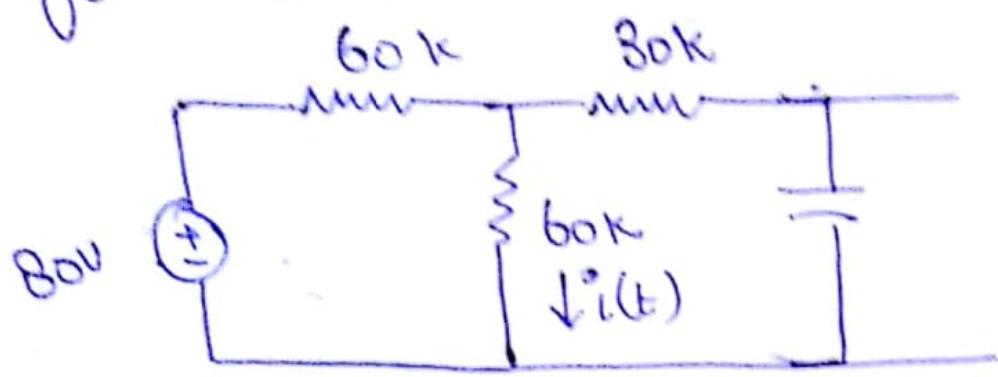

$t > 0$

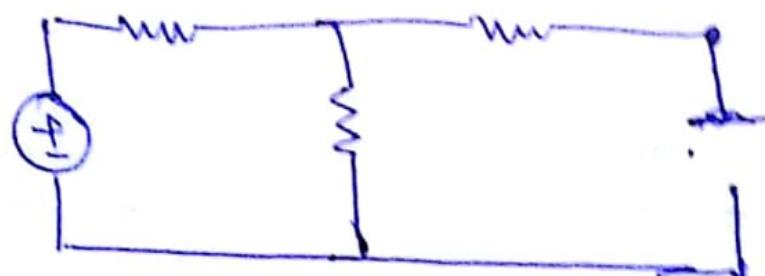

Source free series RLC circuit

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

a) when ($\alpha > \omega_0$) Overdamped

$$i(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

b) Critically damped ($\alpha = \omega_0$)

$$i(t) = A_1 e^{S_1 t} + A_2 t e^{S_1 t} \\ = (A_1 + A_2 t) e^{-\alpha t}$$

$$S_1 = S_2 = -\alpha = -\frac{R}{2L}, C = \frac{4L}{R^2}$$

c) Underdamped ($\alpha < \omega_0$)

$$S_1 = -\alpha + j\omega_d$$

$$S_2 = -\alpha - j\omega_d$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \quad \rightarrow \text{damping frequency}$$

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$B_1 = A_1 + A_2$$

$$B_2 = j(A_1 + A_2)$$

Source free parallel RLC circuit

$$S_1, S_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

a) Overdamped ($\alpha > \omega_0$)

$$v(t) = A_1 e^{S_1 t} + A_2 e^{S_2 t}$$

b) Critically damped ($\alpha = \omega_0$)

$$v(t) = (A_1 + A_2 t) e^{-\alpha t}$$

c) Underdamped ($\alpha < \omega_0$)

$$S_1, S_2 = -\alpha \pm j\omega_d$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$V(t) = V_0 e^{-at} \quad (\text{Initial value at } t=0)$$

Step 2: Assume of a high RLC circuit

$$V(t) = V_0 + A_1 e^{st} + A_2 e^{rt} \quad (\text{undamped})$$

$$V(t) = V_0 + (A_1 + A_2 t) e^{st} \quad (\text{critically damped})$$

$$V(t) = V_0 + (A_1 \cos st + A_2 \sin st) e^{st} \quad (\text{damped})$$

Step 3: Assume of parallel RLC circuit

$$I(t) = I_0 + A_1 e^{st} + A_2 e^{rt} \quad (\text{undamped})$$

$$I(t) = I_0 + (A_1 + A_2 t) e^{st} \quad (\text{critically damped})$$

$$I(t) = I_0 + (A_1 \cos st + A_2 \sin st) e^{st} \quad (\text{damped})$$

$$\underline{\text{Qn}} \quad R = 4\Omega \quad L = 4H \quad C = \frac{1}{4} F$$


Calculate the characteristic roots of the circuit is the natural frequency ω_0 , ζ , ω_n

$$\alpha = \frac{R}{2L} = \frac{4 \times 5}{2 \times 4} = 5 \quad \omega_0 = \frac{1}{\sqrt{LC}} = 1$$

$$s_1 = -5 \pm \sqrt{25 - 1} \\ = -5 \pm \sqrt{24}$$


$$s_1 = -0.101 \\ s_2 = -9.89$$
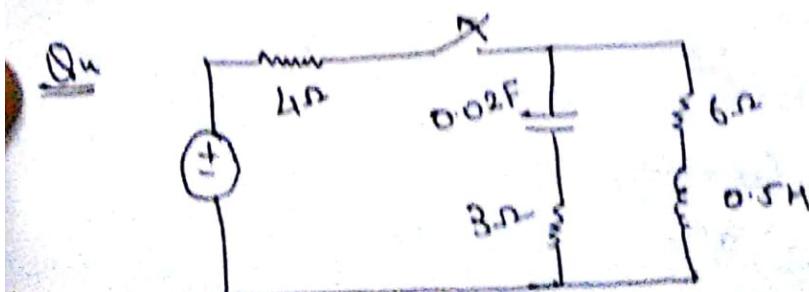
$$I(t) = A_1 e^{(-5+\sqrt{24})t} + A_2 e^{(-5-\sqrt{24})t} \\ = A_1 e^{-0.101t} + A_2 e^{-9.89t}$$



Find $i(t)$ assuming circuit has reached steady state at $t=0^-$


for $t < 0$

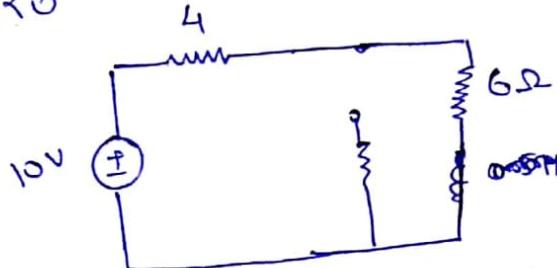

$$i(t)_{0^-} = 1 \text{ Amp.}$$

$$v(0) = 6 \text{ V}$$

for $t > 0$

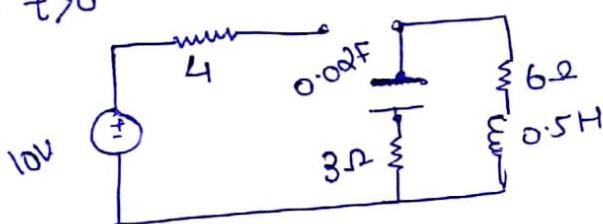

$$\alpha = \frac{R}{2L} = \frac{9}{1} = 9$$

$$\alpha = 9$$

$$\omega_0 = \sqrt{\frac{1}{\frac{9}{100} \times \frac{8}{10}}} = 10$$

$$i(t) =$$

$$s_{1,2} = -9 \pm j\sqrt{19}$$

$$\omega = \sqrt{9 - 100} = \sqrt{-19}$$

$$i(t) = e^{-9t} (B_1 \cos \sqrt{19}t + B_2 \sin \sqrt{19}t)$$

$$\text{At } t=0 \quad i(0) = 1 \text{ A}$$

$$1 = B_1$$

for circuit, applying KVL

$$6i + L \frac{di}{dt} + 3i + \underbrace{1 \int idt}_{C} = v_o$$

$$\frac{di(0)}{dt} = -\frac{1}{L} (R I_0 + v_o)$$

$$= -\frac{1}{2} (9 \times 1 - 6) \quad \begin{matrix} \text{Polarity indicated as was} \\ \text{the cap. is discharging} \end{matrix}$$

$$= -6 \text{ A/s}$$

$$\frac{di(t)}{dt} = (B_1 \cos \sqrt{19}t + B_2 \sin \sqrt{19}t) (-9) e^{-9t} +$$

$$e^{-9t} (-\sqrt{19} B_1 \sin \sqrt{19}t + B_2 \sqrt{19} \cos \sqrt{19}t)$$

$$\frac{d^2l(0)}{dt^2} = -9\beta_1 + \sqrt{9}\beta_2$$


$$-6 = -9 \times 1 + \sqrt{19}\beta_2$$

$$\frac{3}{\sqrt{9}} = \beta_2$$

$$\underline{\beta_2 = 0.6882}$$

$$\therefore \underline{l(t) = e^{9t} (\cos \sqrt{19}t + 0.6882 \sin \sqrt{19}t)}$$


Operational Amplifiers (Op-amp)

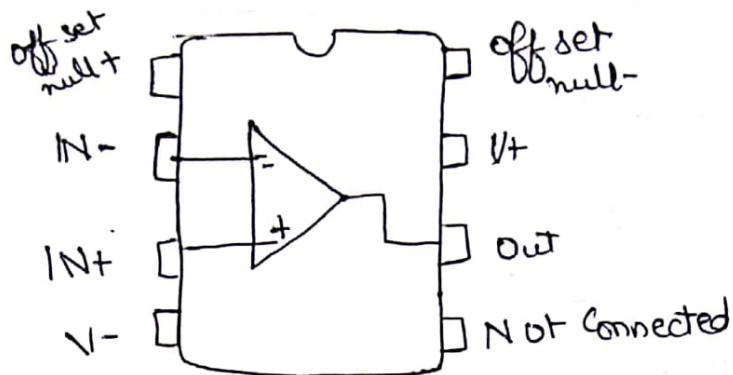

Dual in-line package - 8 pin


741

Schematic symbol of op-amp

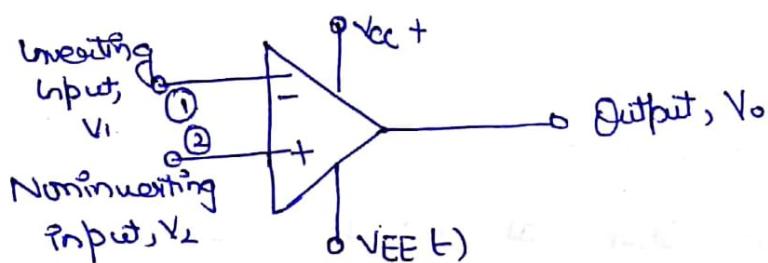

Open loop voltage gain

$$A_{OL} = \frac{V_o}{V_d}$$

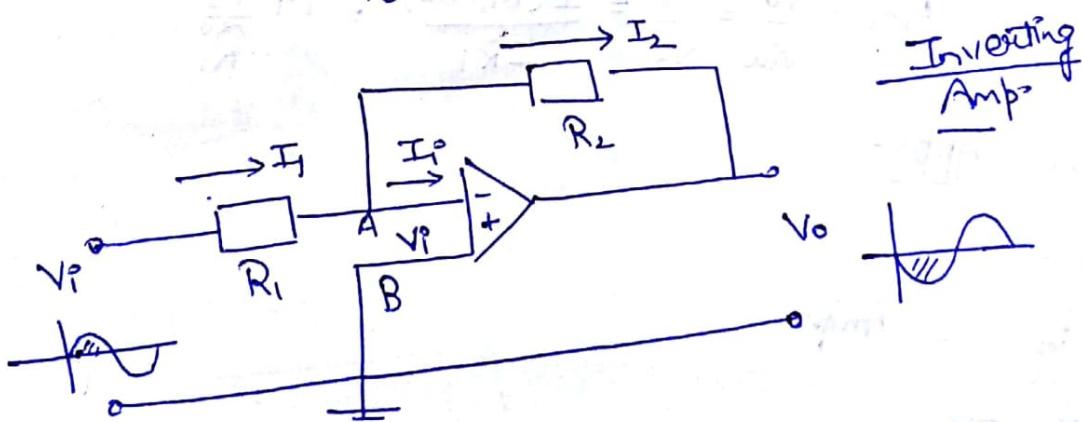

$$I_1 = \frac{V_i}{R_1} \quad I_2 = -\frac{V_o}{R_f}$$

$$\text{Since } I_1 = 0 \\ \therefore I_1 = I_2$$


$$\frac{V_o}{R_f} = -\frac{V_o}{R_i} \Rightarrow \boxed{\frac{V_o}{V_i} = \frac{R_f}{R_i}}$$

amplification factor

Closed loop gain :

$$\boxed{A_{CL} = -\frac{R_f}{R_i}}$$

Noninverting Amp.

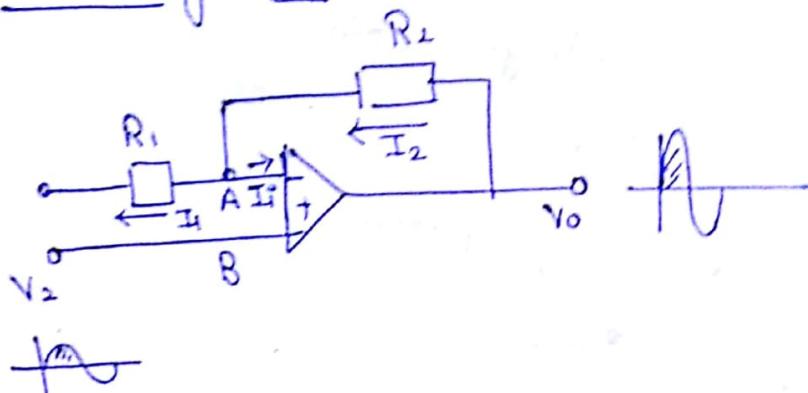

* Since $I_1 = 0 \Rightarrow I_1 = I_2 = I$

* Due to virtual short at input terminal

$$V_2 = V_B = V_A = IR_1$$

$$\boxed{V_0 = I(R_1 + R_2)}$$


$$\underline{R_f = R_2}$$

$$A_{CL} = \frac{V_0}{V_{in}} = \frac{V_0}{V_2} = \frac{I(R_1 + R_2)}{IR_1} = 1 + \frac{R_f}{R_1}$$

Simple Apps-

- ① Adder
- ② Difference Amp
- ③ Subtractor
- ④ Voltage follower

① Adder or Summing ckt

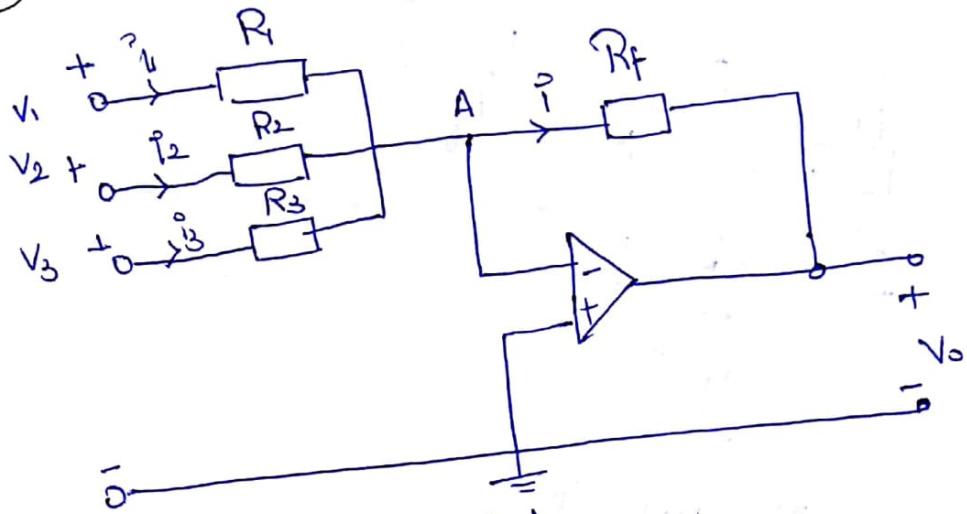

A is virtually grounded

$$i_1 = \frac{V_1}{R_1} \quad i_n = \frac{V_n}{R_n}$$

$$i = -\frac{V_o}{R_f} = 0 - \frac{V_o}{R_f}$$

Applying KCL

$$i_1 + i_2 + i_3 - i_n = i$$

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = -\frac{V_o}{R_f} \quad \text{(here)}$$

$$\therefore V_o = - \left\{ \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right\}$$

$$V_o = - [K_1 V_1 + K_2 V_2 + K_3 V_3]$$

$$\text{If } R_1 = R_2 = R_3 = R_f$$


$$\therefore V_o = - (V_1 + V_2 + V_3)$$

$$\text{If } R_1 = R_2 = R_3 = R$$

$$V_o = - \frac{R_f}{R} (V_1 + V_2 + V_3)$$

$$V_o = - A_{CL} (V_1 + V_2 + V_3)$$

② Difference Amp

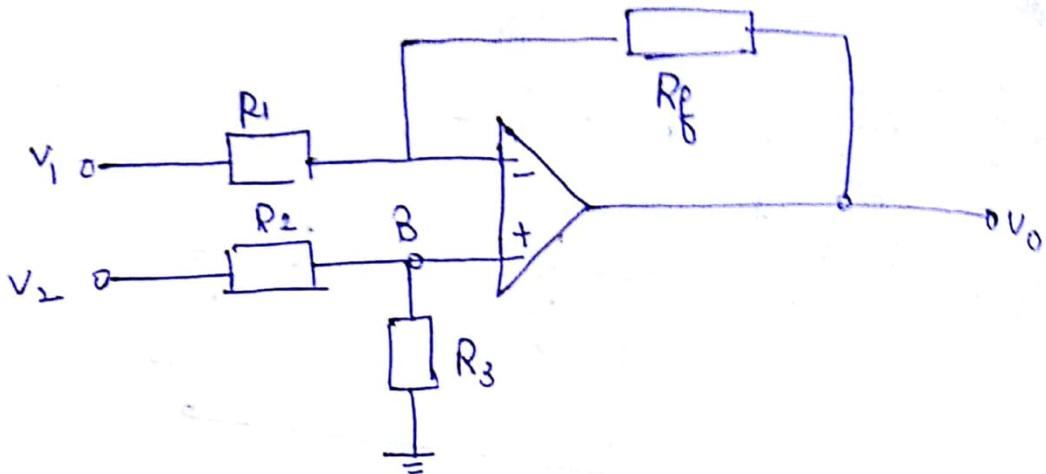

Voltage at point B

$$V_B = \frac{R_3}{R_2 + R_3} V_2$$

* It is a combination of inverting & non-inverting amplifiers

* When $V_1=0$ \rightarrow non-inverting

* When $V_2=0$, \rightarrow inverting

* We shall use superposition theorem to determine output when both the inputs are present

When $V_2=0$, R_2 & R_3 are in ||, carrying no current

$$\therefore V_{OL} = -\frac{R_f}{R_1} V_1$$

When $V_1=0$, \therefore

$$V_B = \frac{R_3}{R_2 + R_3} V_2$$

$$V_{O2} = \left(1 + \frac{R_f}{R_1} \right) V_B$$

$$= \left(1 + \frac{R_f}{R_1} \right) \left(\frac{R_3}{R_2 + R_3} \right) V_2$$

we make $R_1 = R_2$ & $R_f = R_S$

$$V_{o2} = \frac{R_f}{R_1} V_2$$


$$\therefore V_o = V_{o1} + V_{o2}$$

$$\boxed{V_o = -\frac{R_f}{R_1} (V_1 - V_2)}$$

$$A_D = \frac{V_o}{V_1 - V_2} = -\frac{R_f}{R_1}$$

differential gain

③ Subtractor

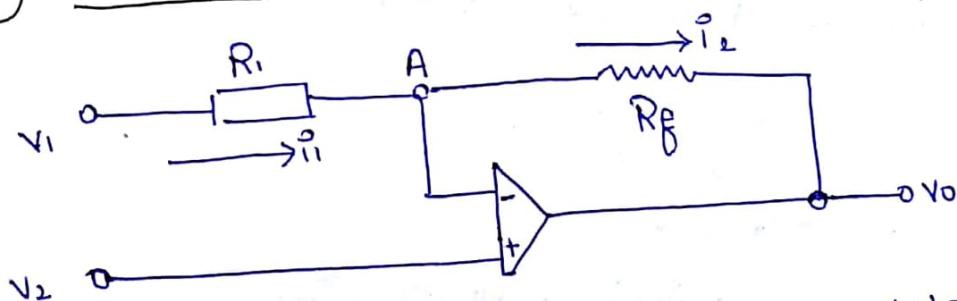

Beacause of virtual short, A is at same potential

as V_2

$$i_1 = i_2$$

$$\frac{V_1 - V_2}{R_1} = \frac{V_2 - V_0}{R_f}$$

$$\boxed{\frac{V_o}{R_f} = \frac{V_2}{R_f} + \frac{V_2 - V_1}{R_1}}$$

$$\boxed{V_o = V_2 \left(1 + \frac{R_f}{R_1}\right) - \frac{R_f}{R_1} V_1}$$

If $R_f \gg R_i$

$$\therefore V_o = \frac{R_f}{R_i} (V_2 - V_1)$$

$$V_o = A_{CL} (V_2 - V_1)$$

Q. $R_i = 20\text{k}\Omega$ $R_f = 2\text{M}\Omega$

$$A_{OL} = -\frac{R_f}{R_i} = -\frac{2 \times 10^6}{20 \times 10^3} = -100$$

Input Resistance = ∞


Output " = 0

Q. $R_f = 200\text{k}\Omega$ $R_i = 2\text{k}\Omega$ $V_1 = 4\text{V}$ $V_2 = 8.8\text{V}$

$$V_o = -\frac{200}{2} \times \frac{(8.8 - 4)}{10} = -20 \text{ V}$$

$$V_o = V_2 \left[1 + \frac{R_f}{R_i} \right] - V_1 \frac{R_f}{R_i}$$

Voltage follower

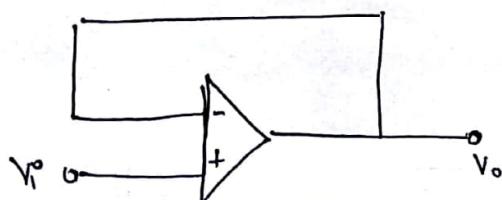


$$A_{CL} = 1 + \frac{R_f}{R_i}$$

The lowest gain possible is 1, for which $R_f = 0$ (shorting) & $R_i = \infty$ (open)


(Buffer amplifier)

Integrating using op-amp

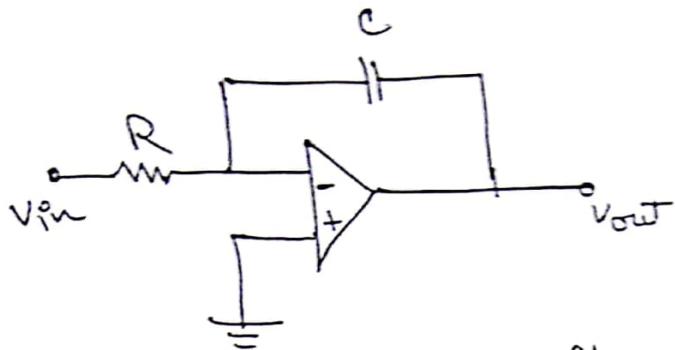

$$V_{out} = \int_0^t -\frac{V_{in}}{RC} dt + V_{initial}$$

Differentiator

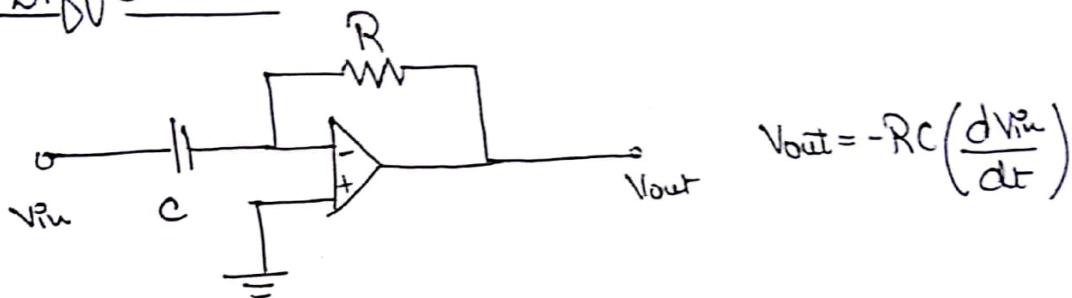

$$V_{out} = -RC \left(\frac{dV_{in}}{dt} \right)$$

Common Mode Rejection Ratio (CMRR)

$$V_o = A_d V_d + A_c V_c$$

Common mode gain

↓
differential gain


$$\therefore CMRR = \frac{A_d}{A_c} \quad (\text{ideally } A_c = 0)$$

but this does not happen.
 $\therefore \text{ideally } CMRR = \infty$

$$V_o = A_d V_d \left(1 + \frac{A_c V_c}{A_d V_d} \right) = A_d V_d \left[1 + \frac{V_c}{V_d} CMRR \right]$$

- ★ Slew rate
- ★ Input bias current


①

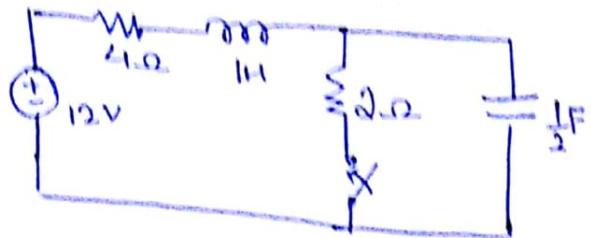

$$k_1 + k_2 e^{-t/\tau}$$


Find the complete response of the cpt 'i' & then
for $t \geq 0$

②

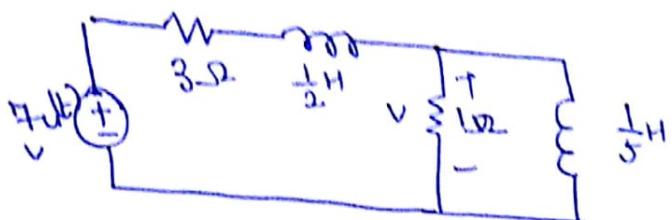

find $v_o(t)$ for $t \geq 0$

①

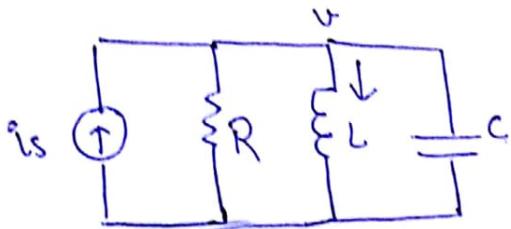

$$i_R + i_L + i_C = i_s$$

$$\frac{v}{R} + \frac{1}{L} \int_{t_0}^t u dt + i_L(t_0) + \frac{c du}{dt} = i_s$$

$$R \frac{du}{dt} + \frac{1}{L} u + \frac{cdv^2}{dt^2} = \frac{dis}{dt}$$

$$cdv^2 + R \frac{du}{dt} + \frac{u}{L} = \frac{dis}{dt}$$

$$\frac{du^2}{dt^2} + \frac{R}{C} \frac{du}{dt} + \frac{u}{LC} = \frac{dis}{dt}$$

$$\text{for } i_s = 1 \quad \frac{dis}{dt} = 0$$

②

$$s^2 + 2\alpha s + \omega^2 = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \alpha = \frac{R}{2C}$$

$$\omega_0 = \frac{1}{\sqrt{10 \times 10^{-3} \times 1 \times 10^{-3}}} = \frac{1}{\sqrt{10^{-5}}} =$$