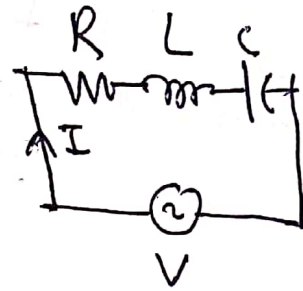


Summary of Resonance (Series RLC)

① Resonance frequency $\omega_0 = \frac{1}{\sqrt{LC}}$



② Quality factor (Q) = $\frac{\omega_0 L}{R} = \frac{1}{\omega_0 R C} = \frac{1}{R} \sqrt{\frac{L}{C}}$

$$Q = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{\text{Resonance freq}}{\omega_2 - \omega_1} = \frac{\omega_0}{BW}$$

↑ Selectivity

$$\left| \frac{V_C}{V} \right| = \left| \frac{V_L}{V} \right| = m_C = m_L = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

At resonance

magnification factor

③

$$R, L, C, \omega_0, BW, S, Q$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad BW = \frac{\omega_0}{Q=S} = \frac{R}{L} \text{ rad/sec}$$


$$\cancel{BW = \frac{\omega_0}{\omega_0 R}} \quad \cancel{\omega_0}$$

$$BW = \frac{\omega_0}{\frac{\omega_0 L}{R}} = \frac{R}{L} \quad \text{or} \quad \frac{\omega_0}{\frac{1}{\omega_0 R C}} = \omega_0^2 R C = \frac{1}{L C} \cdot R C = \frac{R}{L}$$


④ $\omega < \omega_0$ $\omega_0 = \omega$ $\omega > \omega_0$ } Series Resonance

\downarrow \downarrow \downarrow
 R_C R R_L

Parallel RLC Resonance Circuit

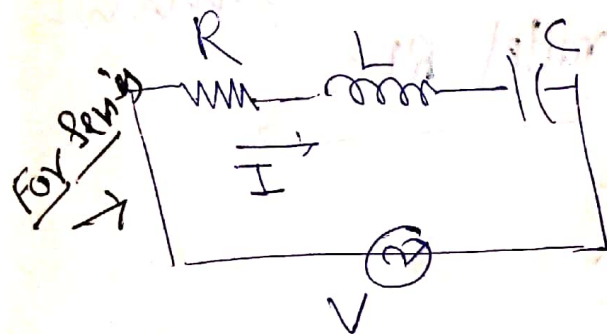

\Rightarrow

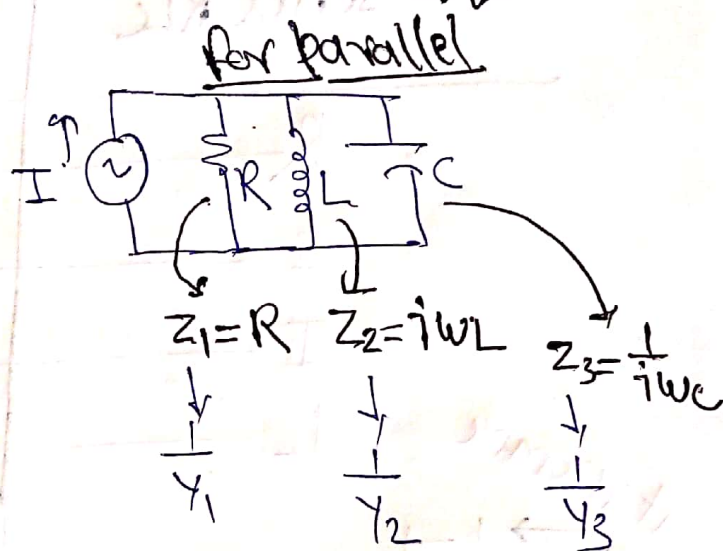

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

Impedance

$$Y = \frac{1}{Z}$$

Admittance

$$Y = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$


$$Y = \frac{1}{R} + \frac{1}{j\omega L} + \frac{j\omega C}{1}$$

$$Y = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

$$|Y| = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}$$

Parallel RLC Resonance using Series RLC Resonance

① For Series RLC

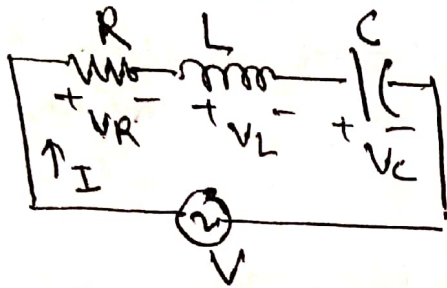

Apply KVL—

$$V = V_R + i(V_L - V_C)$$

$$V = IR + i(IX_L - IX_C)$$


$$\frac{V}{I} = R + i(X_L - X_C)$$

$$Z = R + i(\omega L - \frac{1}{\omega C})$$


$$|Z| = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

②

Phasor diagram:-

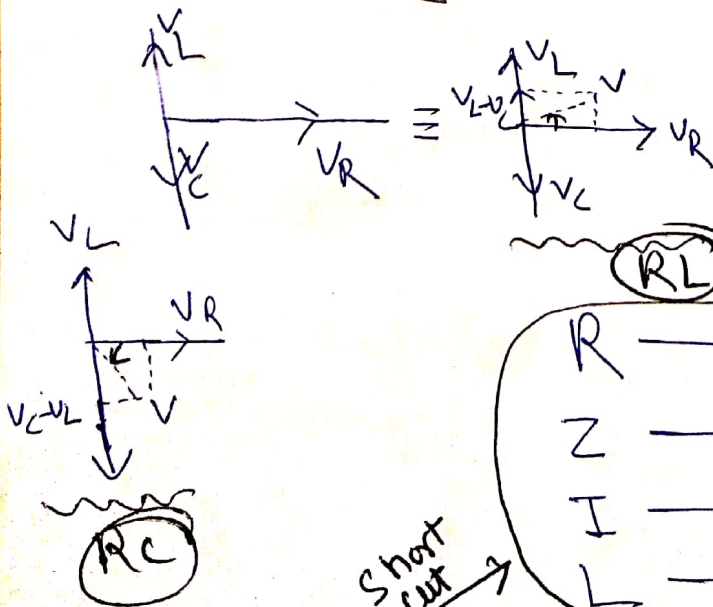

③ For parallel RLC

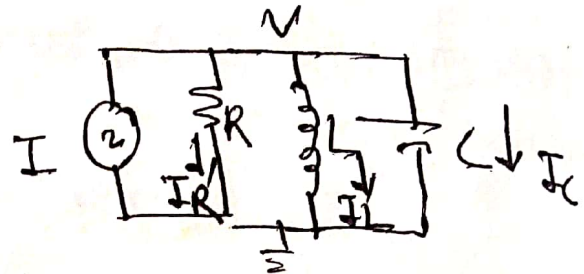

Apply KCL

$$I = I_R + I_L + I_C$$

$$I = \frac{V}{R} + \frac{V}{X_L} + \frac{V}{X_C}$$



$$\frac{I}{V} = \frac{1}{R} + \frac{1}{X_L} + \frac{1}{X_C}$$

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{i\omega L} + \frac{1}{-i\omega C}$$

$$\frac{1}{Z} = \frac{1}{R} + i(\omega C - \frac{1}{\omega L})$$

$$Y = \frac{1}{R} + i(\omega C - \frac{1}{\omega L})$$

$$|Y| = \sqrt{(\frac{1}{R})^2 + (\omega C - \frac{1}{\omega L})^2}$$

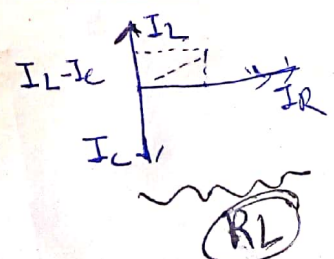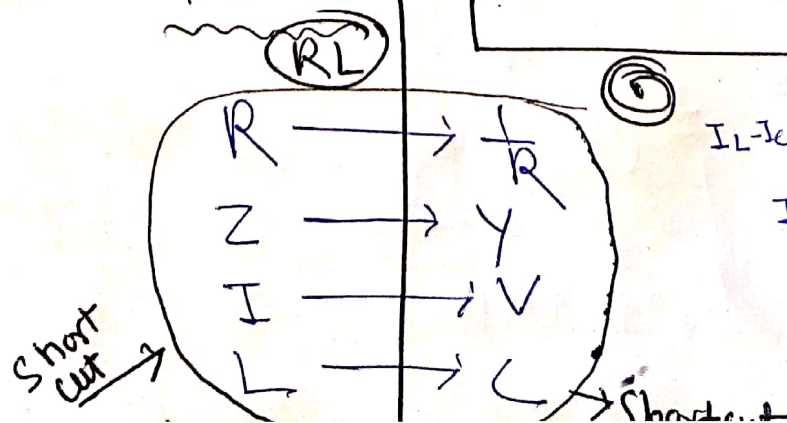

At resonance (Series)

$$\omega L = \frac{1}{\omega C}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

$$\textcircled{1} |Z|_{\min} = R$$

$$\textcircled{2} I_{\max} = \frac{V}{|Z|_{\min}} = \frac{V}{R}$$

$$\textcircled{3} M_L = \frac{V_L}{V}, \quad m_C = \frac{V_C}{V}$$

At resonance

$$M_L = m_C = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 R C} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= Q = S = \frac{\omega_0}{BW} = \frac{\omega_0}{\omega_2 - \omega_1}$$

$$\textcircled{4} BW = \frac{\omega_0}{Q} = \frac{\omega_0}{\frac{\omega_0 L}{R}} = \frac{R}{L}$$

rad/sec

At resonance (Parallel)

$$\omega C = \frac{1}{\omega L}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$

$$\textcircled{1} |Y|_{\min} = \frac{1}{R} \quad \left\{ Y_{\min} = \frac{1}{Z_{\max}} \right\}$$

$$\textcircled{2} |V|_{\max} = \frac{I}{|Y|_{\min}} = \frac{I}{Y_R} = \frac{I}{\frac{1}{R}} = IR$$

$$\boxed{|V|_{\max} = IR}$$

$$M_L = \frac{I_L}{I}, \quad m_C = \frac{I_C}{I}$$

At resonance

$$M_L = m_C = \omega_0 R C = \frac{R}{\omega_0 L} = R \sqrt{\frac{C}{L}}$$


$$= Q = S = \frac{\omega_0}{BW} = \frac{\omega_0}{\omega_2 - \omega_1}$$

$$\textcircled{4} BW = \frac{\omega_0}{Q} = \frac{\omega_0}{\omega_0 R C} = \frac{1}{RC}$$

rad/sec

Bandwidth:

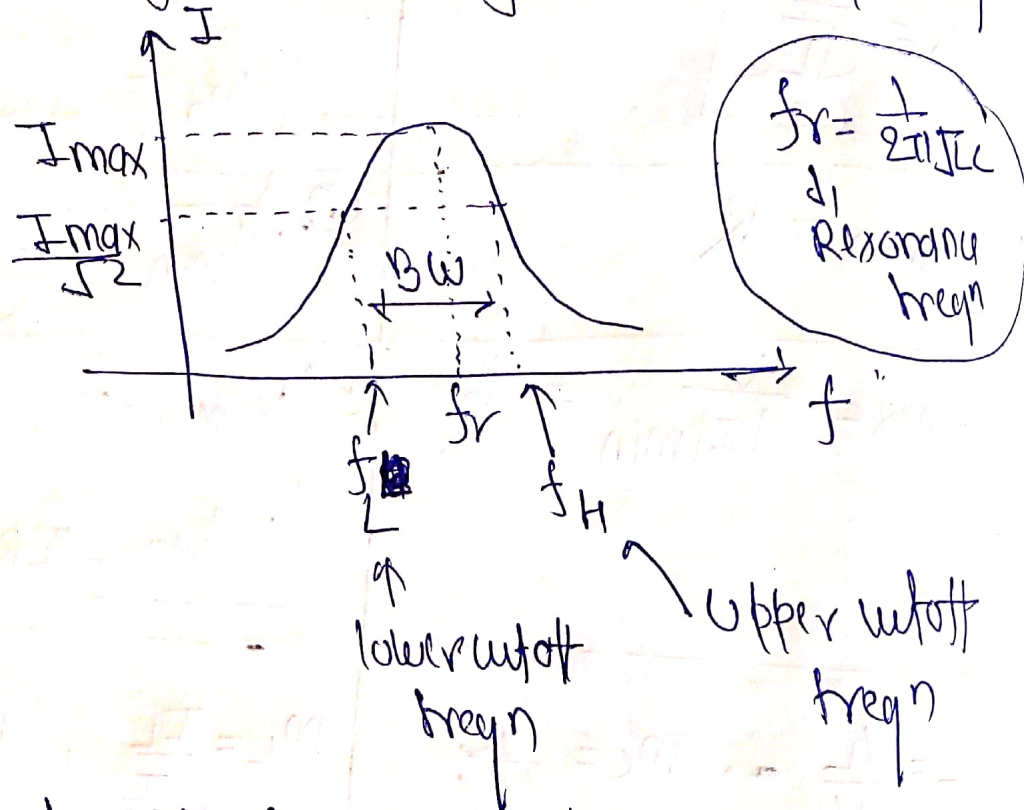The difference between the lower cutoff frequency and upper cutoff frequency at which current is 0.707 (corresponding to half of maximum power)



$$\text{Band width (Bw)} = (f_H - f_L) \text{ Hz}$$


$$\text{Band width (Bw)} = \frac{R}{2\pi L} \text{ Hz}$$

$$\text{Lower cutoff freqn } (f_L) = f_r - \frac{B.w.}{2}$$

$$\text{Upper cutoff freqn } (f_H) = f_r + \frac{B.w.}{2}$$

$$f_r \rightarrow \text{Resonance freqn} = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

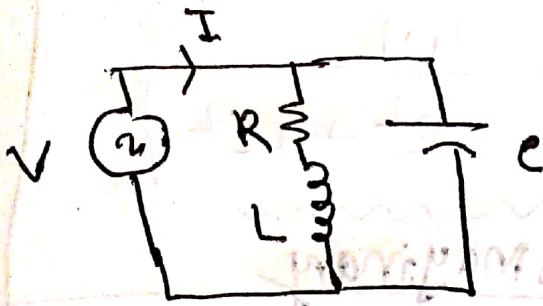Prob: Find the resonance condition of the following circuit.





Soln

$$L \rightarrow X_L = j\omega L = 2\pi fL \text{ ohm}$$

↑
Inductive Reactance

$$C \rightarrow X_C = \frac{1}{j\omega C} = \frac{1}{j2\pi fC} \text{ ohm}$$

↑
Capacitive Reactance.

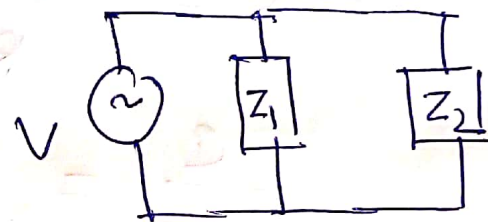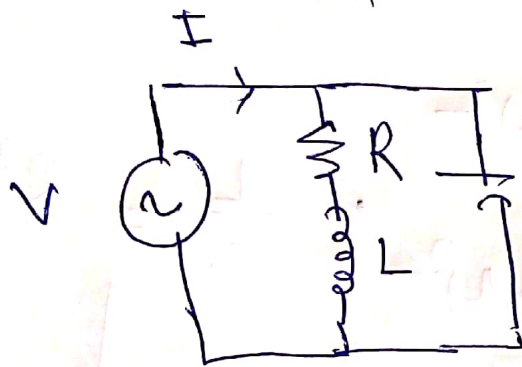

$$Z_1 = R + j\omega L$$

$$Z_2 = \frac{1}{j\omega C}$$

Since the circuit is in parallel combination-

$$Y = \frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{R + j\omega L} + \frac{1}{\frac{1}{j\omega C}}$$

↑
Admittance

↑
Impedance

$$= \frac{R - j\omega L}{(R + j\omega L)(R - j\omega L)} + j\omega C$$

$$= \frac{R - j\omega L}{R^2 + \omega^2 L^2} + j\omega C$$

$$Y = \underbrace{\frac{R}{R^2 + (\omega L)^2}}_{\text{Real}} + j \underbrace{\left(\omega C - \frac{\omega L}{R^2 + (\omega L)^2} \right)}_{\text{Imaginary}}$$

At resonance, the imaginary part = 0

$$\omega C - \frac{\omega L}{R^2 + (\omega L)^2} = 0$$

$$\omega C = \frac{\omega L}{R^2 + (\omega L)^2}$$

$$\frac{C}{L} = \frac{1}{R^2 + (\omega L)^2}; \quad \frac{L}{C} = R^2 + (\omega L)^2$$

$$\frac{(\omega L)^2}{R^2 + (\omega L)^2}$$

$$(\omega L)^2 = \frac{L}{C} - R^2$$

$$\omega L = \sqrt{\frac{L}{C} - R^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

rad/sec

$$\omega = \frac{1}{L} \sqrt{\frac{L}{C} - R^2}$$

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \text{ Hz}$$

and

$$|Y| = \frac{R}{R^2 + (\omega L)^2} \text{ ohm}^{-1}$$

Ans