

## Experiment No. 10


→ Circuit

To study the behavior of Series-Parallel RLC ckt at Resonance.
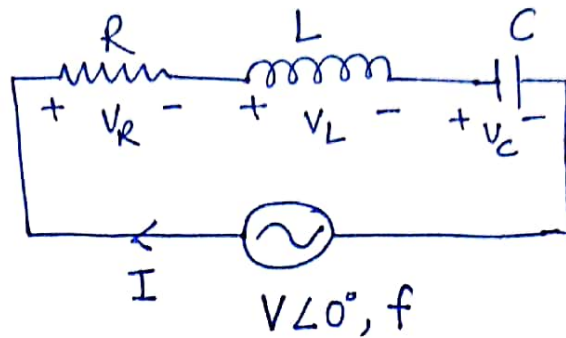
### Series RLC Resonance Circuit

- Inductive Reactance,  
 $X_L = 2\pi fL = \omega L$

- Capacitive Reactance,  
 $X_C = \frac{1}{2\pi fC} = \frac{1}{\omega C}$




Note! when  $X_L > X_C$ , the circuit is inductive  
when  $X_C > X_L$ , the circuit is capacitive


The total circuit impedance,

$$Z = R + jX_T$$

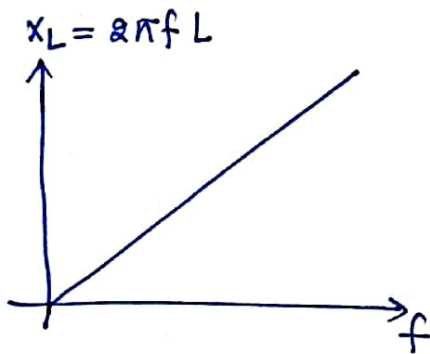
$$\begin{aligned} \text{where, } X_T &= X_L - X_C & X_L > X_C \\ &= X_C - X_L & X_C > X_L \end{aligned}$$



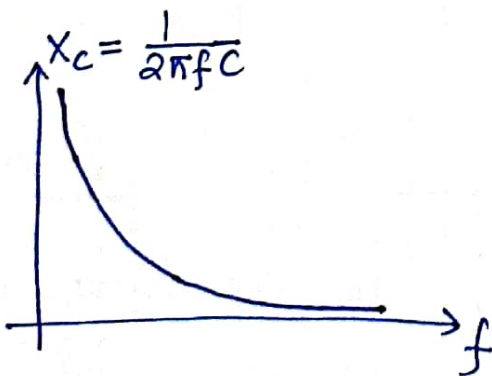
$$\begin{aligned} \text{At } f=0, \quad X_L &= 2\pi fL = 0 \\ \text{At } f=\infty, \quad X_L &= 2\pi fL = \infty \\ [X_L &\propto f] \end{aligned}$$


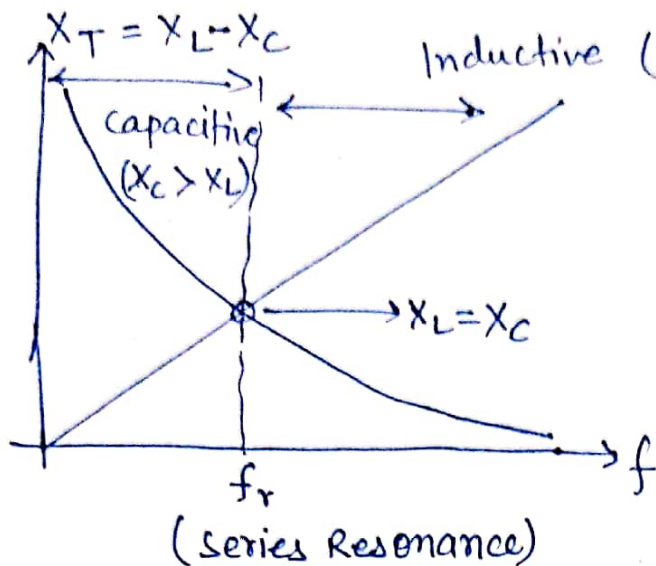
$$\begin{aligned} \text{At } f=0, \quad X_C &= \frac{1}{2\pi fC} = \infty \\ \text{At } f=\infty, \quad X_C &= 0 \\ [X_C &\propto f^{-1}] \end{aligned}$$




⇒

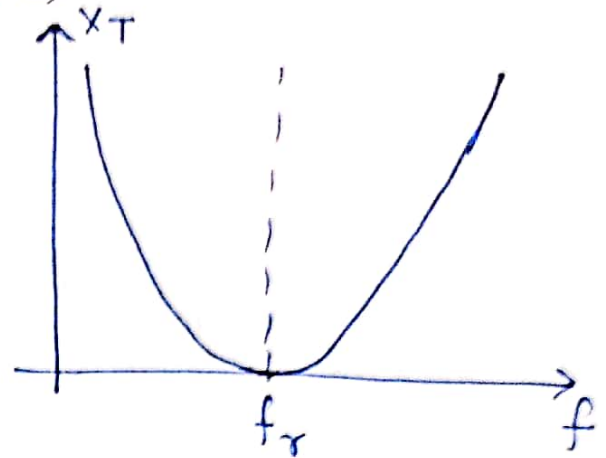

At  $f = f_r \Rightarrow X_L = X_C \Rightarrow Z = R + j(X_L - X_C)$   
 $2\pi f_r L = \frac{1}{2\pi f_r C} \quad \boxed{Z = R} \text{ at } f = f_r$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \text{ (Hz)}$$
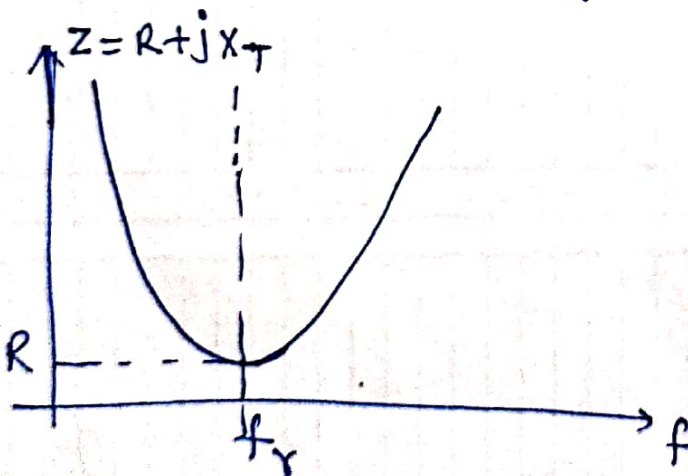
$$\omega_r = \frac{1}{\sqrt{LC}} \text{ (rad)}$$



$Z = R + j(X_L - X_C)$  ohm  
 ↳ complex quantity

$Z = |Z| \angle \phi$  —→ phase  
 ↳ magnitude



$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right)$$

Now, total current,

$$I = \frac{V \angle 0^\circ}{Z} = \frac{V \angle 0^\circ}{|Z| \angle \phi}$$

$$I = \frac{V}{|Z|} \angle -\phi$$

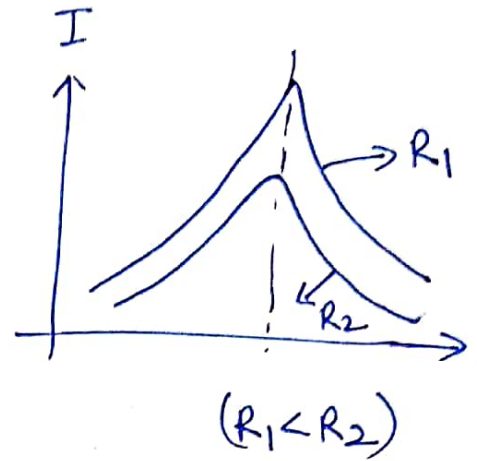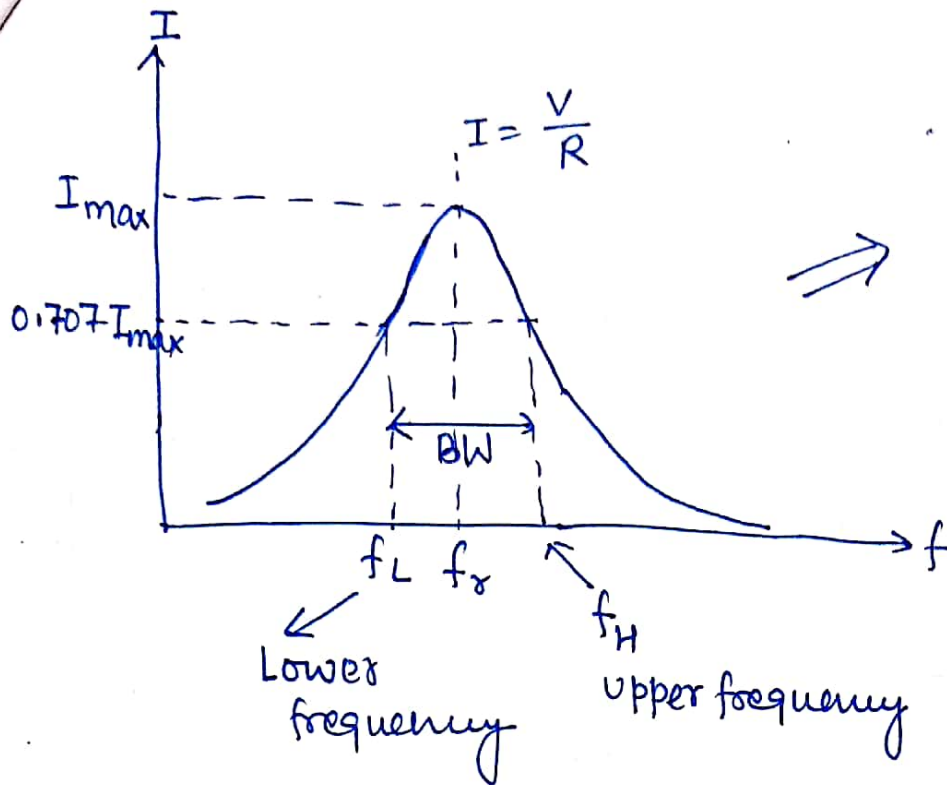

⇒ Current is maximum if  $X_L = X_C$  i.e. at resonance.

Bandwidth,  $BW = f_H - f_L$

where,

$$f_L = \frac{1}{2\pi} \left[ -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \right]$$

$$f_H = \frac{1}{2\pi} \left[ \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \right]$$

Also,  $BW = \frac{f_r}{Q}$

where,  $Q = \frac{\omega_r L}{R} = \frac{2\pi f_r L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$


so,  $BW = \frac{f_r}{Q} = \frac{\frac{1}{2\pi\sqrt{LC}}}{\frac{1}{R}\sqrt{\frac{L}{C}}} = \frac{R}{L} \text{ (rads)} = \frac{R}{2\pi L} \text{ (Hz)}$

$$BW = \frac{f_r}{Q} = f_H - f_L = \frac{R}{2\pi L} \text{ Hz}$$

$$\left. \begin{aligned} V_R &= IR \\ V_L &= I X_L \angle 90^\circ \\ V_C &= I X_C \angle -90^\circ \end{aligned} \right\} \begin{aligned} &= IR \\ &= I \cdot jX_L \\ &= I \cdot (-jX_C) \end{aligned}$$



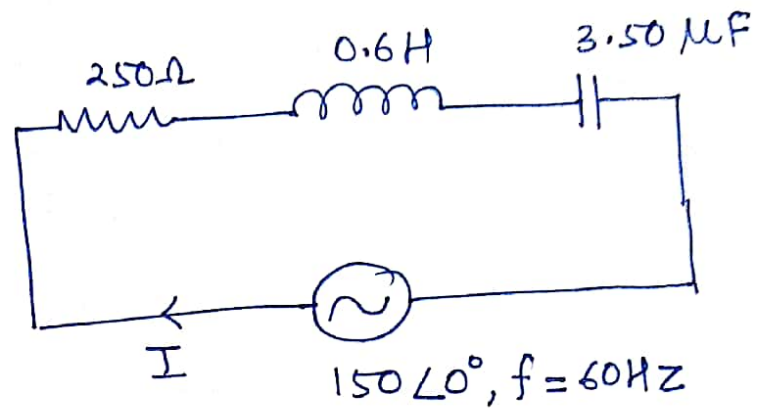Q1. A series RLC circuit is shown in fig. Find (a) the total impedance of the circuit (b) the maximum current in the circuit, (c) the phase angle, (d) the resonant frequency, (e) Quality factor, Q, (f) Bandwidth, and (g) voltage across R, L, and C.



Solution:

$$X_L = 2\pi fL = 2\pi \times 60 \times 0.6 \, \Omega = 226.2 \, \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 60 \times 3.5 \times 10^{-6}} \, \Omega = 757.88 \, \Omega$$

$$(a) \quad Z = R + j(X_L - X_C) = 250 + j(226.2 - 757.88)$$

$X_C > X_L \Rightarrow$  the circuit is capacitive in nature

$$Z = 250 - j531.68 = 587.52 \angle -64.82^\circ$$

(b) max<sup>m</sup> current flow in the circuit at resonance

$$I_{\max} = \frac{150}{250} = \frac{V}{R} = \cancel{0.106} \, 0.6 \, A$$

(c) phase angle,  $\phi = -64.82^\circ$

$$(d) \Rightarrow f_r = \frac{1}{2\pi\sqrt{LC}} = 109.83 \, \text{Hz}$$

$$(e) \quad Q = \frac{X_L}{R} = \frac{226.2}{250} = 0.9048$$

$$(f) \quad BW = \frac{f_r}{Q} = \frac{109.83}{0.9048} = 121.38 \text{ Hz}$$

(g) Total current in the circuit

$$I = \frac{V}{Z} = \frac{150 \angle 0^\circ}{587.52 \angle -64.82^\circ} = 0.255 \angle 64.82^\circ$$


i.e current leads voltage by  $64.82^\circ$ .

$$V_R = IR = 0.255 \times 250 \angle 64.82^\circ \\ = 63.75 \angle 64.82^\circ \text{ volt}$$

$$V_L = I \cdot jX_L = IX_L \angle 90^\circ = 0.255 \times 226.2 \angle 64.82^\circ + 90^\circ \\ = 57.681 \angle 154.82^\circ \text{ volt}$$

$$V_C = I \cdot (-jX_C) = IX_C \angle -90^\circ \\ = 0.255 \angle 64.82^\circ \times 757.88 \angle -90^\circ \\ V_C = 193.2594 \angle -25.18^\circ \text{ volt}$$

## Parallel RLC Resonance Circuit

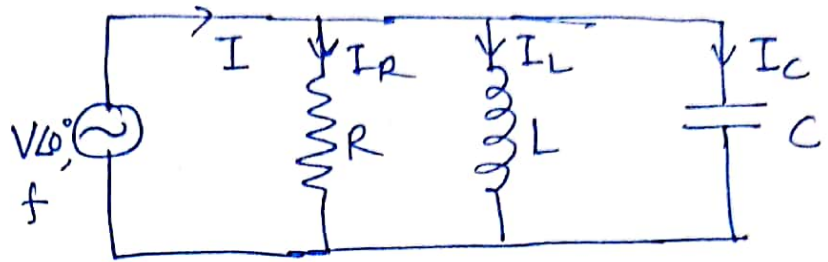

Conductance,  $G = \frac{1}{R}$

Inductive susceptance,  $B_L = \frac{1}{X_L} = \frac{1}{2\pi f L}$

Capacitive susceptance,  $B_C = \frac{1}{X_C} = 2\pi f C$

Admittance,  $Y = \frac{1}{R} + j(B_C - B_L) = G + jB_T$   
 $= G + j(\omega C - \frac{1}{\omega L})$

$$Y = |Y| \angle \phi$$

where,  $|Y| = \sqrt{G^2 + (B_C - B_L)^2} = \sqrt{G^2 + (\omega C - \frac{1}{\omega L})^2}$


$$\phi = \tan^{-1} \left( \frac{B_C - B_L}{G} \right)$$

Similar to series RLC Resonance circuit —

Resonance occurs when  $X_L = X_C$  at  $f = f_r$


Again,  $f_r = \frac{1}{2\pi\sqrt{LC}} \text{ Hz} = \frac{1}{\sqrt{LC}} \text{ (rad)}$
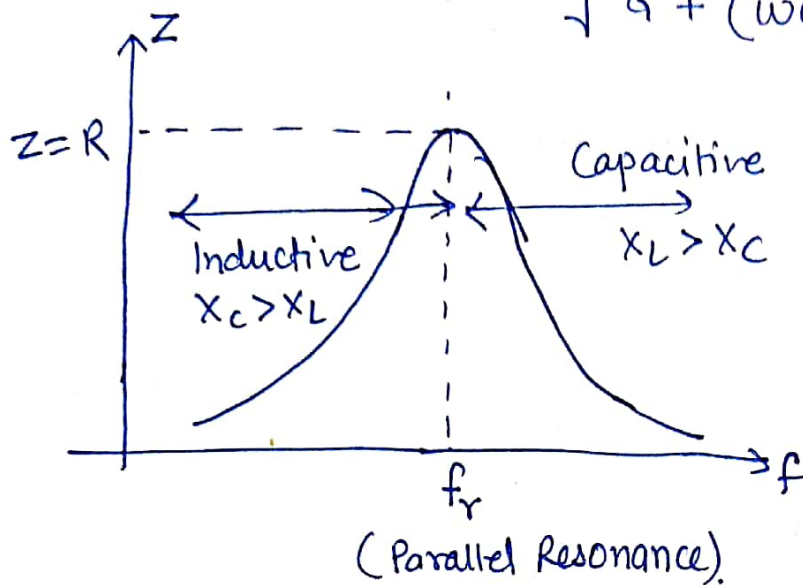
$$\text{Impedance, } Z = \frac{1}{Y} = \frac{1}{\sqrt{G^2 + (\omega C - \frac{1}{\omega L})^2}} \angle \phi$$



The current,  $I = \frac{V \angle 0^\circ}{Z} = V \angle 0^\circ \cdot Y$
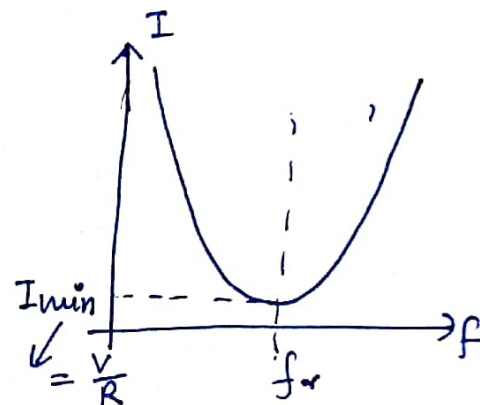
$$I = V \sqrt{G^2 + (\omega C - \frac{1}{\omega L})^2} \angle \phi$$



The current in the circuit is minimum, if  $\omega C = \frac{1}{\omega L}$

$$I_R = \frac{V}{R}$$

$$I_L = \frac{V}{jX_L} = \frac{V}{2\pi f L} \angle -90^\circ$$

$$I_C = \frac{V}{-jX_C} = V \cdot 2\pi f C \angle +90^\circ$$

$$\boxed{I = I_R + I_L + I_C}$$

$I$  = vector sum of  $(I_R, I_L, I_C)$


$$I = \sqrt{I_R^2 + (I_L - I_C)^2}$$

Quality factor,  $Q = \frac{R}{X_L} = \frac{R}{X_C} = R \sqrt{\frac{C}{L}}$

$$BW = f_H - f_L = \frac{f_r}{Q} = \frac{\frac{1}{2\pi\sqrt{LC}}}{\frac{R\sqrt{C}}{L}} = \frac{1}{2\pi\sqrt{LC}} \cdot \frac{\sqrt{L}}{R\sqrt{C}} = \frac{1}{2\pi RC}$$



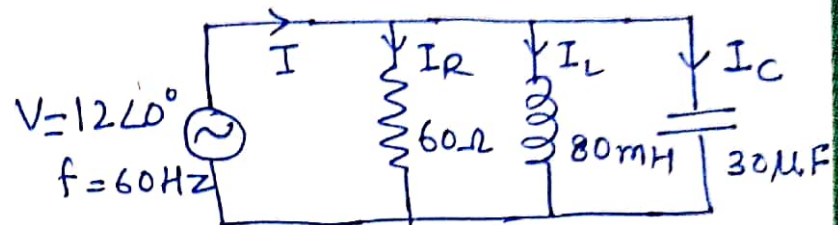Q2. Calculate the impedance in the circuit shown below as well as the current flowing in each element.



Solution:

$$X_L = 2\pi fL = 2\pi \times 60 \times 80 \times 10^{-3} = 30.16\ \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 60 \times 30 \times 10^{-6}} = 88.42\ \Omega$$

$$Z = \frac{1}{\sqrt{\frac{1}{R^2} + \left(\frac{1}{X_L} - \frac{1}{X_C}\right)^2}} = \frac{1}{\sqrt{\left(\frac{1}{60}\right)^2 + \left(\frac{1}{30.16} - \frac{1}{88.42}\right)^2}}$$

$$Z = 36.392\ \Omega \quad \checkmark$$

or,  $G = \frac{1}{R} = 0.0166$

$$B_L = \frac{1}{X_L} = 0.033$$

$$B_C = \frac{1}{X_C} = 0.0113$$

$$\begin{aligned} Y &= G + j(B_C - B_L) \\ &= 0.0166 + j(0.0113 - 0.033) \end{aligned}$$

$$\begin{aligned} Y &= 0.0166 - j0.0217 \quad \checkmark \\ &= 0.0273 \angle -52.58^\circ \\ &= 0.0273 \angle -52.58^\circ \end{aligned}$$

$$Z = \frac{1}{Y} = \frac{1}{0.0273 \angle -52.58^\circ}$$

$$= 36.63 \angle 52.58^\circ \quad \checkmark$$



$$\text{Current, } I = \frac{V}{Z} = \frac{12 \angle 0^\circ}{36.63 \angle 52.58^\circ}$$

$$I = 0.327 \angle -52.58^\circ$$

→ that means current lags voltage by  $52.58^\circ$

$$I_R = \frac{V}{R} = \frac{12}{60} = 0.2 \text{ A}$$

$$I_L = \frac{V}{jX_L} = \frac{12 \angle 0^\circ}{X_L \angle 90^\circ} = \frac{12}{30.16} \angle -90^\circ$$

$$= 0.398 \angle -90^\circ$$

$$I_C = \frac{V}{-jX_C} = \frac{12 \angle 0^\circ}{X_C \angle -90^\circ} = \frac{12}{88.42} \angle +90^\circ$$

$$= 0.136 \angle 90^\circ$$


Also

$$I = \sqrt{I_R^2 + (I_L - I_C)^2} = \sqrt{0.2^2 + (0.398 - 0.136)^2}$$


$$= \underline{0.329 \text{ A}}$$

## Experiment No. 10 (Assignment)

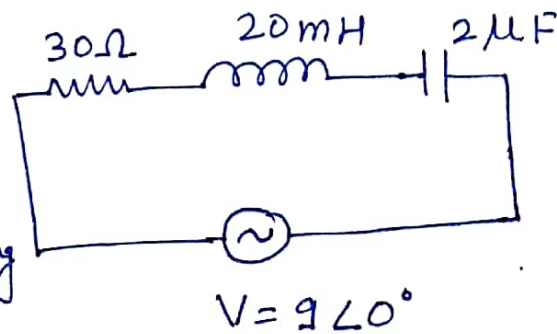Q1. Calculate the resonant frequency, the current at resonant, the voltage across the inductor and capacitor at resonance, the quality factor and the bandwidth of the circuit. Also sketch the corresponding current waveform for all frequencies,



Q2.

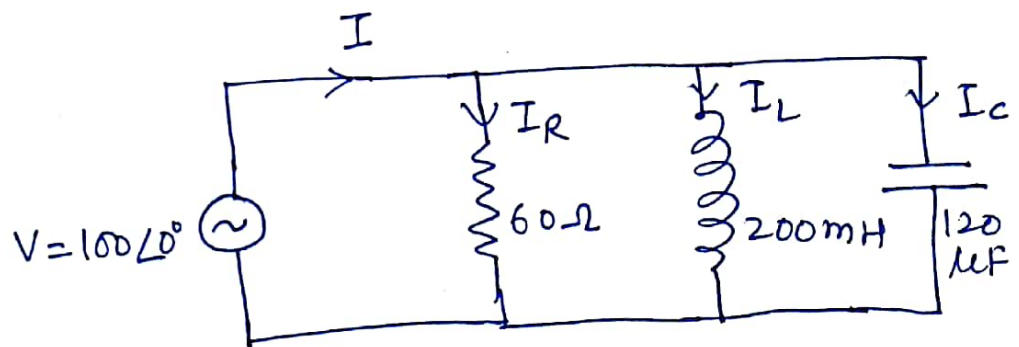

Calculate the resonant frequency, the quality factor, and the bandwidth of the circuit, the circuit current at resonance.