 


# Logic Gates and Circuits

- Drawing Logic Circuit
- Analysing Logic Circuit
- Universal Gates: NAND and NOR
  - ❖ NAND Gate
  - ❖ NOR Gate
- Implementation using NAND Gates
- Implementation using NOR Gates
- Implementation of SOP Expressions
- Implementation of POS Expressions
- Positive and Negative Logic
- Integrated Circuit Logic Families


# Drawing Logic Circuit (1/2)

- When a Boolean expression is provided, we can easily draw the logic circuit.
- Examples:
  - (i)  $F1 = x.y.z'$  (note the use of a 3-input AND gate)




# Drawing Logic Circuit (2/2)

 (ii)  $F2 = x + y'.z$  (if we assume that variables and their complements are available)




(iii)  $F3 = x.y' + x'.z$

 
 
# Analysing Logic Circuit

- When a logic circuit is provided, we can analyse the circuit to obtain the logic expression.
- Example: What is the Boolean expression of F4?



$$F4 = (A'.B'+C)' = (A+B).C'$$

# Universal Gates: NAND and NOR

- **AND/OR/NOT** gates are sufficient for building any Boolean functions.
- We call the set {AND, OR, NOT} a **complete set** of logic.
- However, other gates are also used because:
  - (i) **usefulness**
  - (ii) **economical on transistors**
  - (iii) **self-sufficient**

**NAND/NOR: economical, self-sufficient**  
**XOR: useful (e.g. parity bit generation)**

# NAND Gate (1/2)


- NAND gate is **self-sufficient** (can build any logic circuit with it).
- Therefore, {NAND} is also a **complete set of logic**.
- Can be used to implement AND/OR/NOT.
- IC 7400 (4 NAND Gates)
- Implementing an **inverter using NAND gate**:



$$(x.x)' = x' \quad (\text{T1: idempotency})$$


# NAND Gate (2/2)

- Implementing AND using NAND gates:

 

$$\begin{aligned} ((x.y)' (x.y)')' &= ((x.y)')' && \text{idempotency} \\ &= (x.y) && \text{involution} \end{aligned}$$


- Implementing OR using NAND gates:

 

$$\begin{aligned} ((x.x)' (y.y)')' &= (x'.y')' && \text{idempotency} \\ &= x''+y'' && \text{DeMorgan} \\ &= x+y && \text{involution} \end{aligned}$$
 
# NOR Gate (1/2)

- NOR gate is also self-sufficient.
- Therefore, {NOR} is also a complete set of logic
- Can be used to implement AND/OR/NOT.
- Implementing an inverter using NOR gate:




$$(x+x)' = x' \quad (\text{T1: idempotency})$$




# NOR Gate (2/2)

- Implementing AND using NOR gates:

 

$$\begin{aligned} ((x+x)' + (y+y)')' &= (x' + y')' && \text{idempotency} \\ &= x'' \cdot y'' && \text{DeMorgan} \\ &= x \cdot y && \text{involution} \end{aligned}$$

- Implementing OR using NOR gates:

 

$$\begin{aligned} ((x+y)' + (x+y)')' &= ((x+y)')' && \text{idempotency} \\ &= x+y && \text{involution} \end{aligned}$$

# Implementation using NAND gates (1/2)

- Possible to implement any Boolean expression using NAND gates.

## *Procedure:*

- (i) Obtain **sum-of-products** Boolean expression:

$$\text{e.g. } F3 = x.y' + x'.z$$


- (ii) Use **DeMorgan theorem** to obtain expression using 2-level NAND gates

$$\text{e.g. } F3 = x.y' + x'.z$$

$$= (x.y' + x'.z)' \quad \text{involution}$$

$$= ((x.y')' \cdot (x'.z)')' \quad \text{DeMorgan}$$

## Implementation using NAND gates (2/2)

 

$$F3 = ((x . y')' . (x'.z)')' = x . y' + x'.z$$

# Implementation using NOR gates (1/2)

- Possible to implement any Boolean expression using NOR gates.

## *Procedure:*

- (i) Obtain **product-of-sums** Boolean expression:

$$\text{e.g. } F6 = (x+y')(x'+z)$$


- (ii) Use **DeMorgan theorem** to obtain expression using 2-level NOR gates.

$$\text{e.g. } F6 = (x+y')(x'+z)$$

$$= ((x+y')(x'+z))' \quad \text{involution}$$

$$= ((x+y')' + (x'+z)')' \quad \text{DeMorgan}$$

# Implementation using NOR gates (2/2)

 


$$F6 = ((x+y')' + (x'+z)')' = (x+y').(x'+z)$$

# Implementation of SOP Expressions (1/2)

- Sum-of-Products expressions can be implemented using:
  - ❖ 2-level AND-OR logic circuits
  - ❖ 2-level NAND logic circuits

- AND-OR logic circuit

 



$$F = A.B + C.D + E$$

# Implementation of SOP Expressions (2/2)

- NAND-NAND circuit (by circuit transformation)


a) add double bubbles

  b) change **OR-with-inverted-inputs to NAND**  
& bubbles at inputs to their complements


 
# Implementation of POS Expressions (1/2)

- Product-of-Sums expressions can be implemented using:
  - ❖ 2-level OR-AND logic circuits
  - ❖ 2-level NOR logic circuits
- OR-AND logic circuit




$$G = (A+B).(C+D).E$$



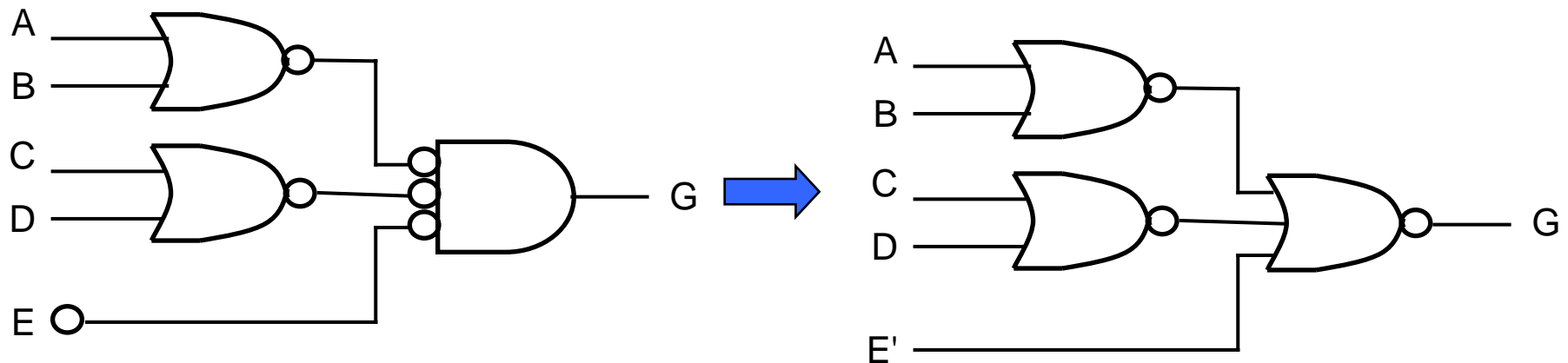
# Implementation of POS Expressions (2/2)

- NOR-NOR circuit (by circuit transformation):
  - a) add double bubbles
  - b) changed AND-with- inverted-inputs to NOR & bubbles at inputs to their complements



# XOR Gate(Exclusive-OR Gate)

 


Output is HIGH whenever two inputs are at opposite levels.


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

(b) The truth table.

# Logic circuit of XOR Gate

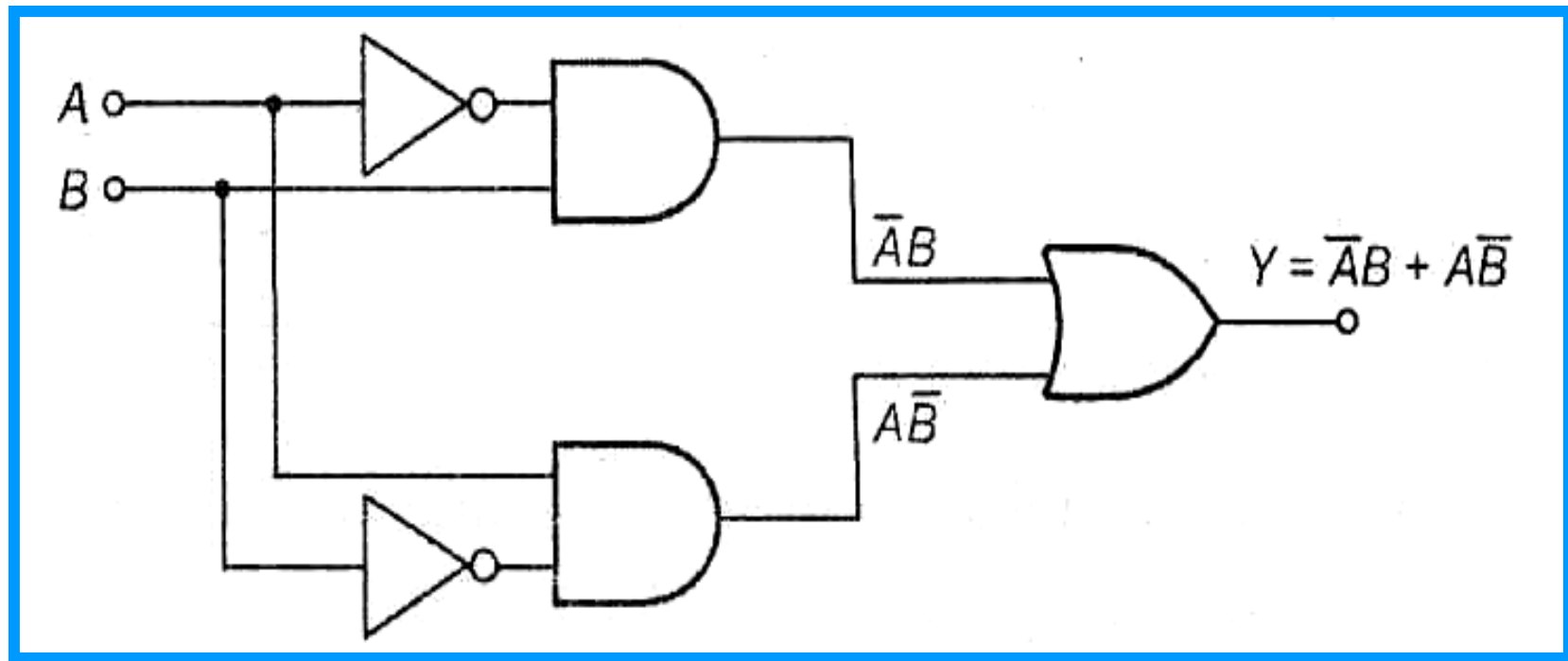

# XNOR Gate(Exclusive-NOR Gate)

 


Output is HIGH whenever two inputs are at same level.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

(b) The truth table.

# Logic circuit of XNOR Gate

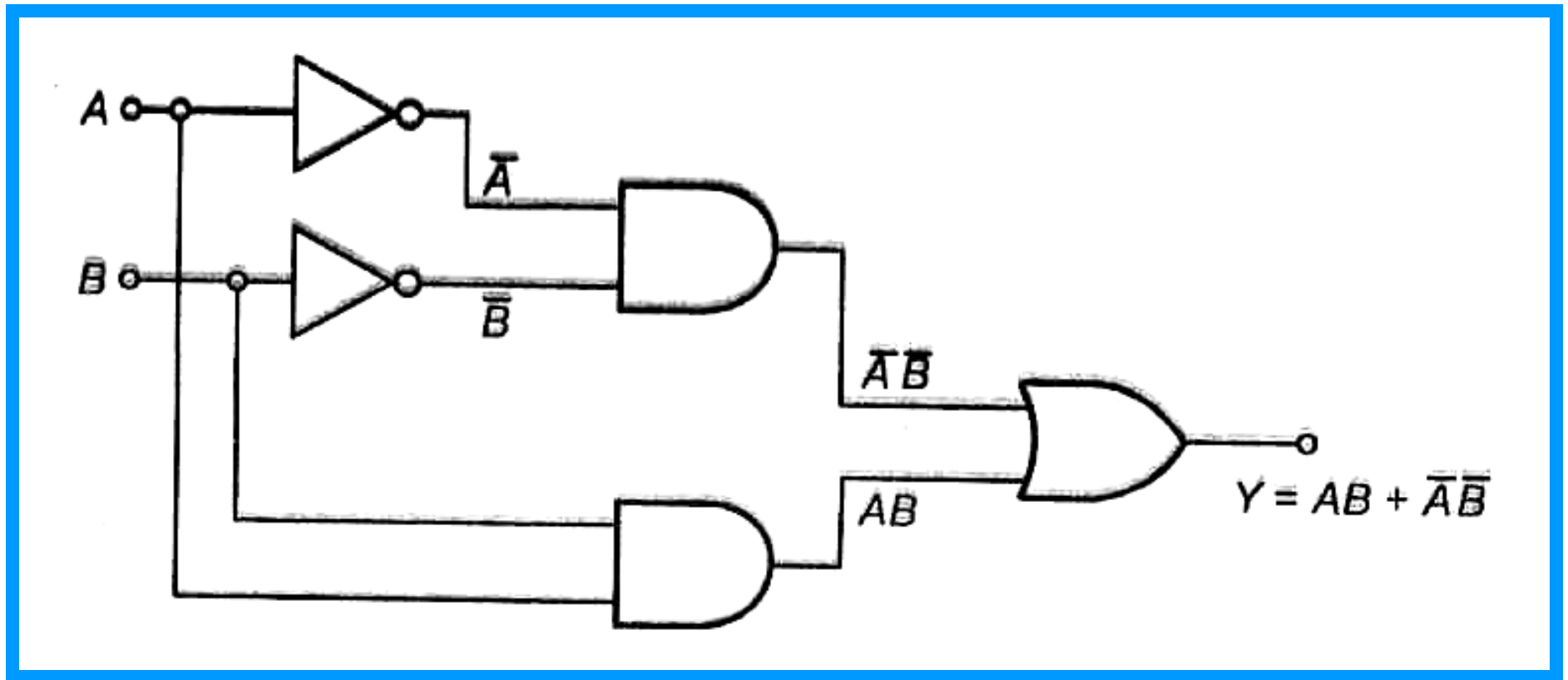

# Positive & Negative Logic (1/2)

- In logic gates, usually:
  - ❖ H (high voltage, 5V) = 1
  - ❖ L (low voltage, 0V) = 0
- This convention is known as **positive logic**.
- However, the reverse convention, **negative logic** possible:
  - ❖ H (high voltage) = 0
  - ❖ L (low voltage) = 1
- Depending on convention, same gate may denote different Boolean function.

# Positive & Negative Logic (2/2)

- A signal that is set to logic 1 is said to be *asserted*, or *active*, or *true*.
- A signal that is set to logic 0 is said to be *deasserted*, or *negated*, or *false*.
- Active-high signal names are usually written in uncomplemented form.
- Active-low signal names are usually written in complemented form.

# Summary

