

Tutorial Sheet -3

1. The adjustable resistor of Fig. 1 can be varied from 0 to 100 k Ω . Calculate the minimum and maximum closed-loop voltage gain. (Ans. : -1, -101)

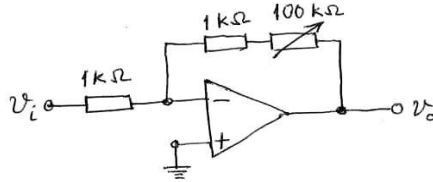


Fig 1

2. Three signals drive the summing amplifier as shown below. What is the output voltage? (Ans. - 3.1 V)

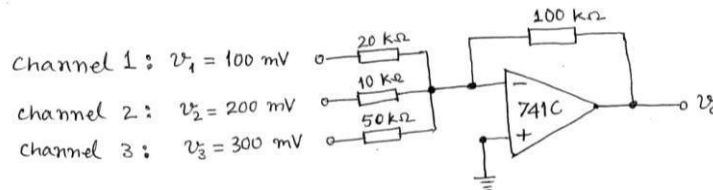


Fig. 2

3. Determine the output voltage V_{out} shown below Fig 3 (Ans. : -3.049 V)

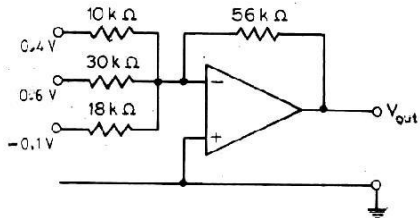


Fig. 3

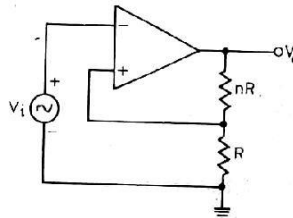


Fig. 4

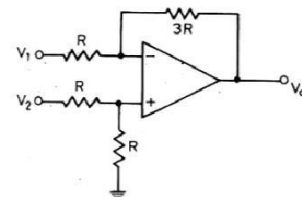


Fig. 5

4. Show that the gain of the op-amp circuit shown in Fig 4, is $n + 1$.
5. Determine the value of V_o in the circuit of Fig.5, in terms of inputs V_1 and V_2 . (Ans. : $2V_2 - 3V_1$)
6. Find out the output voltage V_o in Fig. 6 and Fig. 7.

(Ans: $V_o = 4V, -6V$)

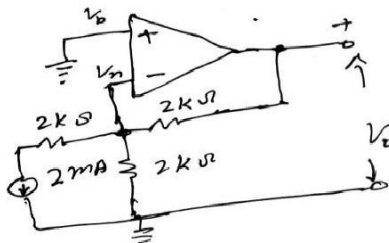


Fig. 6.

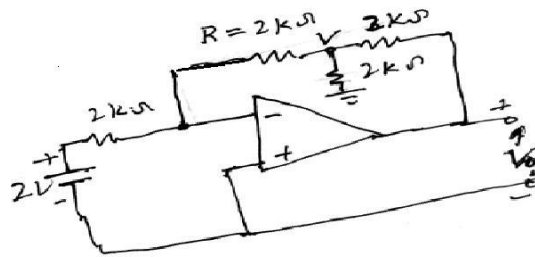


Fig. 7.