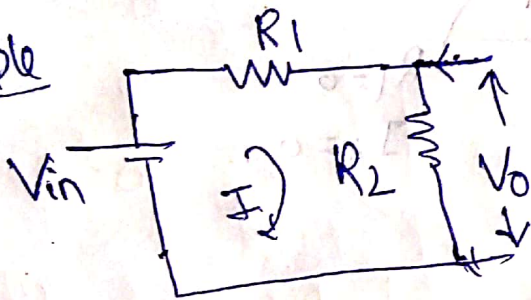


# 

loading effect take place in Voltmeter and Ammeter.

We know that for Voltmeter-

Example




$$I = \frac{V_{in}}{R_1 + R_2}$$

$$V_0 = I \times R_2$$


$$V_0 = \frac{V_{in} R_2}{R_1 + R_2}$$

True value


This circuit has without Voltmeter

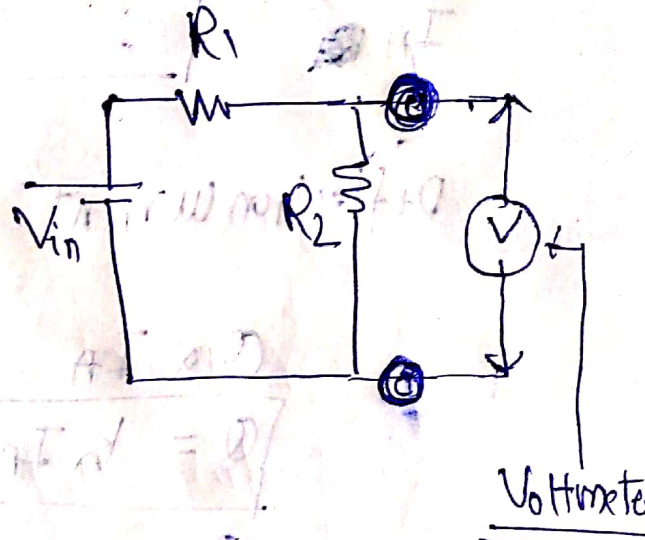

Voltmeter (concept):

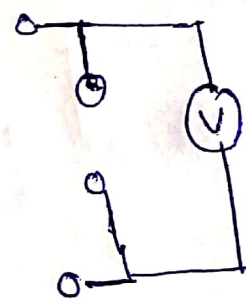


Ideal

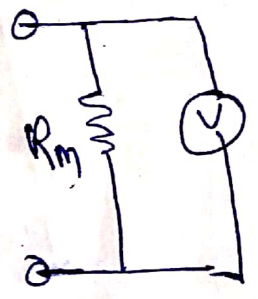


Practical

Again draw the circuit. Since, the voltmeter consists of internal resistance  $R_m$  in practical and  $R_m = \infty$  (open) in ideal

Apply practical condition of voltmeter

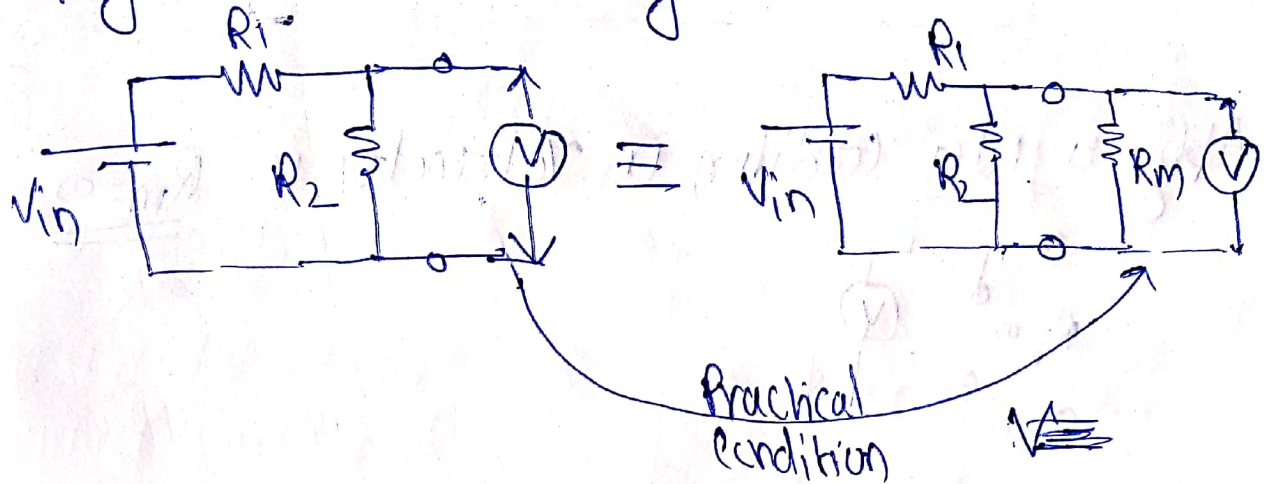
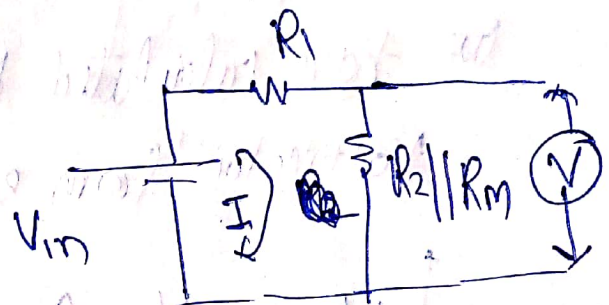
$$I = \frac{V_{in}}{R_1 + (R_2 \parallel R_m)} \quad \text{--- (I)}$$



and  $V = I \times (R_2 \parallel R_m)$  --- (II)

Put the value of  $I$  in equation II

$$V = \frac{V_{in} (R_2 \parallel R_m)}{R_1 + (R_2 \parallel R_m)} \quad \text{--- (III)}$$

↓  
measured value

Therefore, you can see, there is true value and measured value, which is not equal.


i.e

$$V_0 = \frac{V_{in} R_2}{R_1 + R_2} \neq V = \frac{V_{in} (R_2 \parallel R_m)}{R_1 + (R_2 \parallel R_m)}$$



ie.  $V_{\text{(measured)}} \neq V_0 \text{ (true)}$

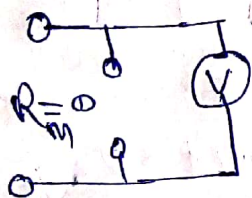Apply a ideal condition in voltmeter ie.  $R_m = \infty$



we have calculated the practical value read by Voltmeter from equation (ii) which is

$$V = \frac{V_{in} (R_2 \parallel R_m)}{R_i + (R_2 \parallel R_m)}$$

or

$$V = \frac{V_{in} \left( \frac{R_2 \times R_m}{R_2 + R_m} \right)}{R_i + \frac{R_2 \times R_m}{R_2 + R_m}} = \frac{(R_2 + R_m) \cdot V_{in} (R_2 R_m)}{R_i (R_2 + R_m) + R_2 R_m}$$

$$V = \frac{\left( \frac{R_2}{R_m} + 1 \right) \cdot (V_{in} R_2)}{\frac{R_i R_2}{R_m} + \frac{R_i R_m}{R_m} + R_2}$$

Put  $R_m = \infty$  for ideal voltmeter in above expression



$$V = \frac{V_{in} R_2}{R_1 + R_2}$$

i.e. At ideal condition -

$$\text{True value} = \text{measured value}$$

$$V_0 = \frac{V_{in} R_2}{R_1 + R_2} \equiv V = \frac{V_{in} R_2}{R_1 + R_2}$$

$$\text{Error} = \text{True value} - \text{measured value} \\ = 0$$

Summary: loading effect is a <sup>phenomenon</sup> ~~phenomenon~~, it happened due to presence of internal resistance of voltmeter. It can overcome by increasing the value of internal resistance.


$$\text{i.e. } R_m \uparrow \text{ loading effect } \downarrow$$

Note i.e. the voltmeter resistance should be high as much as possible




# loading effect in Ammeter

Example:

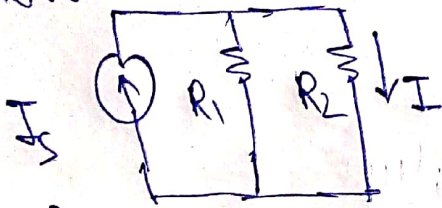


$$I = \frac{I_s \times R_1}{R_1 + R_2} \quad \text{--- (1)}$$

True value

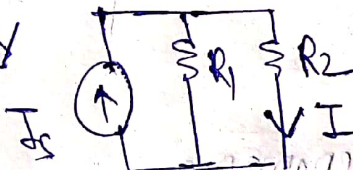


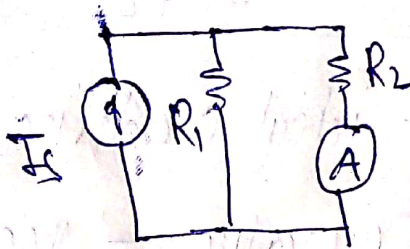Note: This circuit has without Ammeter i.e no internal resistance




(A) = Ammeter which is used to measure the current


We know that

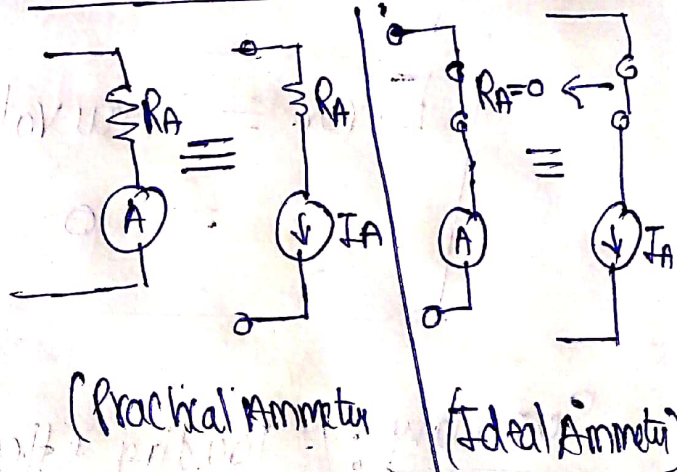

Apply Practical Ammeter first

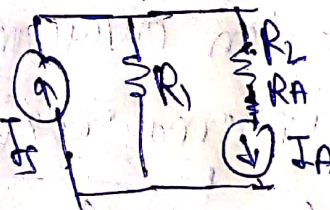

0V

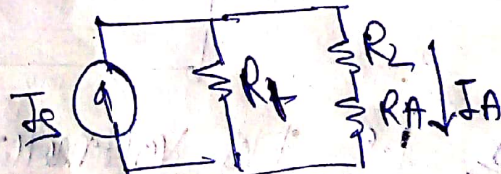

Measured value

$$I_A = \frac{I_s R_1}{R_1 + R_2 + R_A} \quad \text{--- (2)}$$



we can see that true value is not equal to measured value. Therefore, load effect taking place which is happen due to presence of internal resistance.

i.e.

$$I = \frac{I_s \times R_1}{R_1 + R_L}$$

↓  
True value

≠

$$I_A = \frac{I_s \times R_1}{R_1 + R_2 + R_A}$$

↓  
Measured value

⇒ How to overcome the load effect.

It is possible only when neglect the internal resistance of Ammeter i.e.  $R_A = 0$

We have, 
$$I_A = \frac{I_S \times R_1}{R_1 + R_2 + R_A} = \frac{I_S \times R_1}{R_1 + R_2}$$

$$I_A = \frac{I_{SY} R_1}{R_1 + R_L}$$

Under this condition — True value = measured value

$$I = \frac{I_s \times R_1}{R_1 + R_2} \Rightarrow I_A = \frac{I_s \times R_1}{R_1 + R_2}$$