

Solution of Tutorial 9

Q1. A 40KVA single phase transformer has 400 turns on primary and 100 turns on secondary the primary is

connected to 200V, 50Hz supply, Determine

- 1) The secondary voltage on open circuit.
- 2) The current flowing through the two windings on full load.
- 3) The maximum value of flux.

Solution: Tr, rating=40KVA, $N_1=400$, $N_2=100$

- 1) Secondary voltage on open circuit: V_2

Primary induced voltage $V_1=200V$,

- 1) Secondary voltage on open circuit: V_2

$$\frac{V_2}{V_1} = \frac{N_1}{N_2}$$
$$V_2 = \frac{N_1}{N_2} * V_1 = 2000 * \frac{100}{400} = 500 \text{ volts}$$

- 2) Primary Current (I_1): at full load,

$$I_1 = \frac{KVA * 100}{V_1} = 40 * \frac{1000}{200} = 20A$$

secondary current at full load $I_2 = \frac{KVA * 100}{V_2} = 40 * \frac{1000}{500} = 80A$

- 3) Maximum value of flux

$$\text{EMF equation } E = 4.44 f N_1 \Phi_m$$

$$\Phi_m = \frac{V_1}{4.44 * f * N_1} = \frac{200}{4.44 * 50 * 200} = 0.022 \text{ wb}$$

2)

Q2

The equivalent parameters of a transformer, having a turns ratio of 5, are $R_1=0.5\Omega$, $R_2=0.021\Omega$, $X_1=3.2\Omega$, $X_2=0.12\Omega$, $R_c=350\Omega$, and $X_m=98\Omega$. Draw the approximate equivalent circuit of the transformer, referred to


- The primary
- The secondary.

Solution

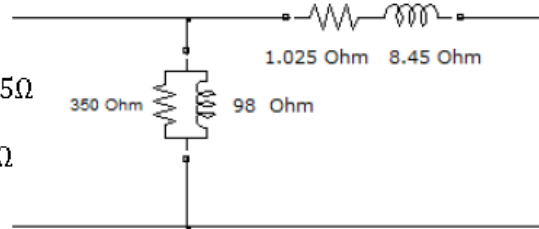a) Referred to primary

$$R_{eq} = R_1 + a^2 R_2 = 0.5 + 5^2(0.021) = 1.025\Omega$$

$$X_{eq} = X_1 + a^2 X_2 = 3.2 + (5)^2(0.12) = 6.2\Omega$$




b) Referred to secondary

$$R_{eq} = \left(\frac{1}{a^2}\right) R_1 + R_2 = \left(\frac{1}{25}\right) 0.5 + (0.021) = 0.041\Omega$$

$$X_{eq} = \left(\frac{1}{a^2}\right) X_1 + X_2 = \left(\frac{1}{25}\right) 3.2 + (0.12) = 0.248\Omega$$

$$R_c' = \left(\frac{1}{a^2}\right) R_c = \left(\frac{1}{25}\right) 350 = 14\Omega$$
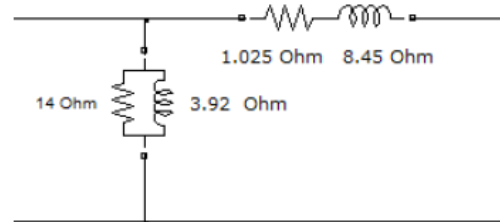
$$X_m' = \left(\frac{1}{a^2}\right) X_m = \left(\frac{1}{25}\right) 98 = 3.92\Omega$$



Q3


A 15-kVA, 2400:240-V, 60 Hz transformer has the following equivalent circuit parameters:

$$\begin{array}{lll} R_1 = 2.5\Omega & R_2 = 0.025\Omega & X_1 = 7\Omega \\ X_2 = 0.07\Omega & R_c = 32\text{ k}\Omega & X_m = 11.5\text{ k}\Omega \end{array}$$

If the transformer is supplying a 10-kW, 0.8 PF lagging load at rated voltage, assuming the output voltage is the reference, **draw** the transformer's **exact** equivalent circuit referred to the primary (H.V) side and use it to **calculate**:

- The input current
- The input voltage
- The input power factor

Solution

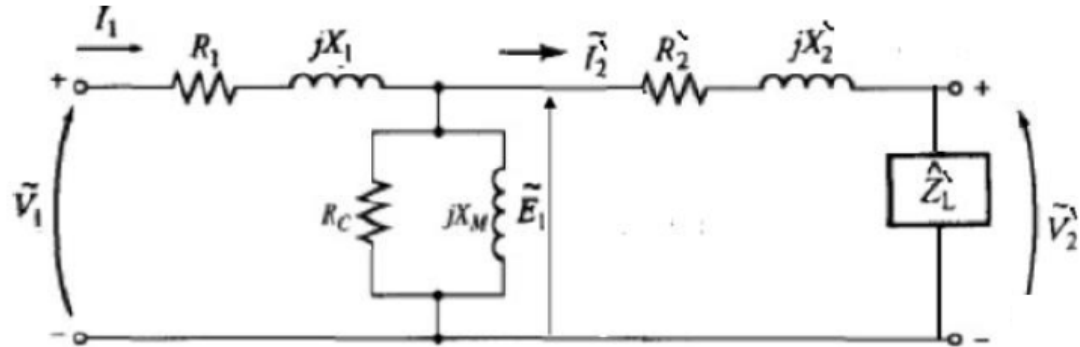

1. The input current

$$\vec{I}_1 = \vec{I}_o + \vec{I}_2'$$

$$|\vec{I}_2'| = \frac{P_{load}}{|\vec{V}_2'| * pf} = \frac{10 * 10^3}{2400 * 0.8} = 5.2 \text{ Amp}$$

$$\vec{I}_2' = |\vec{I}_2'| \angle (-\cos^{-1}(p.f)) = 5.2 \angle -\cos^{-1}(0.8) = 5.2 \angle -36.87 \text{ Amp}$$

$$\vec{I}_o = \frac{\vec{E}_1}{R_c // X_m}$$

$$\vec{E}_1 = \vec{V}_2' + \vec{I}_2'(R_2' + jX_2')$$

$$= 2400 \angle 0 + 5.2 \angle -36.87 (10^2 * 0.025 + j10^2 * 0.07)$$

$$= 2432.4 \angle 0.5 \text{ volt}$$

$$R_c // X_m = \frac{R_c * X_m}{R_c + X_m} = \frac{32 * 10^3 * j11.5 * 10^3}{32 * 10^3 + j11.5 * 10^3} = 10.82 \angle 70.23 \text{ k}\Omega$$

$$\vec{I}_o = \frac{2432.4 \angle 0.5}{10822 \angle 70.23} = 0.2247 \angle -69.73 \text{ Amp}$$

$$\vec{I}_1 = 0.2247 \angle -69.73 + 5.2 \angle -36.87 = 5.4 \angle -38.16 \text{ Amp}$$

2. The input voltage

$$\begin{aligned}\bar{V}_1 &= \bar{E}_1 + \bar{I}_1(R_1' + jX_1') \\ &= 2432.4\angle 0.5 + 5.4\angle -38.16 (2.5 + j7) \\ &= 2466.6\angle 0.99 \text{ volt}\end{aligned}$$

3. The input power factor

$$\begin{aligned}pf_{inp} &= \cos(\angle \bar{V}_1 - \angle \bar{I}_1) \\ &= \cos(0.99 + 38.16) \\ &= 0.775\end{aligned}$$

Q


The parameters of a 2300/230 V, 50Hz transformer are given below:

$$\begin{array}{lll}R_1 = 0.286 \, \Omega & R_2' = 0.319 \, \Omega & X_1 = 0.73 \, \Omega \\ X_2' = 0.73 \, \Omega & R_c = 250 \, \Omega & X_m = 1250 \, \Omega\end{array}$$

The secondary load impedance is $Z_L = 0.387 + j 0.29$. Draw the exact equivalent circuit with the normal voltage across the primary (H.V side) and use it to find:

1. Secondary voltage
2. Input power factor
3. Power input.
4. Power output
5. Primary copper loss
6. Secondary copper loss
7. Core loss

Solution

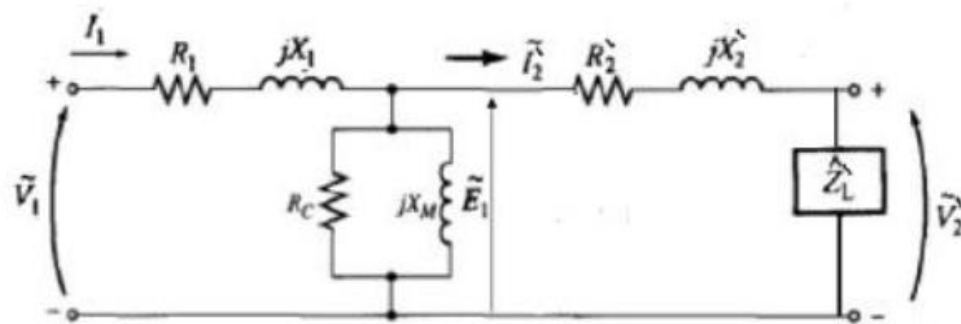


$$Z_L = 0.387 + j 0.29 \quad a = 2300/230 = 10$$

Since V_1 is rated value:

$$V_1 = 2300 \text{ V}$$

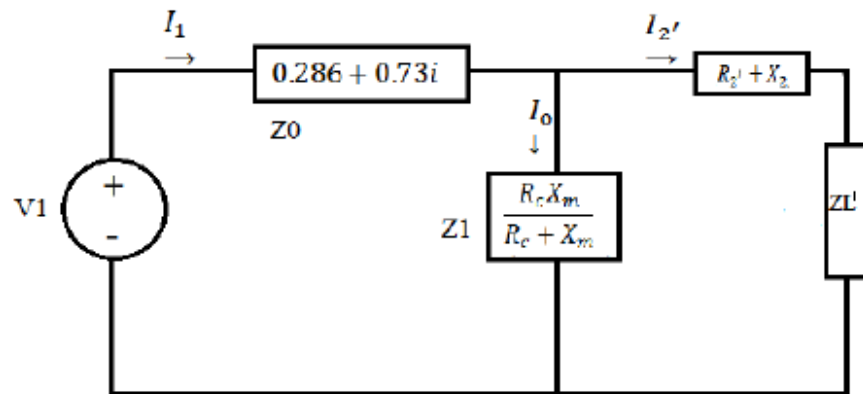
$$Z_{L'} = a^2 Z_L = 38.7 + 29i = 48.36 \angle 36.84^\circ$$



$$Z_1 = \frac{R_c X_m}{R_c + X_m} = 240.58 + 48i = 245.32 \angle 11.28$$

$$Z_2 = (R_2' + X_2) + Z_{L'} = 39.02 + 29.73i = 49.055 \angle 37.3$$
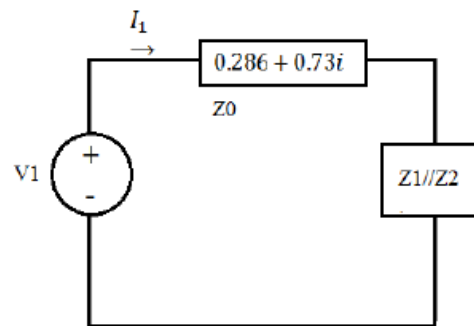
$$Z_0 = 0.286 + 0.73i = 0.784 \angle 68.6$$



$$I_1 = \frac{V_1}{Z_{eq}} = 45.46 - 30.29i = 54.6 \angle -33.67^\circ$$

$$I_0 = I_1 \frac{Z_2}{Z_2 + Z_1} = 9 - 1.9i = 21 \angle -64.65^\circ$$

$$I_2' = I_1 - I_0 = 36.42 - 28.38i = 46.17 \angle -37.9^\circ$$

1. Secondary Voltage

$$V_{2'} = I_{2'} Z_{l'} = 2232.678 - 41.856i = 2233 \angle -1.07^\circ V$$

$$V_2 = \frac{V_{2'}}{a} = 223.3 - 4.1698i = 223.3 \angle -1.07^\circ V$$

2. Input p.f

$$p.f = \cos(V_{1angle} - I_{1angle}) = \cos(33.6) = 0.8329 \text{ lag}$$

3. Power Input:

$$|I_1| |V_1| \cos(-33.6) = 104.4 \text{ kW}$$

4. Power Output:

$$|I_2| |V_2| \cos(\varphi_2) = 80.1 \text{ kW}$$

5. Power loss (copper):

$$\text{Primary: } |I_1|^2 R_1 = 858.8 \text{ W}$$

$$\text{Secondary } |I_{2'}|^2 R_{2'} = 683.3 \text{ W}$$

6. Power loss (core):

$$P = |I_0|^2 R_c = 20.5 \text{ kW}$$

Q

The equivalent parameters of a 150kVA, 2400V/240V transformer, are $R_1=0.2\Omega$, $R_2=2\text{m}\Omega$, $X_1=0.45\Omega$, $X_2=4.5\text{m}\Omega$, $R_c=10\text{k}\Omega$, and $X_m=1.55\text{k}\Omega$. The transformer is operating at rated load and rated voltage with 0.8 lagging power factor. Using the approximate equivalent circuit referred to the primary side, determine:

1. Voltage regulation.
2. The transformer power loss.
3. Efficiency.

Solution

Using the approximate circuit we can get:

$$R_{eq} = R_1 + a^2 R_2 = 0.2 + (10)^2 * (2) * 10^{-3} = 0.4 \Omega$$

$$X_{eq} = X_1 + a^2 X_2 = 0.45 + (10)^2 * (4.5) * 10^{-3} = 0.9 \Omega$$

$$P_{core} = \frac{V_1^2}{R_c} = \frac{2400^2}{10 * 10^3} = 5.76 \text{ w}$$

Ac
Go

$$P_{cu fl} = (I_{2 fl})^2 R_{eq} = \left(\frac{S_{fl}}{V_2}\right)^2 R_{eq} = \left(\frac{150 * 10^3}{2400}\right)^2 (0.4) = 1562.5 \text{ w}$$

$$X = \text{load factor} = 1 \text{ (because stated at rated load)}$$

$$pf = \text{power factor} = \cos(\phi) = 0.8 \text{ lag}$$

1. Voltage Regulation

$$\begin{aligned} \varepsilon &= \frac{X \cdot S_{rated}}{|V_2|^2} [R_{eq} \cos \phi + X_{eq} \sin \phi] \\ &= \frac{(1)(150 * 10^3)}{(2400)^2} [(0.4)(0.8) + (0.9) \sin((\cos^{-1} 0.8))] \\ &= 2.24 \% \end{aligned}$$

2. Transformer Power loss

$$\begin{aligned}P_{loss} &= P_{core} + X^2 P_{cu fl} \\&= 576 + 1^2(1562.5) \\&= 2.1385 \text{ Kw}\end{aligned}$$

3. Efficiency

$$\begin{aligned}\eta &= \frac{XS_{rated} \cos \phi}{XS_{rated} \cos \phi + P_{core} + X^2 P_{cu fl}} \\&= \frac{(1)(150 * 10^3)(0.8)}{(1)(150 * 10^3)(0.8) + 576 + 1^2(1562.5)} \\&= 98.25 \%\end{aligned}$$

q

The equivalent parameters of a 110kVA, 2200V/110V transformer, are $R_1=0.22\Omega$, $R_2=0.5m\Omega$, $X_1=2\Omega$, $X_2=5m\Omega$, $R_c=5494.5\Omega$, and $X_m=1099\Omega$. Using the approximate equivalent circuit referred to the primary side, when the transformer is operating at 80% full load with unity power factor determines:

1. Voltage regulation.
2. The transformer power loss.
3. Efficiency.

Solution

Using the approximate circuit we can get:

$$R_{eq} = R_1 + a^2 R_2 = 0.22 + (20)^2 (0.5 * 10^{-3}) = 0.42 \Omega$$

$$X_{eq} = X_1 + a^2 X_2 = 2 + (20)^2 (5 * 10^{-3}) = 4 \Omega$$

$$P_{core} = \frac{V_1^2}{R_c} = \frac{2200^2}{5494.5} = 880.88 \text{ w}$$

$$P_{cu\ fl} = (I_2\ fl)^2 R_{eq} = \left(\frac{S_{fl}}{V_2}\right)^2 R_{eq} = \left(\frac{110 * 10^3}{2200}\right)^2 (0.42) = 1050 \text{ w}$$

$X = \text{load factor} = 0.8$ (because stated 80% full load)

$pf = \text{power factor} = \cos(\phi) = 1$ (because stated unity power factor)

1. Voltage Regulation

$$\varepsilon = \frac{X \cdot S_{rated}}{|V_2|^2} [R_{eq} \cos \phi + X_{eq} \sin \phi]$$

$$\varepsilon = \frac{(0.8 * 110 * 10^3)}{(2200)^2} [(0.42)(1) + (4)(0)] = 0.76 \%$$

2. Transformer Power loss

$$\begin{aligned} P_{loss} &= P_{core} + X^2 P_{cu\ fl} \\ &= 880.88 + 0.8^2 * 1050 \\ &= 1.55 \text{ Kw} \end{aligned}$$

3. Efficiency

$$\begin{aligned} \eta &= \frac{XS_{rated} \cos \phi}{XS_{rated} \cos \phi + P_{core} + X^2 P_{cu\ fl}} \\ \eta &= \frac{0.8 * (110 * 10^3)}{0.8 * (110 * 10^3) + 880.88 + 0.8^2 * 1050} \\ &= 98.26\% \end{aligned}$$

Q

A 120 KVA, 2400/240 volt transformer has the following parameters:

$R_1=0.75 \text{ ohm}$, $X_1=0.8 \text{ ohm}$, $R_2=0.0045 \text{ ohm}$, $X_2=0.008 \text{ ohm}$

The total transformer losses at full load is 4 kW and the load that achieve the transformer maximum efficiency is 57.73% of the rated load. calculate:

1. The equivalent impedance referred to the primary.
2. The iron and full load copper losses.
3. The transformer maximum efficiency at 0.8 p.f lag.
4. The transformer voltage regulation at the loading conditions mentioned in 3.

Solution

1. The equivalent impedance referred to the primary.

$$R_{eq} = R_1 + a^2 R_2 = 0.75 + (10)^2 (0.0045) = 1.2 \Omega$$

$$X_{eq} = X_1 + a^2 X_2 = 0.8 + (10)^2 (0.008) = 1.6 \Omega$$

2. The iron and full load copper losses.

$$P_{loss fl} = P_{core} + P_{cu fl} = 4 \text{ Kw} \rightarrow (1)$$

$$X_{\eta_{max}} = \sqrt{\frac{P_{core}}{P_{cu fl}}} = 0.5773 \rightarrow (2)$$

Solving (1) and (2) we get

$$P_{core} = 1 \text{ Kw} \quad P_{cu fl} = 3 \text{ Kw}$$

3. The transformer maximum efficiency at 0.8 p.f lag.

$$\eta_{max} = \frac{X_{\eta_{max}} S_{rated} \cos \phi}{X_{\eta_{max}} S_{rated} \cos \phi + P_{core} + X_{\eta_{max}}^2 P_{cu fl}}$$

$$\begin{aligned} \eta_{max} &= \frac{(0.5773)(120 * 10^3)(0.8)}{(0.5773)(120 * 10^3)(0.8) + 1 * 10^3 + (0.5773)^2 (3 * 10^3)} \\ &= 96.57\% \end{aligned}$$

- 4. The transformer voltage regulation at the loading conditions mentioned in 3.**

$$\begin{aligned}\varepsilon &= \frac{X_{\eta_{max}} \cdot S_{rated}}{|V_2|^2} [R_{eq} \cos \phi + X_{eq} \sin \phi] \\ &= \frac{(0.5773)(120 * 10^3)}{(2400)^2} [(1.2)(0.8) + (1.6) \sin((\cos^{-1} 0.8))] \\ &= 2.3 \text{ \%}\end{aligned}$$