


Jaypee Institute of Information Technology
Electronics & Communication Engineering
Electronics Science - I (ISB/IEC/III)

Tutorial 8

- Que 1 [03] A series resonance network, consisting of a resistor of ~~300 Ω~~ 30Ω , a capacitor of $2 \mu F$ and an inductor of 20 mH is connected across a sinusoidal supply voltage which has a constant output of 9 volts at all frequencies. Calculate, the resonant frequency, the ~~Circuit~~ Current at resonance, the voltage across the inductor and capacitor at resonance, the quality factor and Band Width of the circuit. Also find the upper and lower -3 dB frequency points f_H & f_L .
- Que 2 [03] A series circuit consists of a resistance of 4Ω , an inductance of 500 mH and a variable capacitance connected across a 100 V , 50 Hz supply. Calculate the capacitance required to produce a series resonance condition and the voltage generated across both the inductor and the capacitor at the points of resonance.
- Que 3 [03] A parallel resonance network, consisting of a resistor of ~~600~~ 60Ω , a capacitor of $120 \mu F$ and an inductor of 200 mH is connected across a sinusoidal supply voltage which has a constant output of 100 volts at all frequencies. Calculate, the resonant frequency, the quality factor and Band Width of the circuit, the Circuit Current at resonance ~~how...~~

Ques 4.
[C03]

A constant voltage of frequency, 1 MHz is applied to a lossy inductor (r in series with L), in series with a variable capacitor C (Fig below). The current drawn is maximum when $C = 400\text{ pF}$, while current is reduced to $(\frac{1}{\sqrt{2}})$ of the above value, when $C = 450\text{ pF}$. Find the value of r and L . Calculate the quality factor of the coil and the bandwidth.

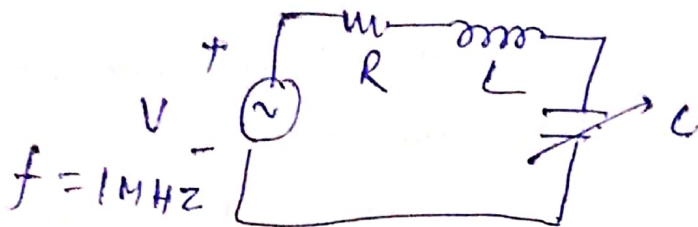

Ques 5.

[C03]

A coil having a resistance of 15Ω and an inductance of 0.75 H , is connected in series with a capacitor (Fig 5.1). The circuit draws maximum current, when a voltage of 200 V at 50 Hz is applied. A second capacitor is then connected in parallel to the circuit (Fig 5.2). What should be its value such that the combination acts like a non-inductive resistance, with same voltage (200 V) at 100 Hz ? Calculate the current drawn by the two circuits too.

