

Topic : Voltmeter and Ammeter

Voltmeter

Ideal
Practical

Voltmeter is use for measuring the voltage or open circuit voltage

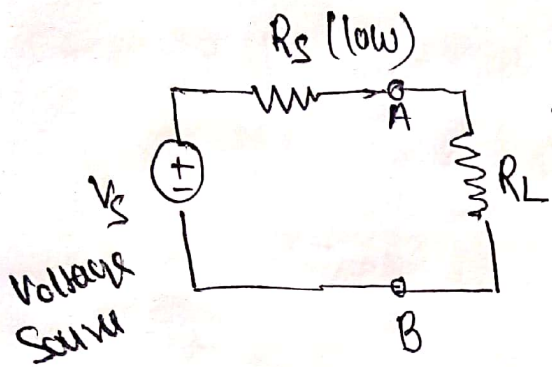


Fig. (a)

Practical voltage Source

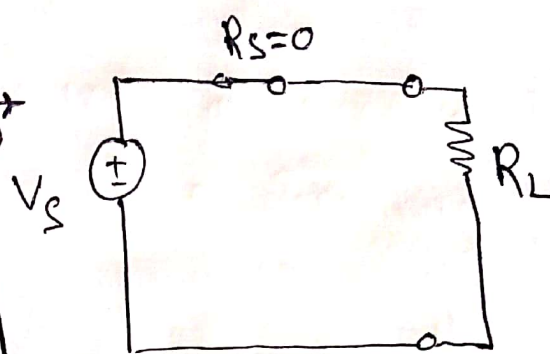


Fig. (b)

Ideal Voltage Source

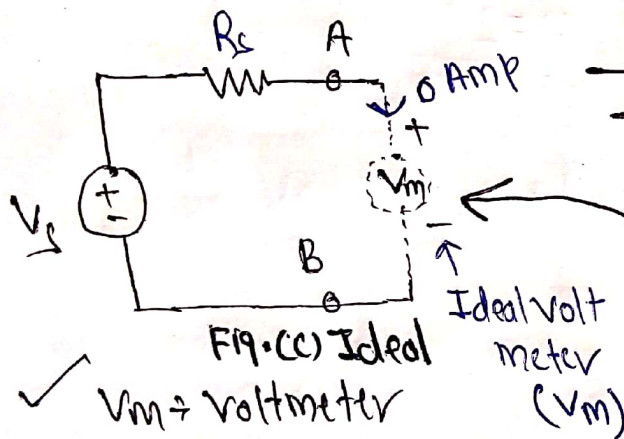


Fig. (c) Ideal

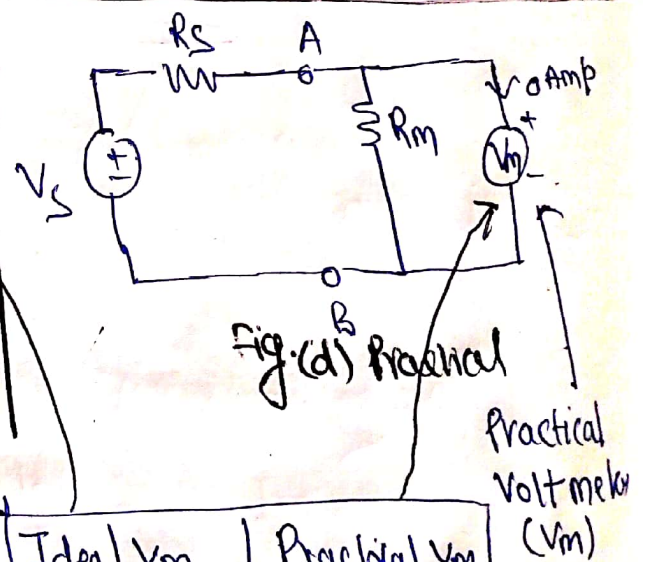


Fig. (d) Practical

Note ① Voltage always measure across the open terminal. Therefore, I have connected voltmeter across the A-B terminal so that it can measure the voltage.

② Ideal voltmeter always have Zero Amperment

Ideal V_m	Practical V_m
Internal Resistance $R_m = \infty$	Practical Internal Resistance $R_m \neq 0$

Apply KVL in Fig. (c)

$$+V_s + 0R_s + V_m$$

$$V_s = V_m$$

V_m (Voltmeter) measures the voltage across A-B terminal

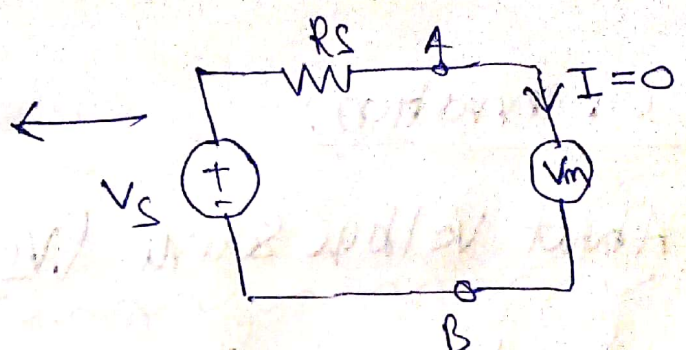


Fig. (c)

Apply KVL

$$V_s - R_s I - I R_m$$

$$I = \frac{V_s}{R_s + R_m}$$

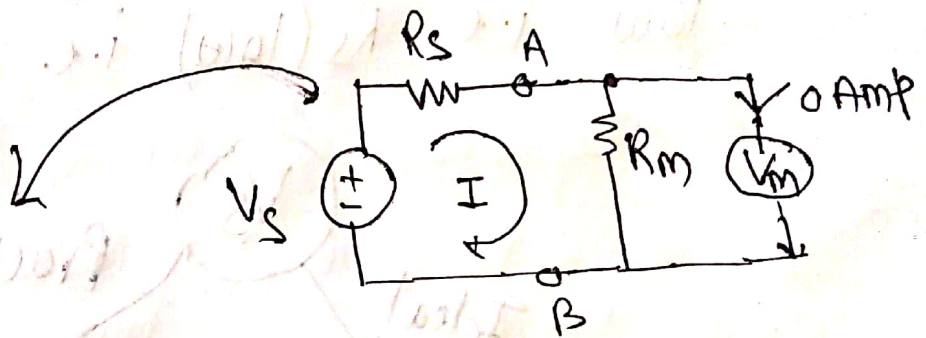




Fig. (d)

therefore,

$$V_m = I \times R_m$$

$$V_m = \frac{V_s R_m}{R_s + R_m}$$

Note

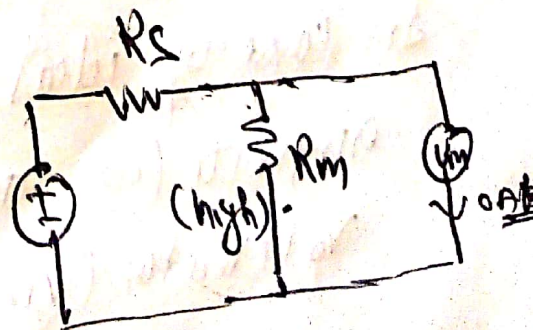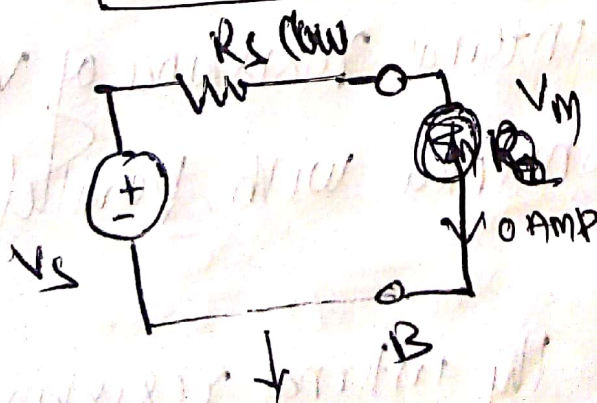


Observation:

About Voltage Source (V_s):

In ideal case, the internal resistance of V_s is zero
i.e. $R_s = 0$

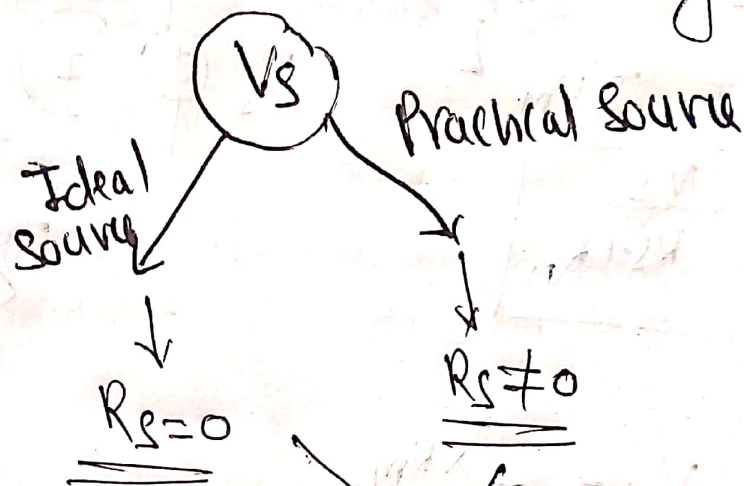In practical case, the internal resistance of V_s is low i.e. R_s (low) i.e. something value




Both are connected in series with V_s .

About Voltmeter (V_m):

In case of ideal, the internal resistance of V_m is infinity (∞) and connected with parallel to voltmeter (V_m)

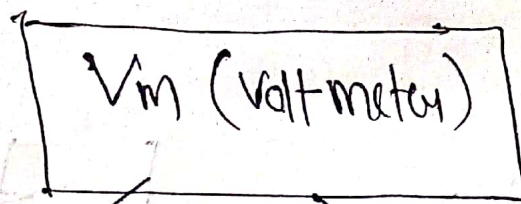In case of practical, the internal resistance of V_m is R_m (having some value) and connected with parallel to voltmeter (V_m).



Ideal Voltmeter (V_m)

Internal resistance

$$R_m = \infty$$

Connected with
Parallel to V_m

Practical Voltmeter (V_m)

Internal resistance

$$R_m = \text{high}$$

Connected with
parallel to V_m

Ammeter: It is used for measure the current across short circuit

Ideal Practical

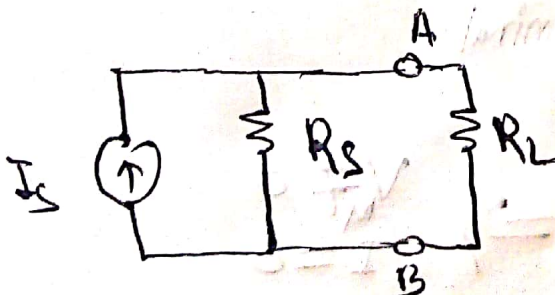


Fig. (a) Practical Current Source

$$R_s = \text{high}$$


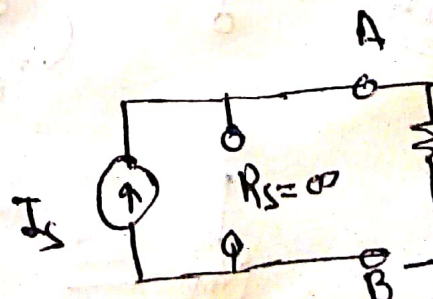
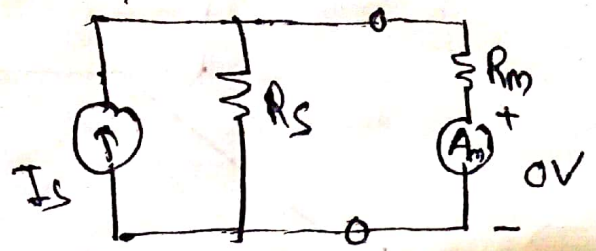



Fig. (b) Ideal Current Source

$$R_s = \text{very high} = \infty$$

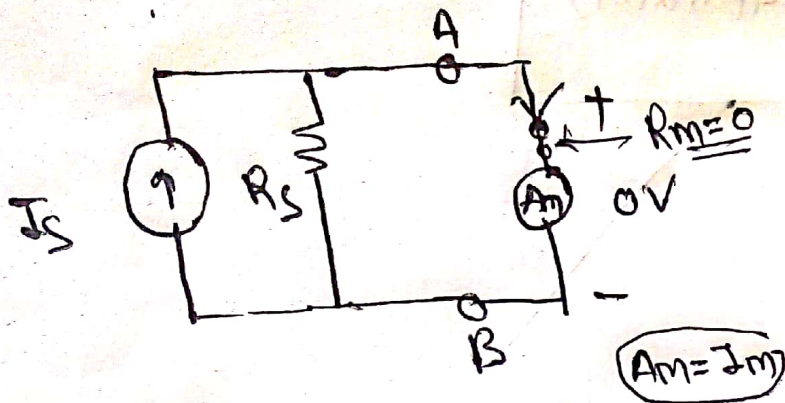

Ideal (I_m)	Practical (I_m)
① Internal Resistance $R_m = 0$	① Internal Resistance $R_m \neq 0$ (Something value)
② Voltage across ammeter is zero due to short	② Voltage across the ammeter is zero due to short circuit

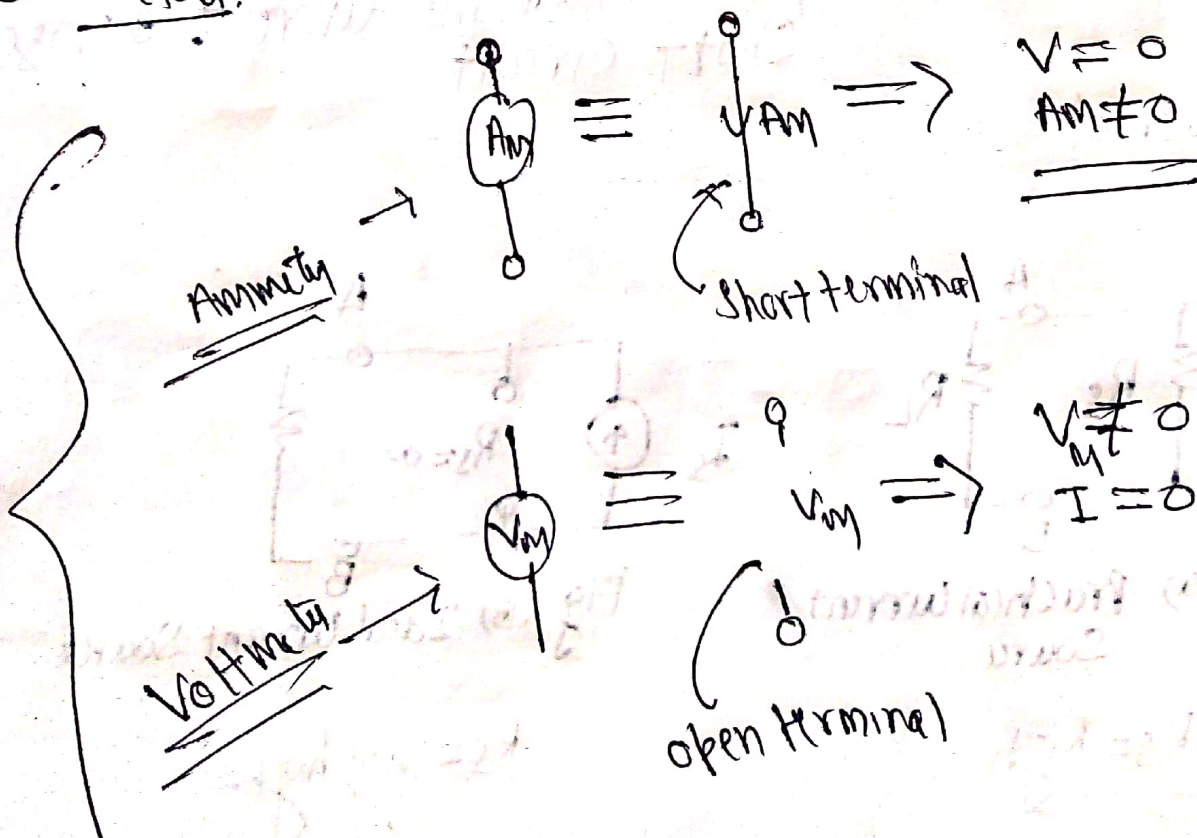③ Obj: Ammeter measure short short current.



Symbol and system
 Apply current division




$$A_m = \frac{I_s \times R_s}{R_s + R_m}$$

or I_m

$$I_m = A_m = \frac{I_s \times R_s}{R_s}$$

$$I_m = I_s$$


Fig. (c) For Ideal Ammeter

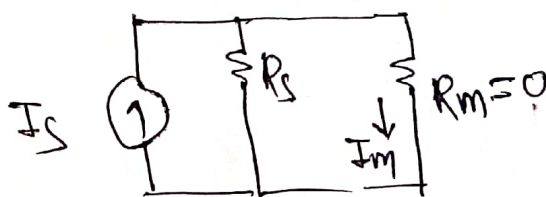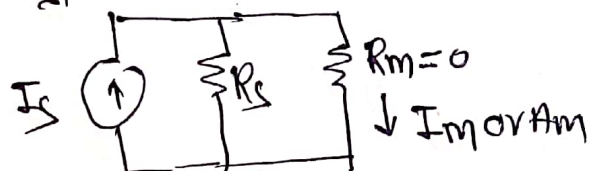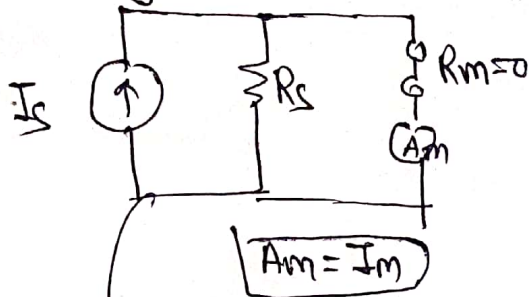

Apply current division

$$I_m = \frac{I_s \times R_s}{R_s + R_m}$$

Fig. (d) For Practical Ammeter

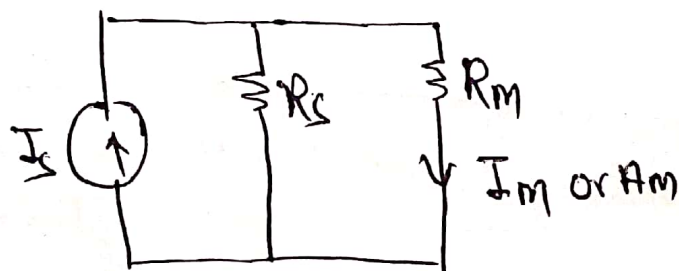

Observation:

