

Experiment 2(b)



Zener diode as voltage regulator

PAGE No. _____
DATE / / 20__

Aim :- To construct a Zener diode voltage regulator and measure its line and load regulation.

Apparatus :- Zener diode, resistor, variable DC power supply, milliammeter, voltmeter, Rheostat and wire.

Observation

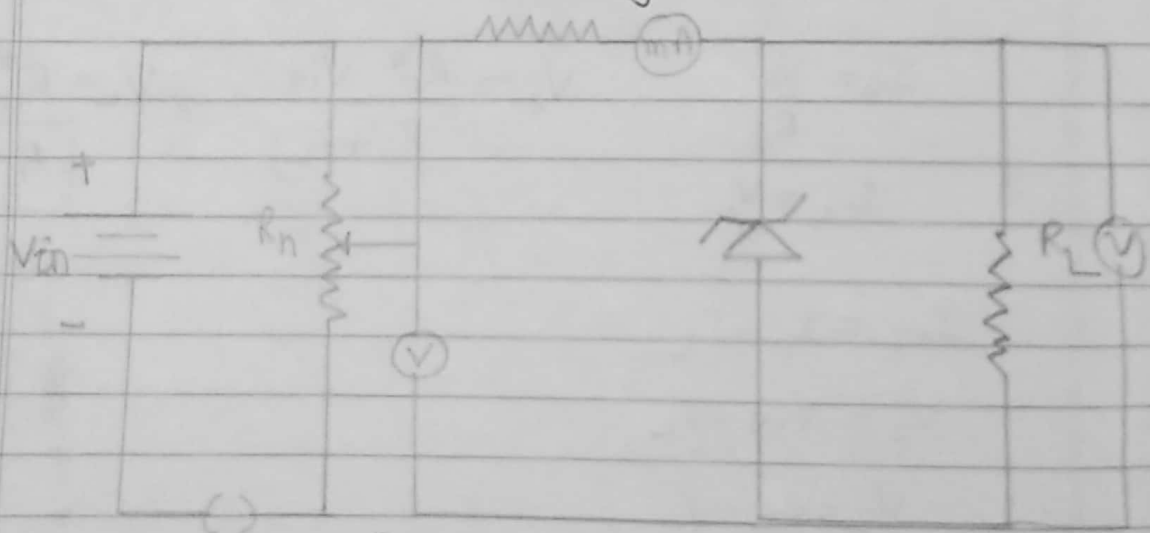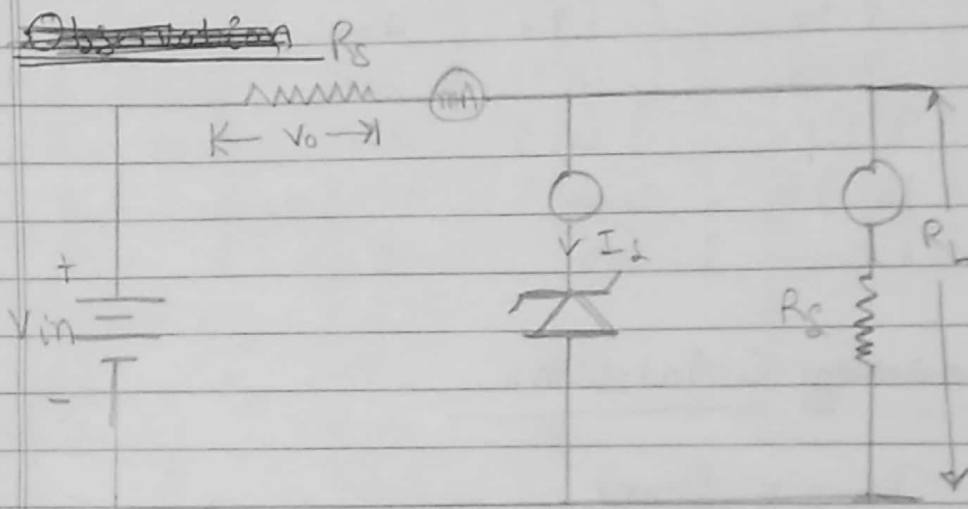

Formula used :-

(a) For line Regulation

$$\% \text{ of line Regulation} = \frac{\Delta V_o}{\Delta V_{in}} \times 100$$

(b) For load regulation

$$= \frac{V_{NL} - V_{FL}}{V_{NL}} \times 100$$

Observations

Series Resistance = 600Ω

PAGE No

DATE: / / 201

Line regulation Load Resistance = $17,000\Omega$

S.No	V_{in} in V	V_o in V	Rheostat (R_h)
1	0	0	1000
2	1.19	1.15	900
3	2.38	2.29	800
4	3.56	3.43	700
5	4.74	4.57	600
6	5.92	5.59	500
7	7.10	5.596	400
8	8.28	5.597	300
9	9.51	5.598	200
10	10.75	5.599	100
12		5.6	0.

Load Reg. Calculations

$$I_{max} = \frac{\text{Power}}{\text{Zener Voltage}}$$

$$I_s = \frac{V_s}{R_s}$$

$$V_s = \frac{R_s * V_{in}}{(R_s + R_L)}$$

$$V_L = \frac{R_L * V_{in}}{(R_s + R_L)}$$

$$I_L = \frac{V_L}{R_L}$$

$$I_z = I_s - I_L$$

$$V_s = V_{in} - V_L$$

$$V_L = V_z$$

Load Regulation Observation Table-II

PAGE No
DATE: / / 201

S.No	$R_L (\Omega)$	$V_o (V)$
1	1000	5.6
2	900	5.6
3	800	5.6
4	700	5.6
5	600	5.6
6	500	5.6
7	400	5.6
8	300	5.6
9	200	4.8
10	100	3
11	0	0

Calculations :-

Results :-

$$(a) \text{ of line Regulation} = \frac{5.6 - 1.177}{12 - 1.19} \times 100 = 40.91$$

$$(b) \text{ of load Regulation} = \frac{5.6 - 4.8}{5.6} \times 100 = 14.28$$

